

EE1002

Introduction to Circuits and Systems

Part 1 : Lecture 8

DC Transients

Comparison of capacitor and inductor

Cap

Energy due to static charge

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

DC-Steady state behaviour:

$$i_c = 0 \text{ as } \frac{dv_c}{dt} = 0$$

↳ Open Lkt

$$\text{Series: } \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\text{parallel } C_{eq} = C_1 + C_2 + C_3$$

$$\text{Energy} = \frac{1}{2} \cdot C \cdot V^2$$

Ind

Energy due to moving charge

$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$v_L = 0 \text{ as } \frac{di_L}{dt} = 0$$

↳ Short circuit.


$$\text{Series } L_{eq} = L_1 + L_2 + L_3$$

$$\text{parallel } \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

$$E_{eq} = \frac{1}{2} L \cdot I^2$$


DC Steady-state of circuits containing L and C

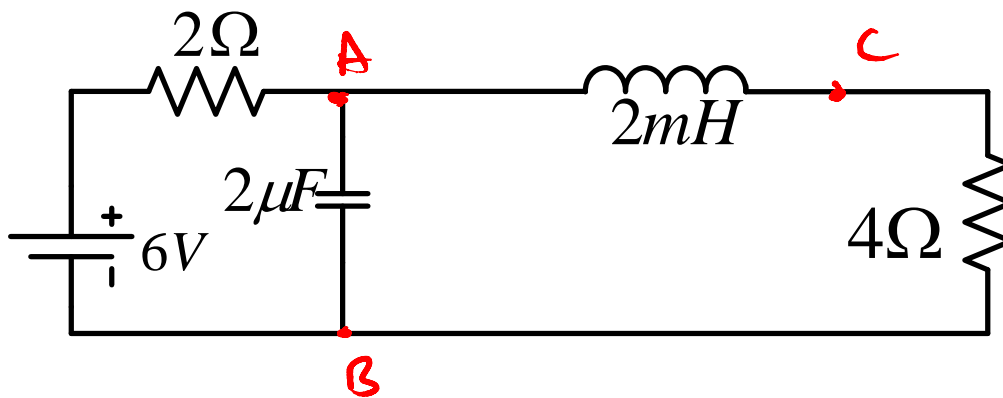Find the energy stored in the inductor and the capacitor.



$$E_{2\mu F} = \frac{1}{2} \times 2 \times 10^{-6} \times 4^2 \text{ J.}$$
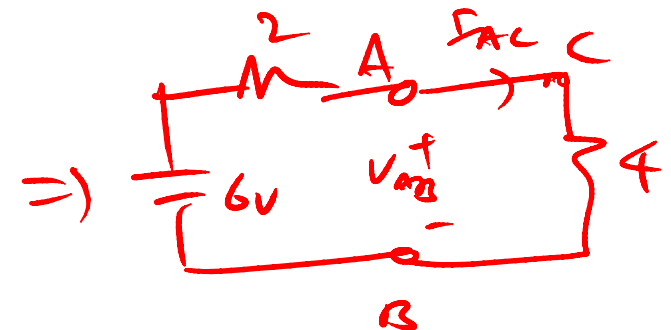
$$E_{2mH} = \frac{1}{2} \times 2 \times 10^{-3} \times 1^2 \text{ J.}$$



$$V_{AB} = 6 \times \frac{4}{2+4} = 4V.$$

$$I_{AC} = \frac{6}{2+4} = 1A.$$


DC Transients

- Understanding DC transients
- Developing the time-function for the transients
- Solving First-order transients in circuits
- Preparing for Lab 4 and 5

DC Transients

- The time-varying voltages and currents resulting from the adding or removing voltage and current source to circuits containing energy storage elements, are called **transients**.

RC Circuit with a DC source

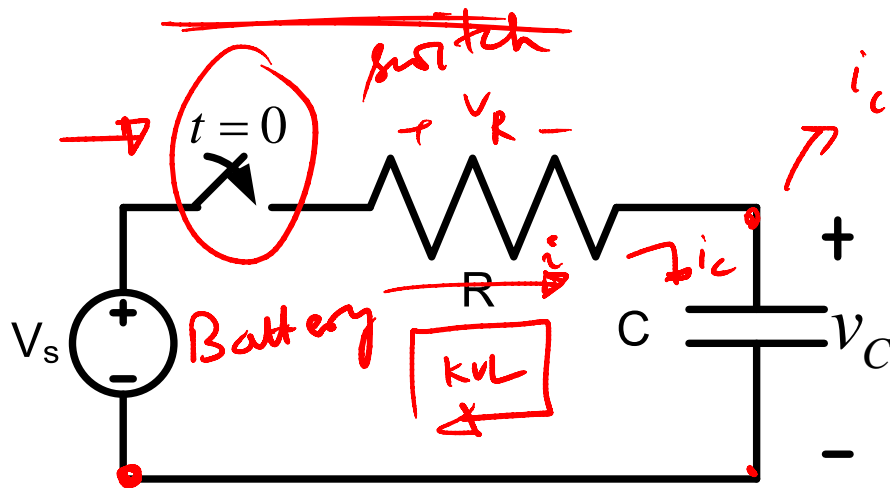

$$i_c = C \cdot \frac{dv_c}{dt}$$

$$-V_s + v_R + v_c = 0$$

$$v_R = iR = RC \frac{dv_c}{dt}$$



$$-V_s + RC \frac{dv_c}{dt} + v_c = 0$$

First order ODE

$$RC \frac{dv_c}{dt} + v_c = V_s$$

$v_c(t)$

At $t=0^+$

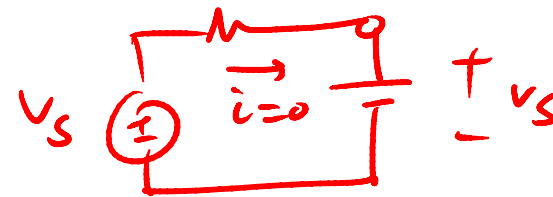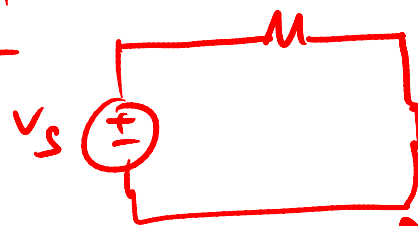


$$V_s = 5V$$

$$R = 100\Omega$$

$$C = 4700 \times 10^{-6} F$$

$$5 \times RC = 5 \times 100 \times 4700 \times 10^{-6}$$

RL Circuit with DC source


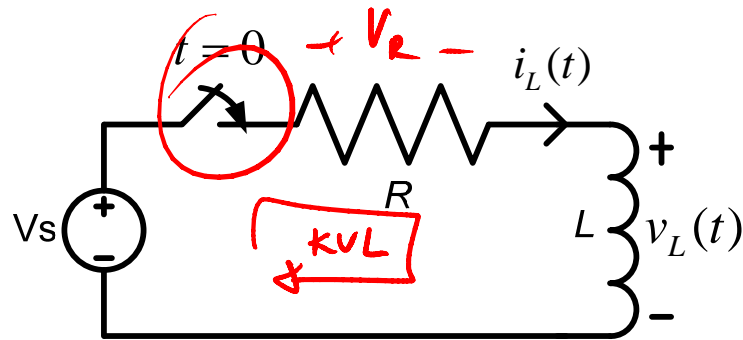


$$-V_s + V_R + V_L = 0$$

$$-V_s + iR + L \frac{di}{dt} = 0 \quad i = i_L(t)$$

$$\frac{L}{R} \frac{di}{dt} + i = \frac{V_s}{R}$$

Rearrange.

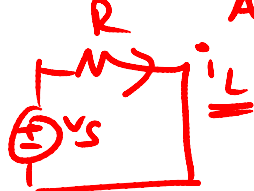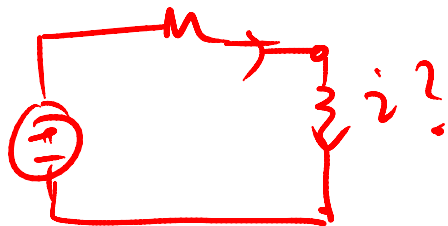

At $t=0^-$: Before sw is closed


$t=0^+$ After sw is closed

$$i_L(0^-) = i_L(0^+)$$

At $t=0^+$ $i_L = 0$

$$V_L = L \cdot \frac{di_L}{dt}$$
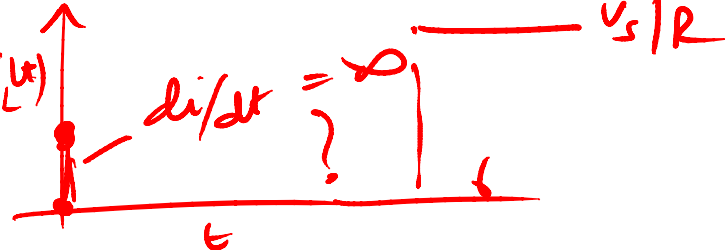
$$\frac{di_L}{dt} = \frac{V_L}{L} = \frac{V_s}{L}$$



First order circuits with DC excitation

Time constant

$$\tau \frac{dx}{dt} + x = K$$

K : is a constant.

$x(t)$
DC steady-state value of x ?
 $\frac{dx}{dt} = 0 \Rightarrow x_{ss} = \underline{\underline{K}}$

Solution of the differential equation:

$$\underline{x(t)} = \underline{(x(0) - K)e^{-\frac{t}{\tau}} + K}$$


\checkmark \checkmark \checkmark

$V_S = V_{TH}$ $x(0) = x(t=0)$
 $\frac{V_S}{R} = \frac{V_{TH}}{R_{TH}}$ initial value
 $\tau = RC, LR$

Shape of First-order transient

$$\underline{x(t) = K + (x(0) - K) \times e^{-t/\tau}}$$

t	<u>$(1 - e^{-t/\tau})$</u>
τ	<u>0.632121</u>
2τ	<u>0.864665</u>
3τ	<u>0.950213</u>
4τ	<u>0.981684</u>
5τ	<u>0.993262</u>

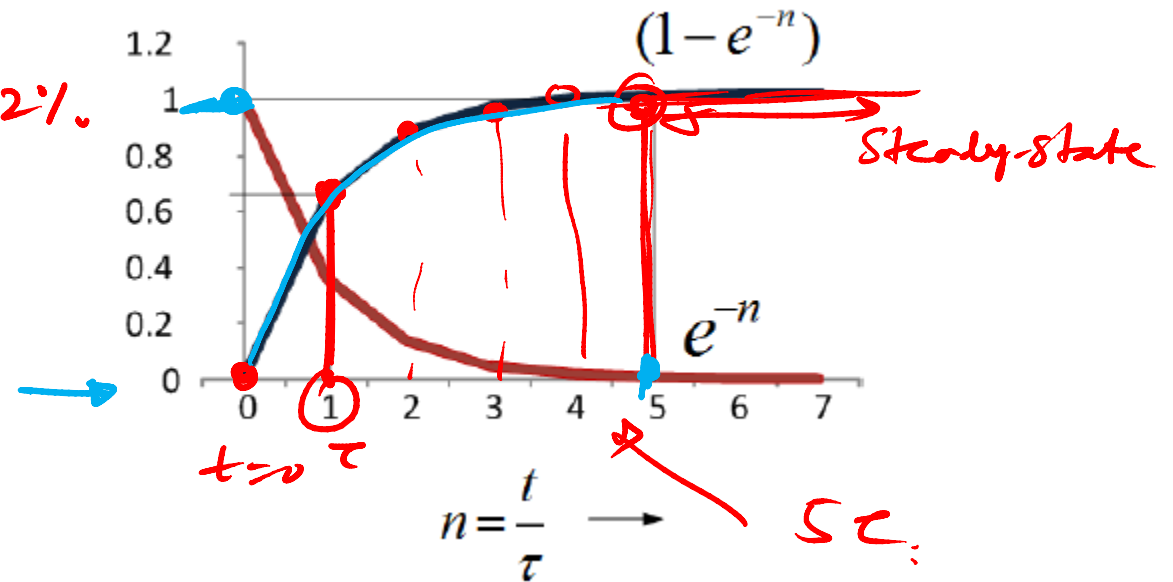

RC and RL comparing to the general form

✓ $\tau \frac{dx}{dt} + x = K \Rightarrow$ Solution: $x(t) = (x(0) - K)e^{-\frac{t}{\tau}} + K$

$$RC \frac{dv_c}{dt} + v_c = V_s$$

$$x(t) = v_c(t)$$

$$\tau = R \cdot C \rightarrow \text{Time constant}$$

$$K = V_s$$

$$v_c(t) = [v_c(0) - V_s] e^{-\frac{t}{RC}} + V_s$$

$$\frac{L}{R} \frac{di_L}{dt} + i_L = \frac{V_s}{R}$$

$$x(t) = i_L(t)$$

$$\tau = \frac{L}{R}$$

$$K = \frac{V_s}{R}$$



$$i_L(t) = \left[i_L(0) - \frac{V_s}{R} \right] e^{-\frac{t}{L/R}} + \frac{V_s}{R}$$

Steps for solving RC and RL circuits


- Use DC steady-state analysis of the circuit
① before the transient starts to find initial value
– $v_c(0^-) = v_c(0^+), i_L(0^-) = i_L(0^+).$
- Use Thevenin's equivalent circuit to
② reduce any circuit to the standard form
- Find the time constant and DC voltage
③ from the Thevenin's equivalent

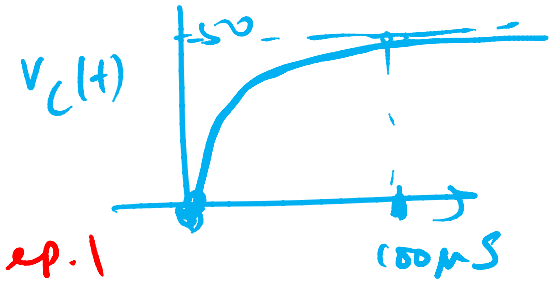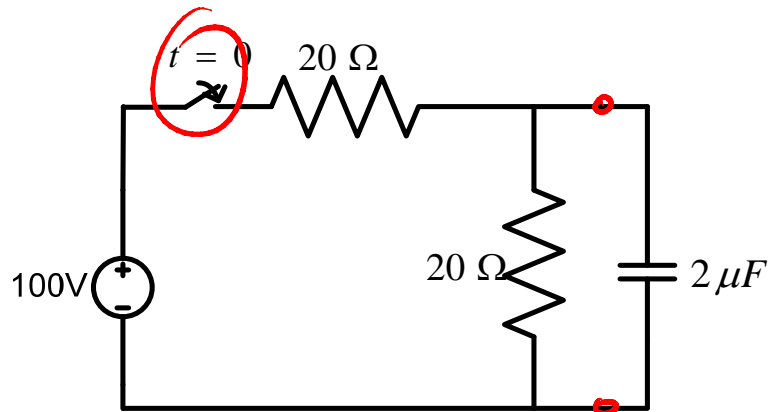Example



Find the capacitor voltage as a function of time.



Step 1

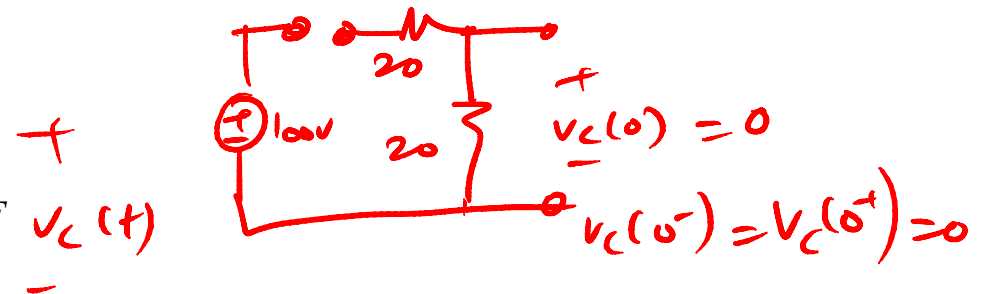

Step 2

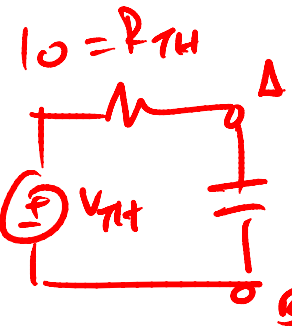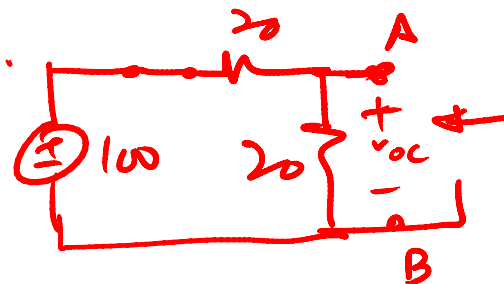

$$\tau = R_{TH} C$$


$$= 10 \times 2 \mu F$$

$$= 20 \mu S.$$


Step 3

$$v_C(t) = \left[v_C(0) - V_{TH} \right] e^{-t/\tau} + V_{TH}$$

Example

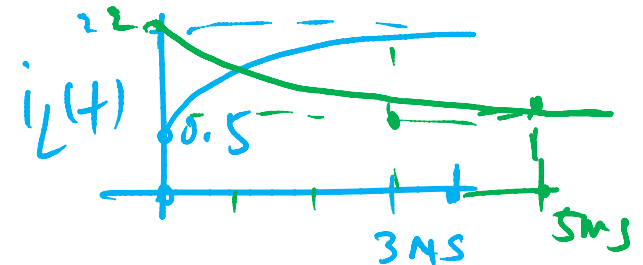


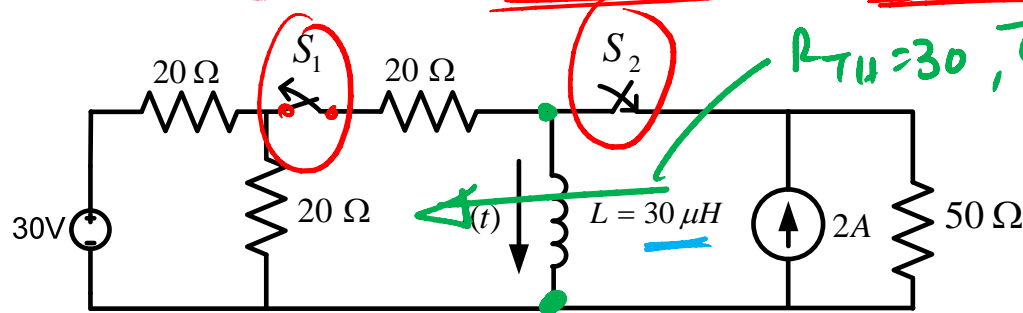Find the inductor current as a function of time. Before $t=0$, switch S_1 was closed and S_2 was open. At $t=0$, S_1 is opened and S_2 is closed. Find the current $i(t)$ after $t=0$.




$R_{TH} = 30, \tau = 1\mu s$

Step 1. Find $i_L(0^+) = i_L(0^-)$

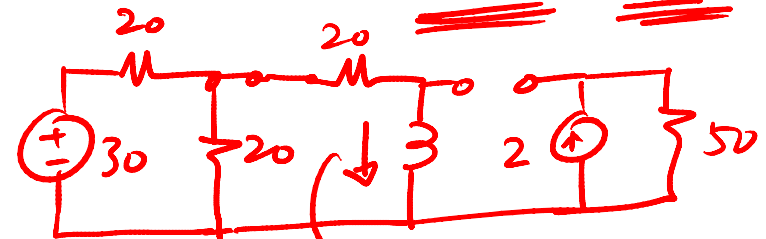

$i_L(0^-) = 0.5A$
 $= i_L(0^+)$

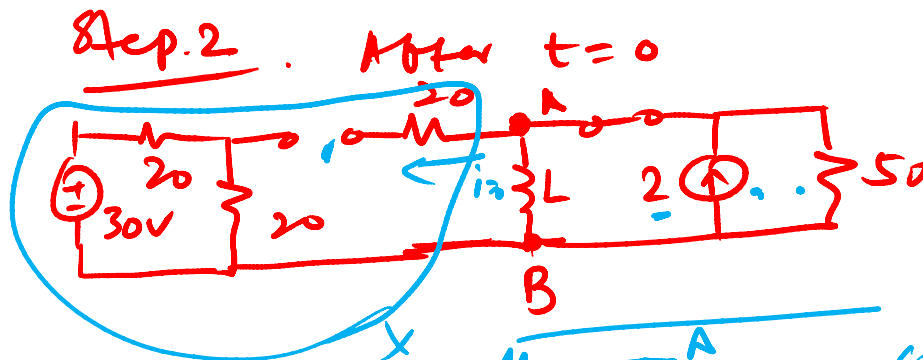

$\tau = \frac{L}{R_{TH}} = \frac{30}{50} \mu s$

Step 3

$$i_L(t) = \left[i_L(0) - \frac{V_{TH}}{R_{TH}} \right] e^{-t/\tau} + \frac{V_{TH}}{R_{TH}}$$

$$= [0.5 - 2] e^{-t/\tau} + 2A$$

Appendix

Solving the First order ordinary linear differential equation with a constant forcing function.

First order circuits with DC excitation

$$\tau \frac{dx}{dt} + x = K \quad K \text{ is a constant.}$$

- Two parts of the general solution
 - Particular solution (forced solution)
 - Complementary solution (homogeneous eqn)

Particular solution

- The particular solution is obtained from the forcing function.
- It is normally of the same functional form as the forcing function and its derivatives.
- A table containing various forcing functions and their corresponding particular solutions are readily available.
- http://www.efunda.com/math/ode/linearde_undeterminedcoeff.cfm

When forcing function is DC

- The particular solution is a constant

$$\tau \frac{dx_p}{dt} + x_p = K$$

$$\text{Let } x_p = K'.$$

$$\text{Then } 0 + K' = K \Rightarrow K' = K$$

$$\text{i.e. } x_p = K$$

Homogeneous equation

$$\tau \frac{dx_c(t)}{dt} + x_c(t) = 0$$

$$\frac{dx_c(t)/dt}{x_c(t)} = \frac{-1}{\tau}$$

$$\ln[x_c(t)] = \frac{-t}{\tau} + c$$

$$x_c(t) = e^c e^{-\frac{t}{\tau}} = K'' e^{-\frac{t}{\tau}}$$

Complete Solution

$$\tau \frac{dx}{dt} + x = K$$

$$x(t) = x_c + x_p = K'' e^{-\frac{t}{\tau}} + K$$

$$x(0) = K'' e^{-0} + K \Rightarrow K'' = x(0) - K$$

$$x(t) = (x(0) - K) e^{-\frac{t}{\tau}} + K$$