

# EE1002

# Introduction to Circuits and Systems


Part 1 : Lecture 6  
Equivalent Circuits  
Nonlinear Elements  
Maximum Power

# Equivalent Circuits

- One-port networks and equivalent circuits

- Thevenin's equivalent circuit
- Norton's equivalent circuit


$\rightarrow$  linear circuit  
ckt.

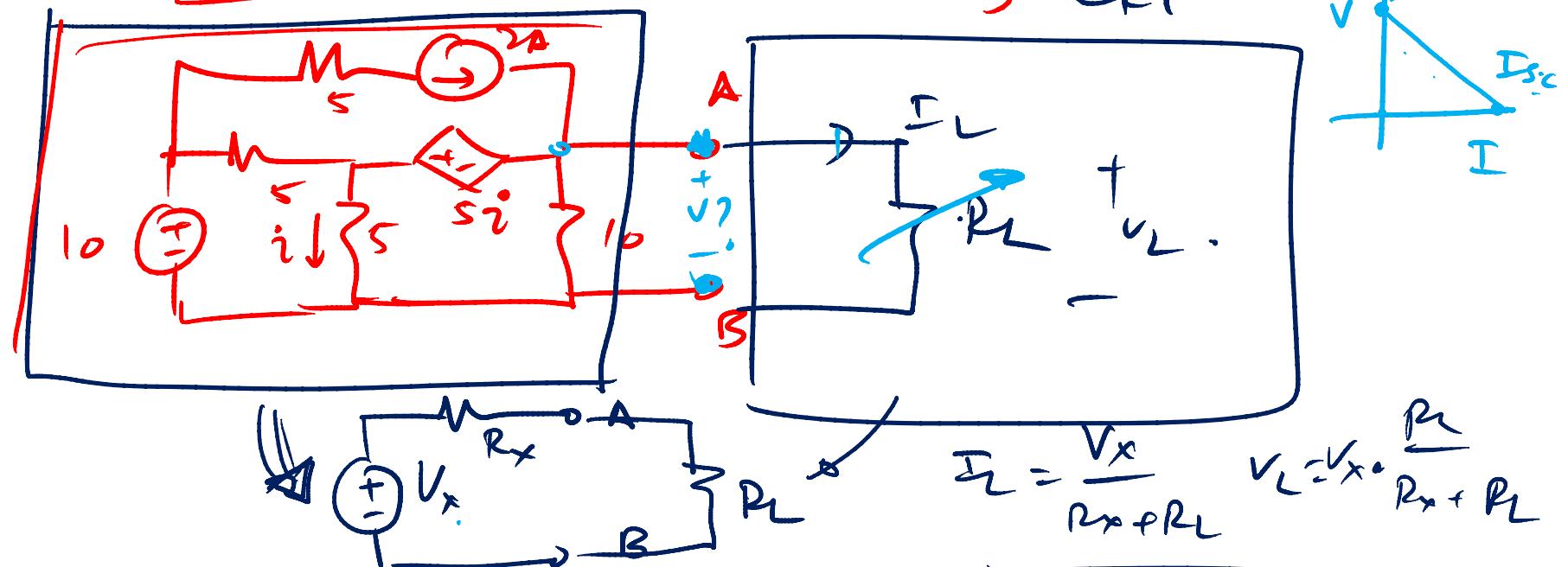

# One-port networks and equivalent circuits

- Two-terminal circuits can be replaced by an **equivalent circuit** consisting of a source and a resistance.
- A voltage source with a series resistance (Thevenin equivalent circuit)
- A current source with a parallel resistance (Norton equivalent circuit)


# Thevenin equivalent

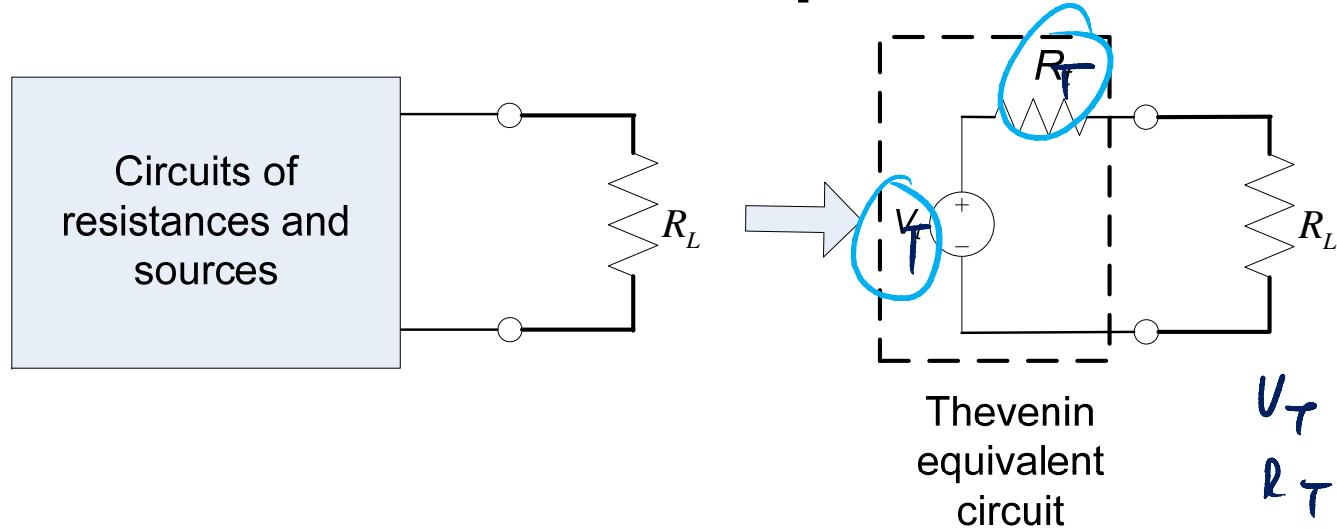

- A voltage source in series with a resistance
- The voltage source is called Thevenin's voltage
- The series resistance is called Thevenin's resistance

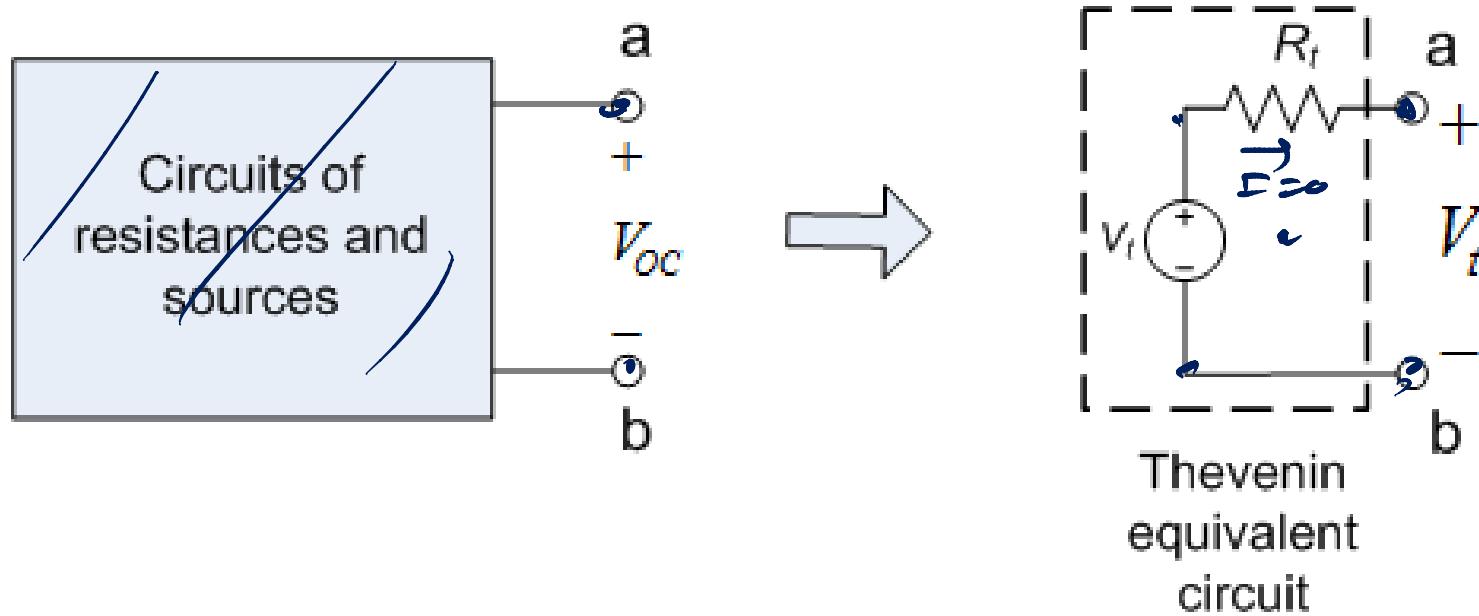
# Thevenin Voltage

- Value of the voltage source is the open circuit voltage between the two terminals
- Called the Thevenin voltage



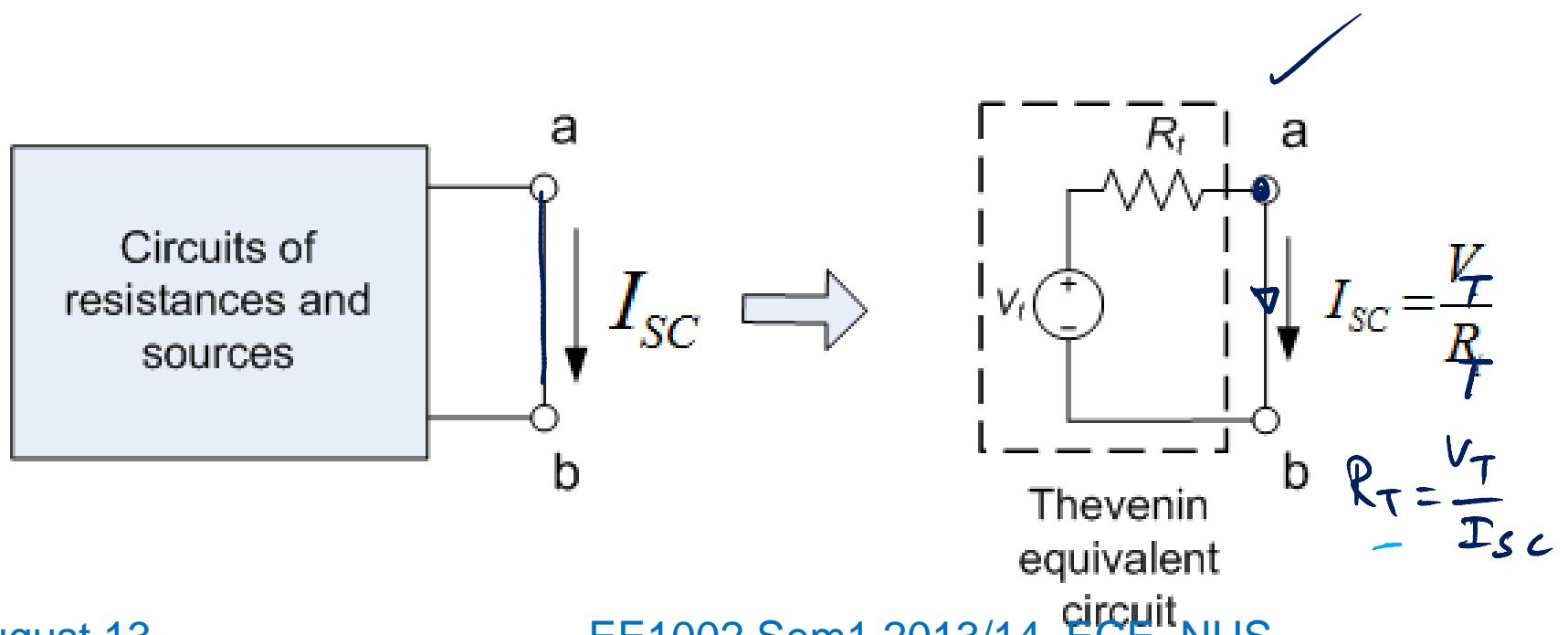
# Thevenin Resistance

- Find the **short circuit current** between the two terminals
- Calculate the Thevenin resistance



# Norton Equivalent

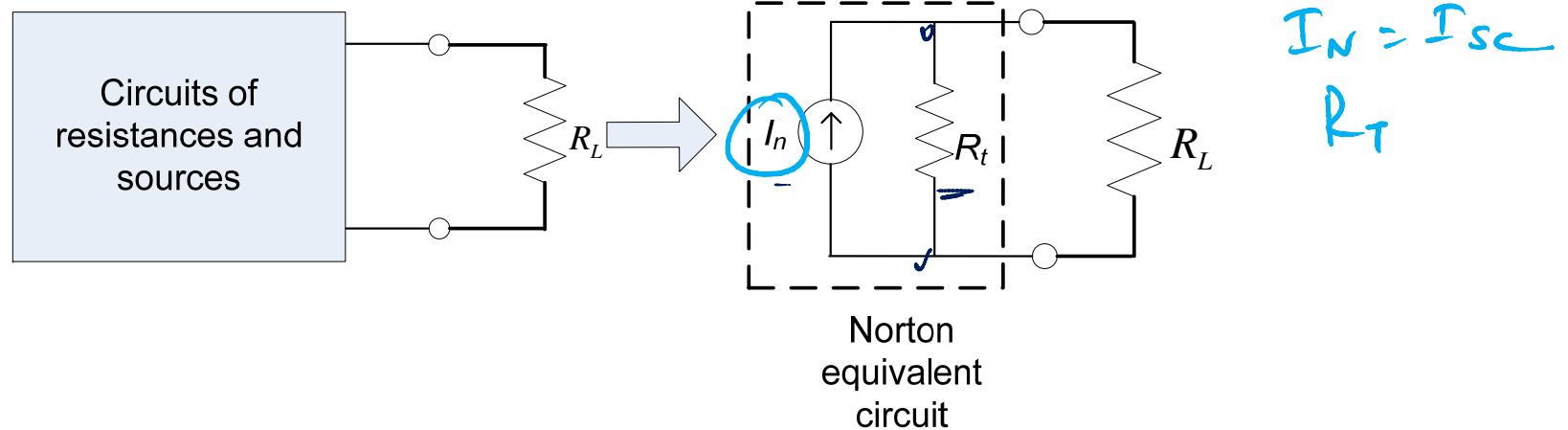


- A current source in parallel with a resistance
- The current source is called Norton's current
- The series resistance is called Thevenin's resistance
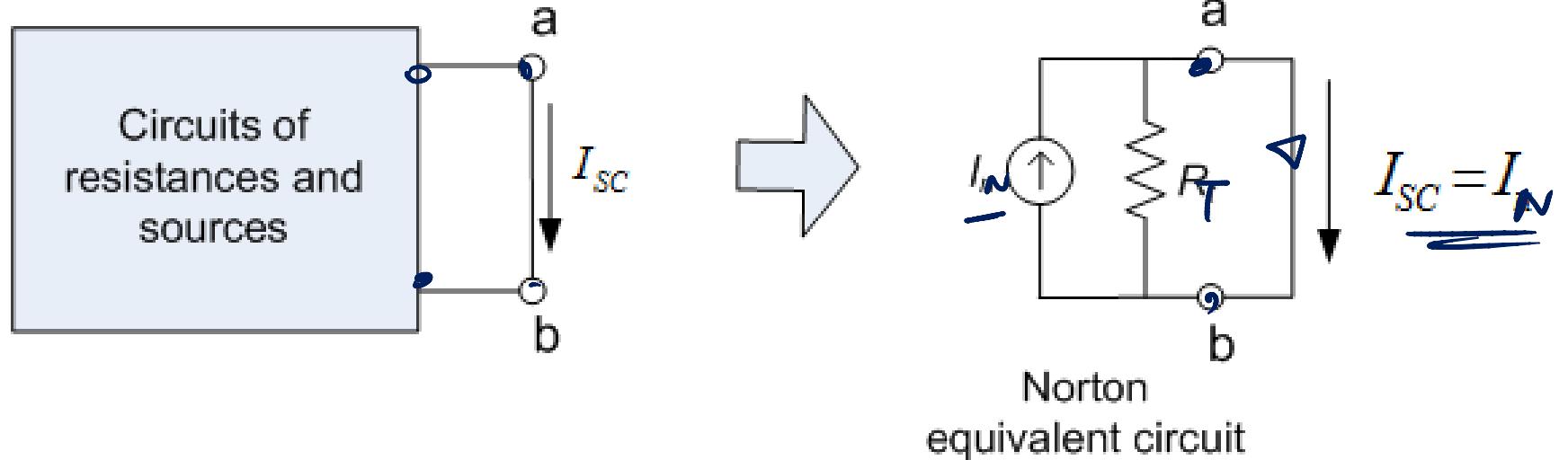
# Norton's current

- Value of the current source is the **short circuit current** between the two terminals
- Called the Norton's current

$$I_{SC} = I_N \times \frac{R_T}{R_T + 0}$$



# Steps to find the equivalent circuits

- Obtain the open circuit voltage between the two terminals – Thevenin's voltage
- Obtain the short circuit current between the two terminals – Norton's current
- Calculate the Thevenin's resistance as

$$R_T = \frac{V_{OC}}{I_{SC}}$$



KCL at node a:

$$\frac{U-24}{4} - 3 + \frac{U}{12} = 0$$

$$\Rightarrow 3(U-24) - 36 + U = 0 \Rightarrow 4U = 72 + 36 = 108 \Rightarrow U = 27V = V_{OC}$$
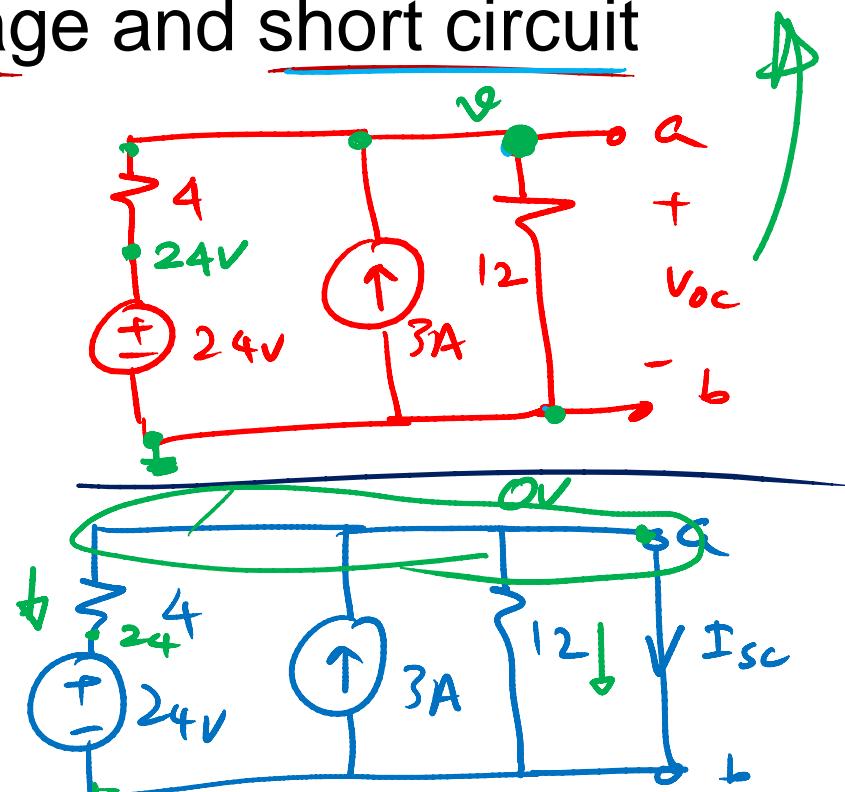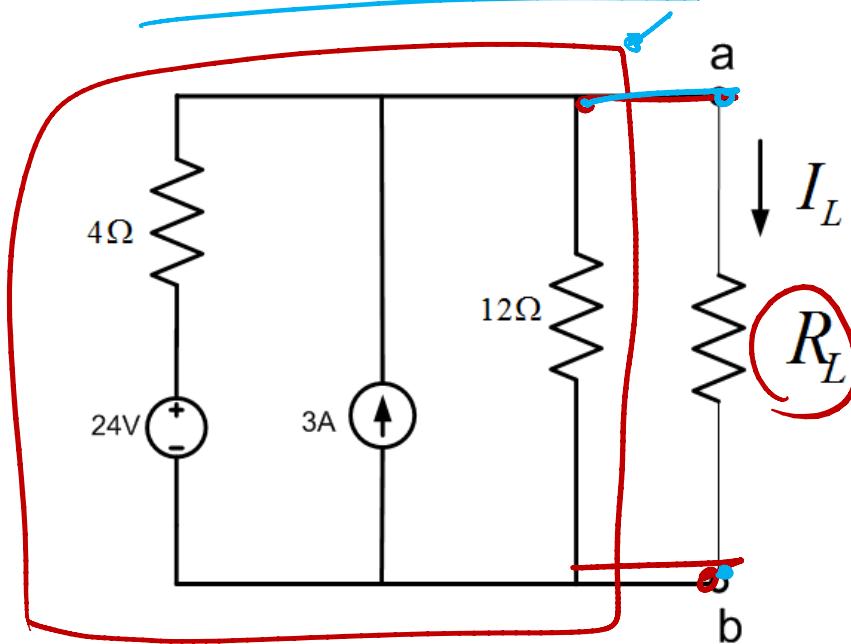
## Example2

To find open circuit voltage and short circuit current of the circuit.



$$\text{KCL : } \frac{U-24}{4} + (-3) + 0 + I_{sc} = 0 \Rightarrow I_{sc} = 9A$$

$$R_T = \frac{V_{oc}}{I_{sc}} = \frac{27}{9} = 3\Omega$$

## ~~Example 2~~ Contd.




- { 1). Ohm's law , P.S.C.
  - 2). KCL, & KVL
  - 3). Node voltage Analysis , Mesh Current Analysis .
  - 4). Superposition - Kill Sources -
  - 5). Equivalent Circuits. Thev., Norton
  - 6). Nonlinear Elements - Graphical Analysis .  
(Load line)
  - 7). Maximum Power Transfer
- Mid term. I syllabus .

KCL at v:

$$i = \frac{24-v}{4}$$
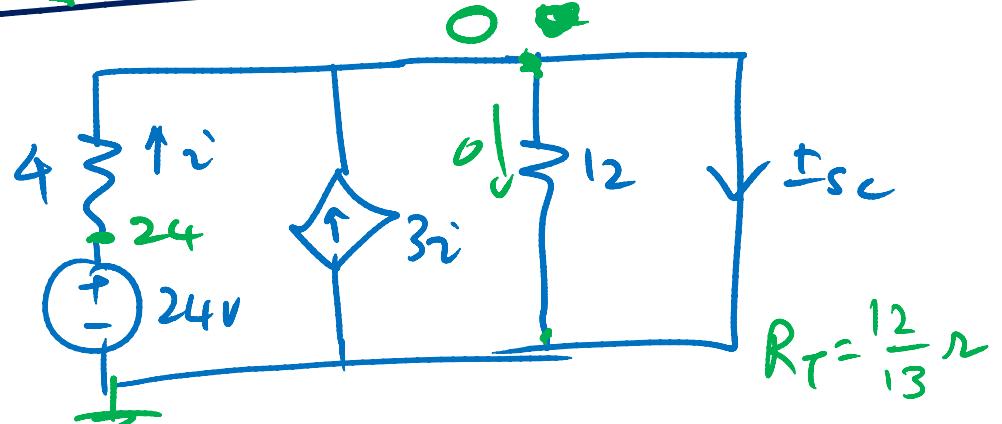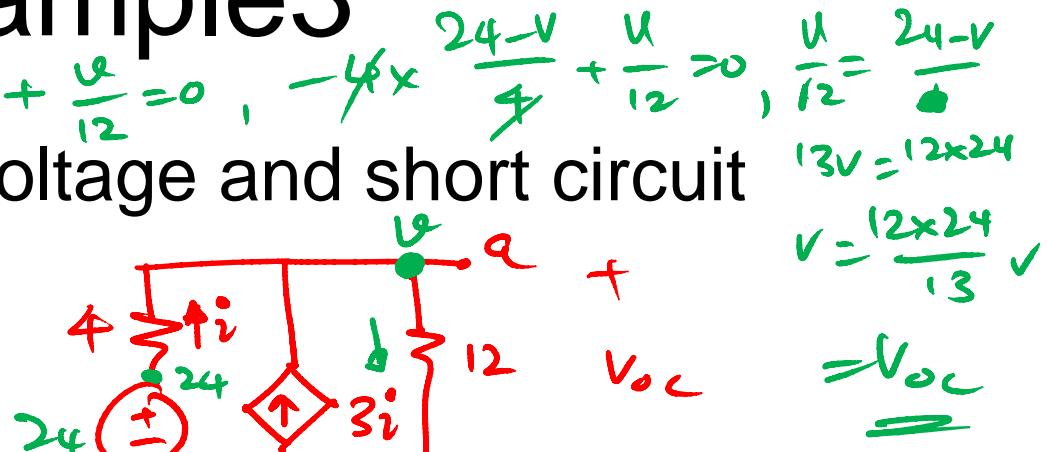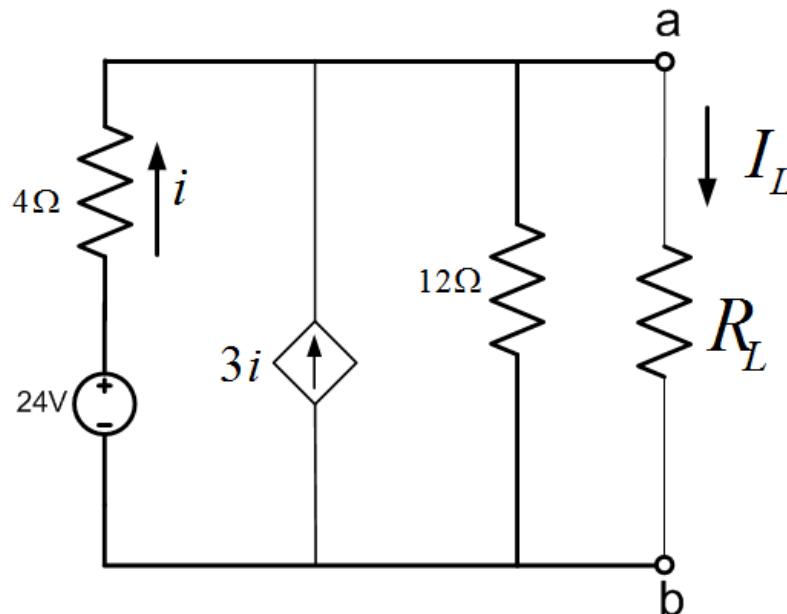
## Example 3

To find open circuit voltage and short circuit current of the circuit



KCL :

$$i = \frac{24-0}{4} = 6A$$



$$-4i + I_{sc} = 0 \Rightarrow I_{sc} = 24A.$$

# Other ways to find Thevenin Resistance ✓

- If the circuit consists of independent sources only (**can not use this if there are dependent sources**) and resistances,
  - Kill all the sources. This would result in a purely resistive network
  - Find the equivalent resistance between the two terminals, by repeated application of series parallel rule
  - Thevenin resistance is equal to the equivalent resistance

# Example1

Finding Thevenin resistance

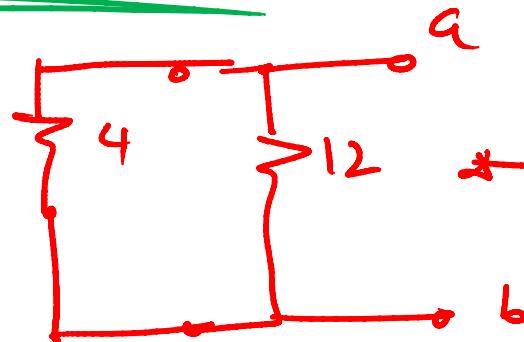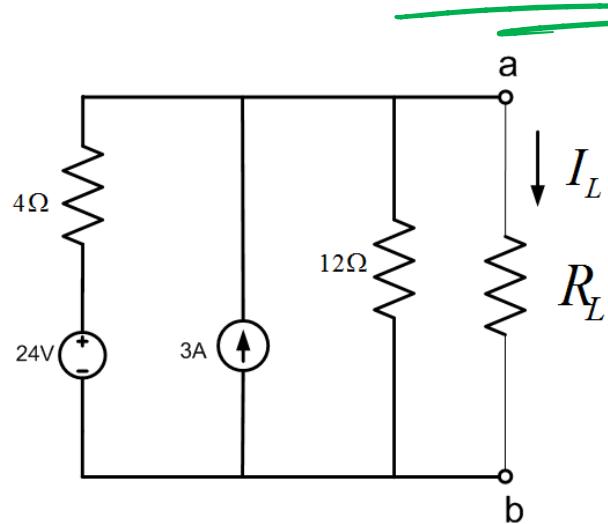



$$\begin{aligned}R_{eq} &= \frac{4 \times 12}{4 + 12} \\&= \frac{48}{16} \\&= 3\Omega.\end{aligned}$$

# Other ways to find Thevenin Resistance

- Test source method is used if the circuit contains dependent sources
  1. Kill the independent sources  
(Do not kill the dependent sources)
  2. Apply a known source (either a voltage or current source) between the two terminals
  3. Find the voltage and current across the terminals by solving the circuit
  4. Then calculate Thevenin's resistance as voltage divided by current.
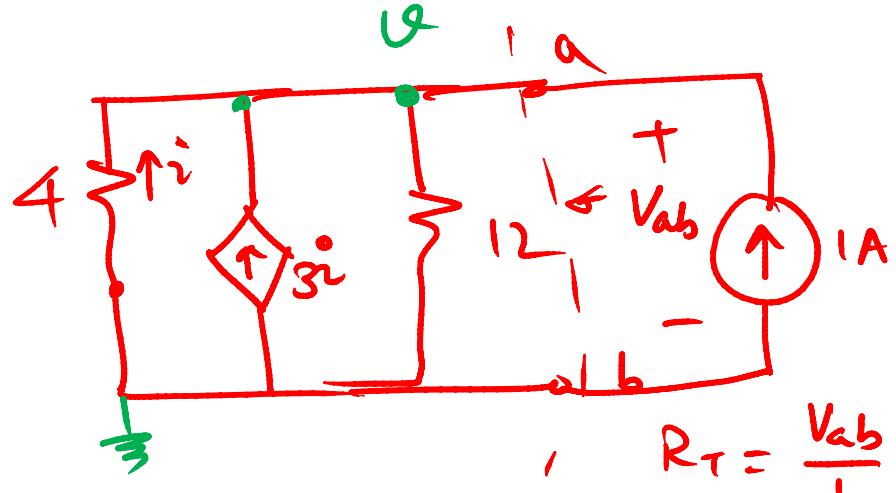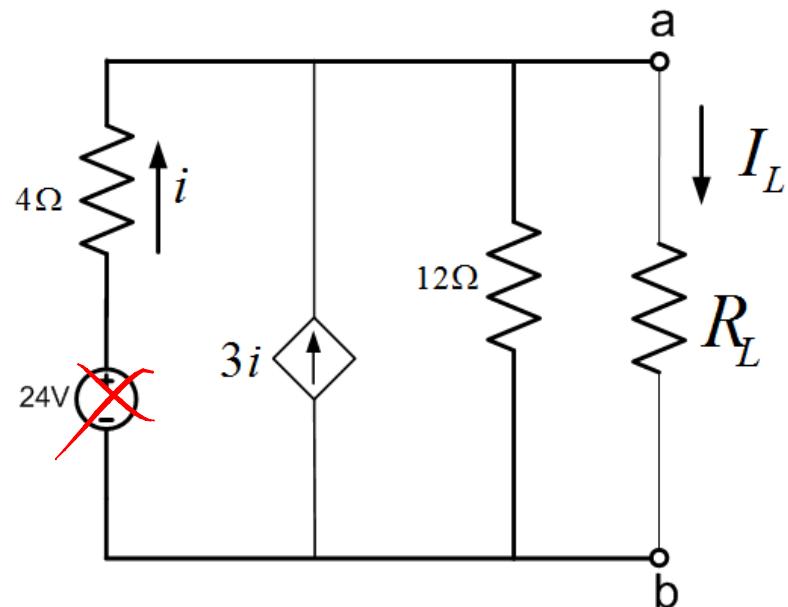
# Example2

Finding Thevenin resistance – Test source method




$$\begin{aligned}
 & \text{KCL at node } a: i_1 - i_2 - 3i = 0 \\
 & i_1 = \frac{V_a - V_b}{4} = -\frac{V_b}{4} \\
 & -i_2 + \frac{V_b}{12} - 1 = 0 \\
 & +4 \times \left(\frac{V_a}{4}\right) + \frac{V_a}{12} - 1 = 0 \\
 & V_a = \frac{12}{13} V \\
 & V_{ab} = \frac{12}{13} V \\
 & R_T = \frac{V_{ab}}{1} = \frac{12}{13} \Omega
 \end{aligned}$$


Mid-term  
will be  
in 6<sup>th</sup> week  
~~Thursday~~
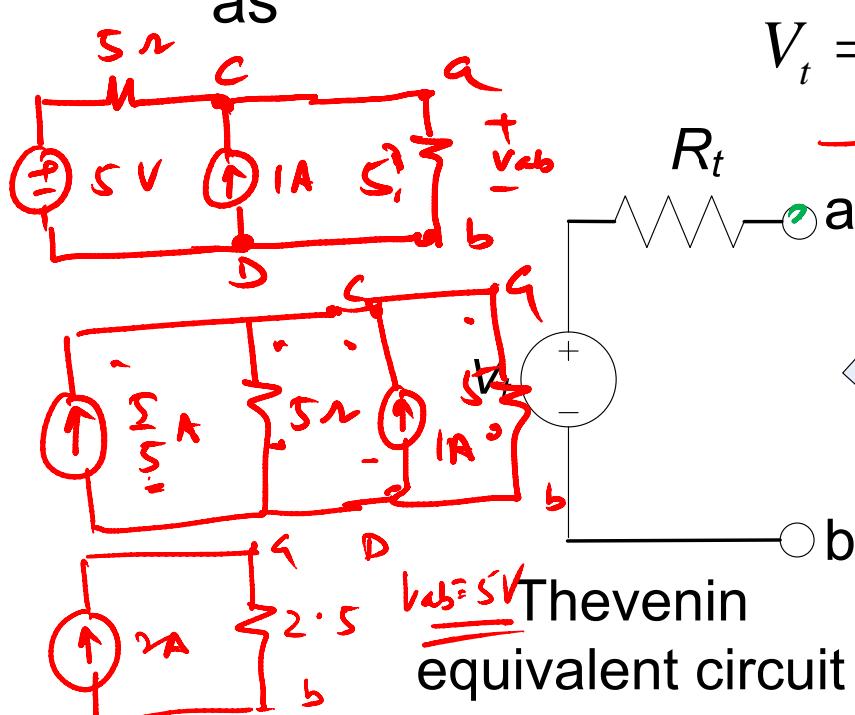
# Source Conversion

- A voltage source with a series resistance is equivalent to a current source with the resistance in parallel.
- The values of the voltage and current source are given as






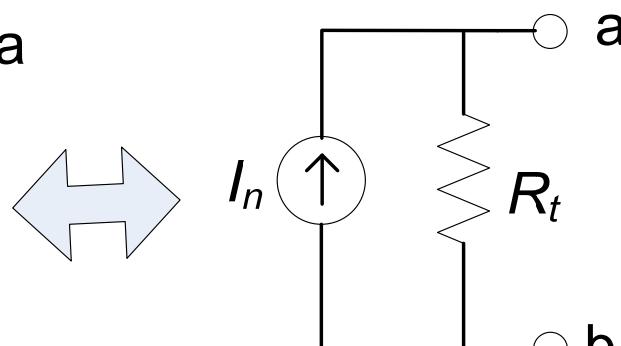
$$V_t = I_n R_t, \quad I_n = \frac{V_t}{R_t}$$




Norton  
equivalent circuit
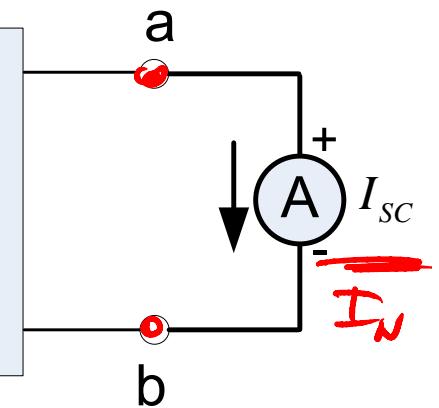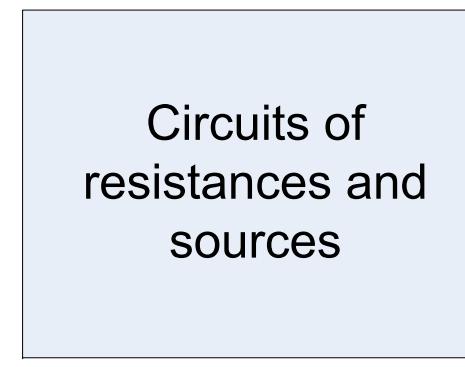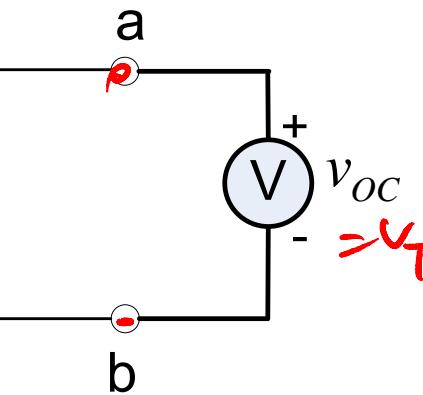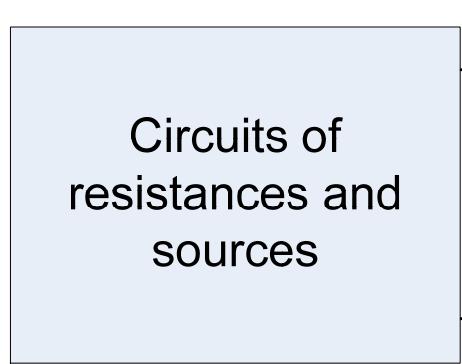
# Experimental determination of Thevenin and Norton equivalents



$$R_T = \frac{V_{OC}}{I_{SC}}$$

# Maximum power transfer

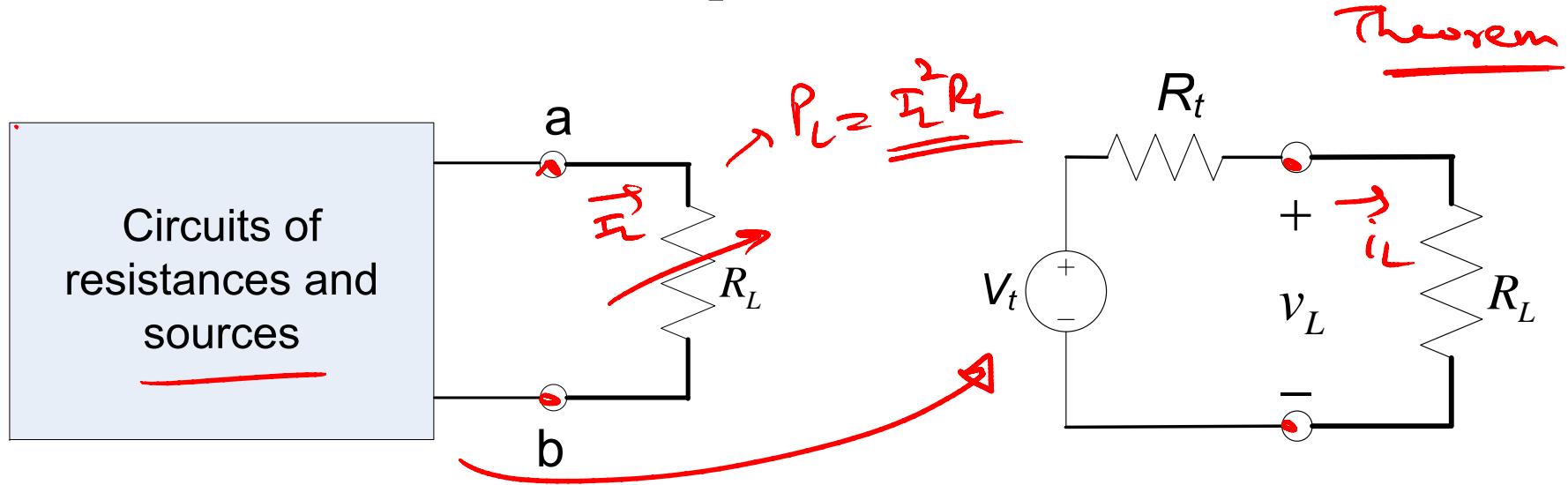

$$i_L = \frac{v_T}{R_L + R_T}$$

$$P_L = i_L^2 R_L = \frac{v_T^2}{(R_L + R_T)^2} R_L$$

$$\underline{P_L(R_L)} \quad f = \gamma(x)$$


$$\frac{dP_L}{dR_L} = \frac{v_T^2 (R_L + R_T)^2 - 2v_T^2 R_L (R_L + R_T)}{(R_L + R_T)^4} = 0$$

$$v_T^2 (R_L + R_T)^2 - 2v_T^2 R_L (R_L + R_T) = 0$$


$R_L = R_T$
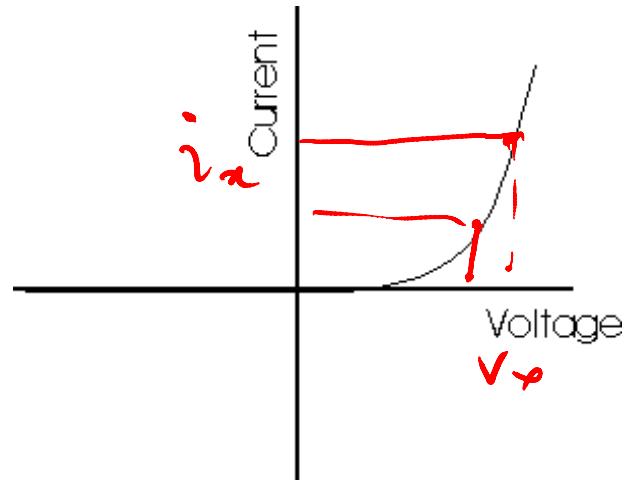
# Nonlinear elements

- Nonlinear elements may not have an analytical function
- How to solve a linear circuit with one nonlinear element?




Diode  
~~Ex~~  
 $i = f(v)$

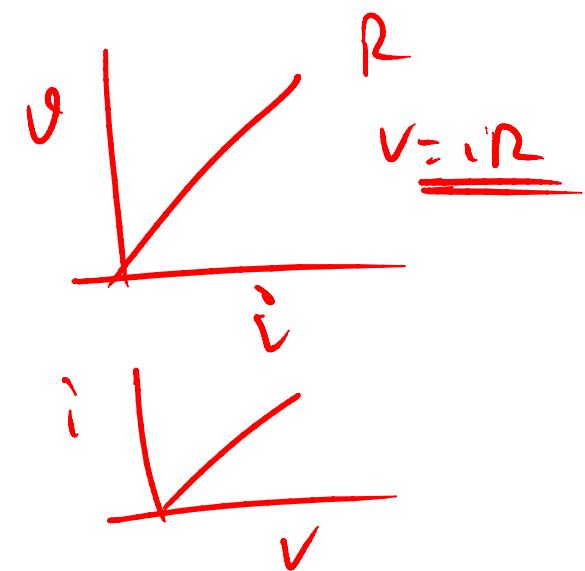

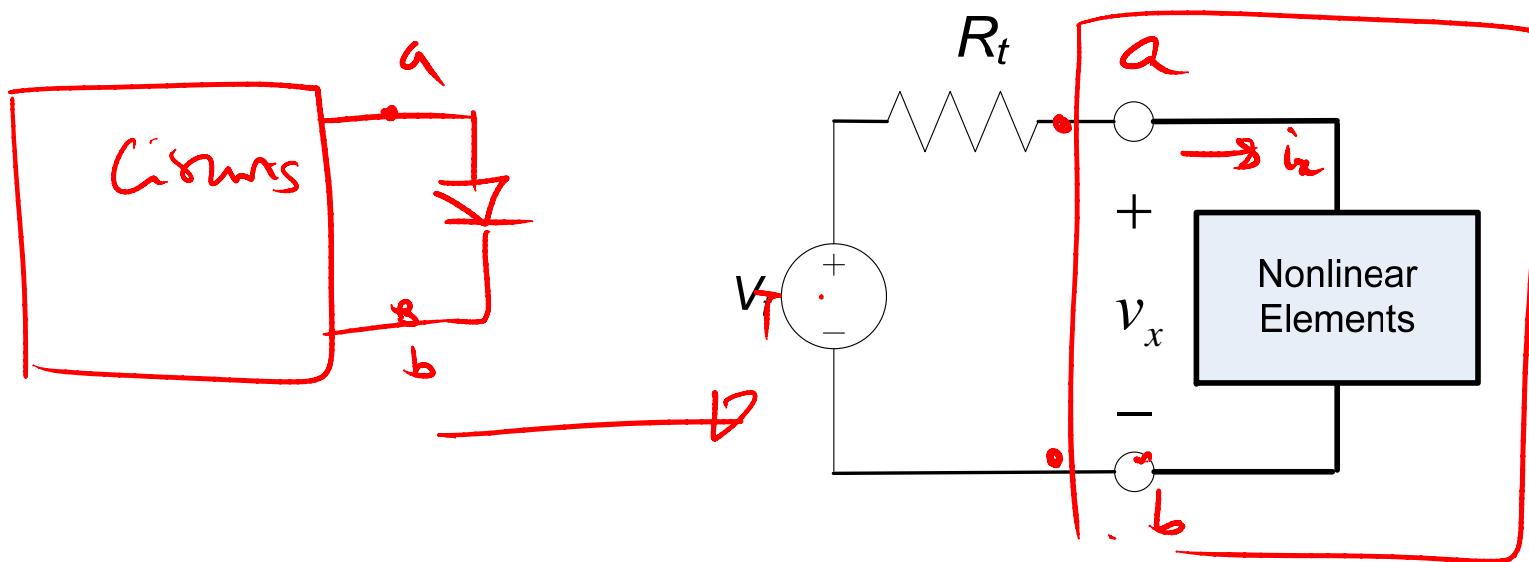
# Solving circuits with one Nonlinear element


- Replace the circuit by its Thevenin's equivalent considering the nonlinear element as the load
- Use graphical analysis technique


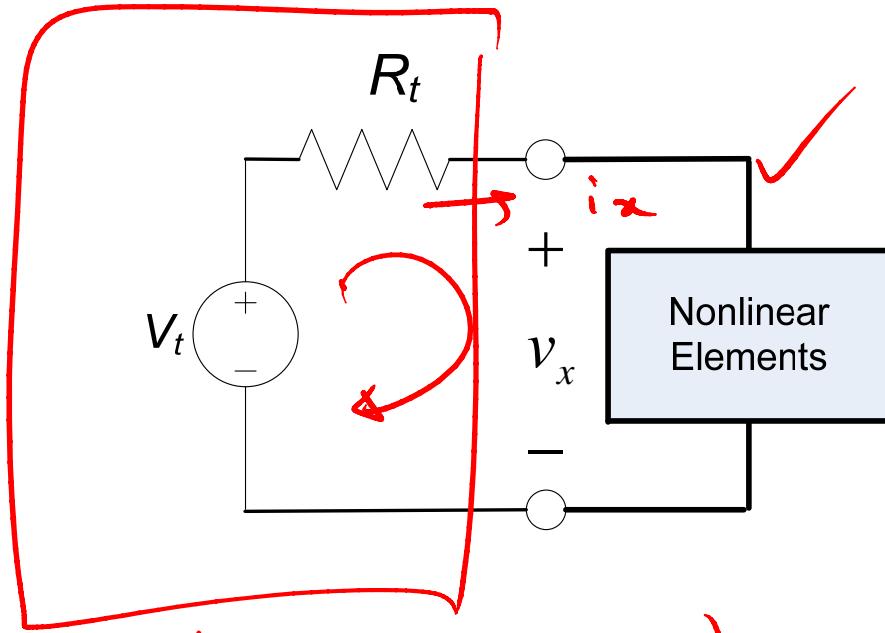
# Treating the nonlinear elements as load



KVL:

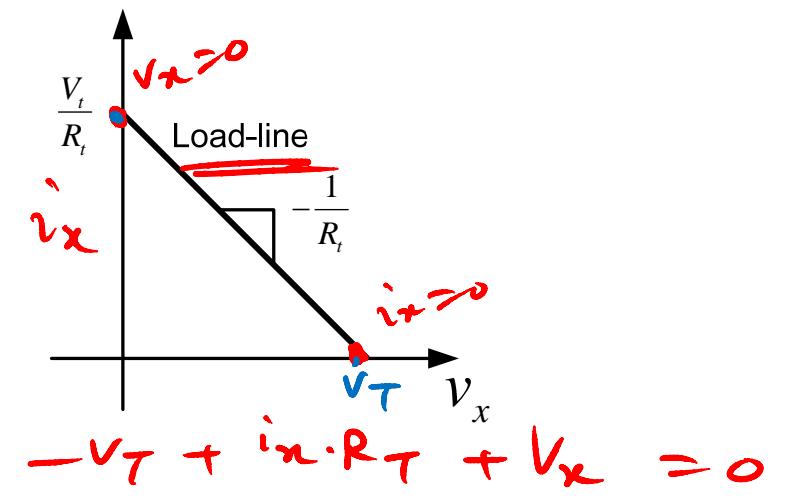



$$v_T = i_x R_T + v_x$$

$$i_x = \left( -\frac{1}{R_T} \right) v_x + \left( \frac{v_T}{R_T} \right)$$

$$y = mx + c$$
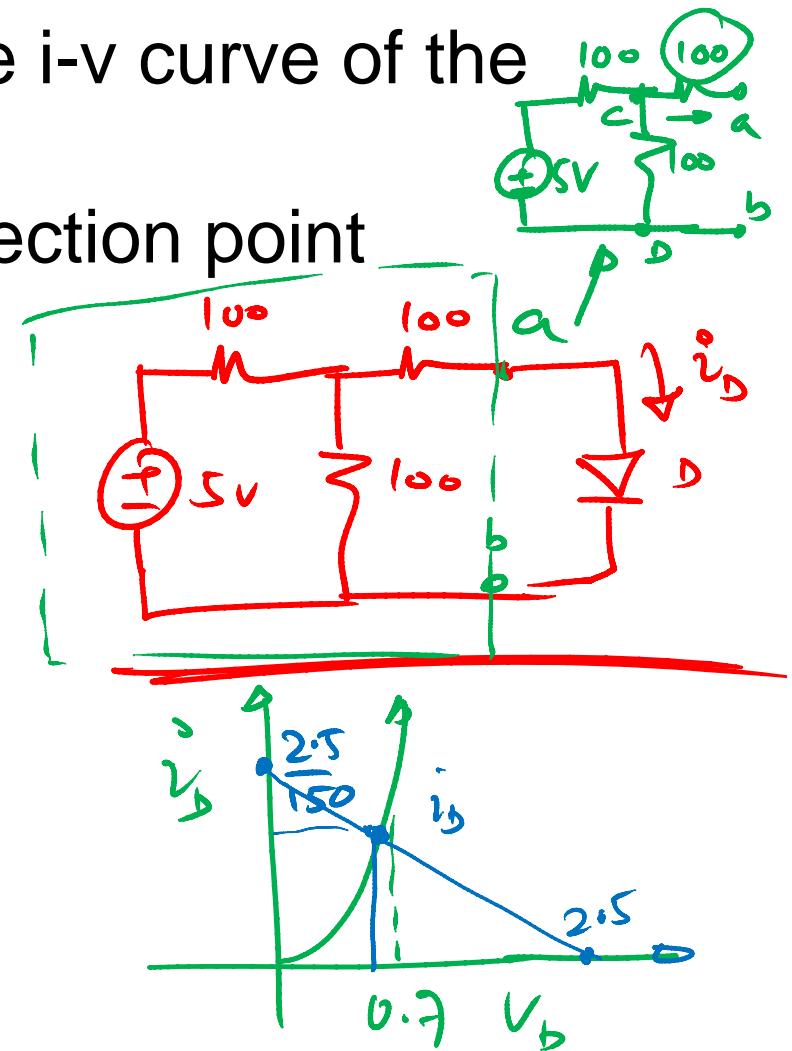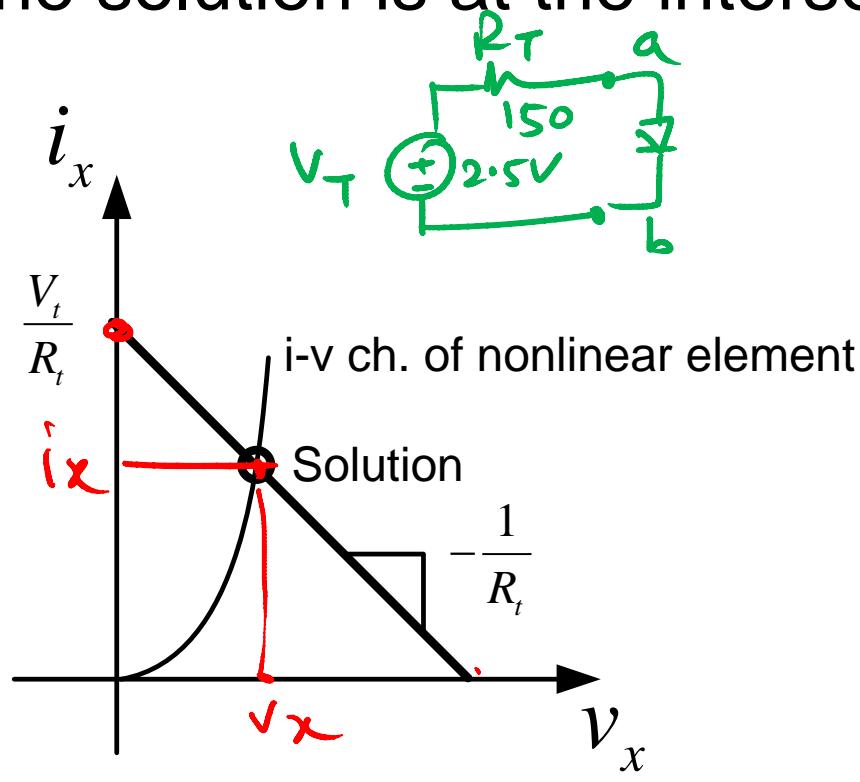
# Graphical (Load-line) analysis



- Merge the load line onto the i-v curve of the nonlinear element
- The solution is at the intersection point



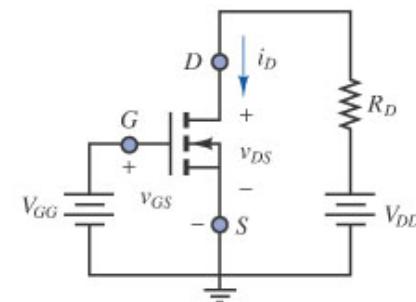
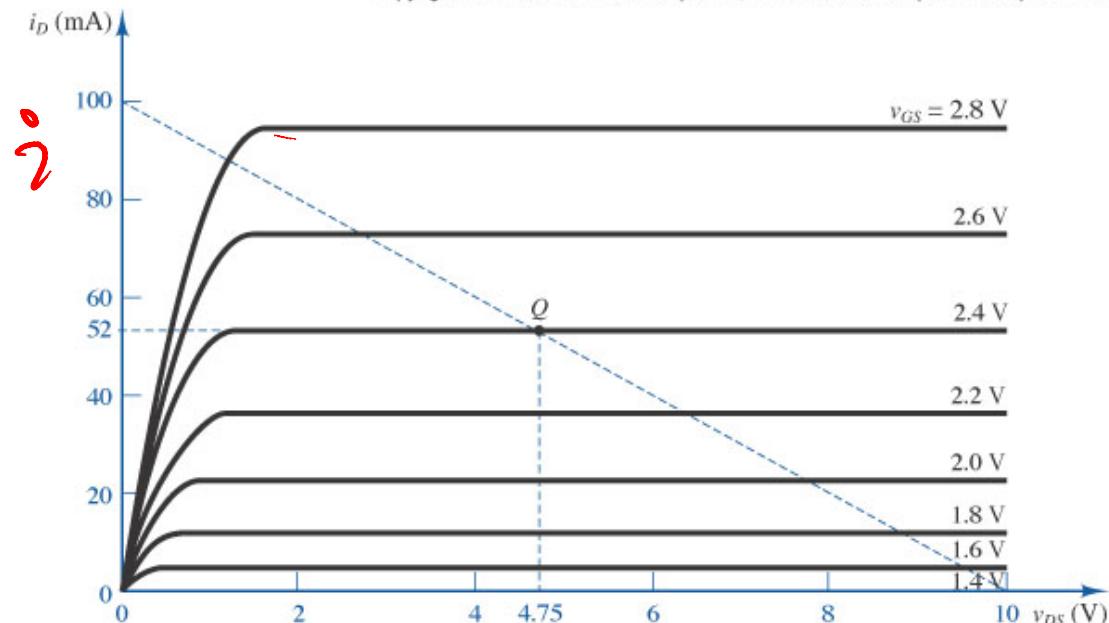
# Practical Example

Transistor

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



# Example 1

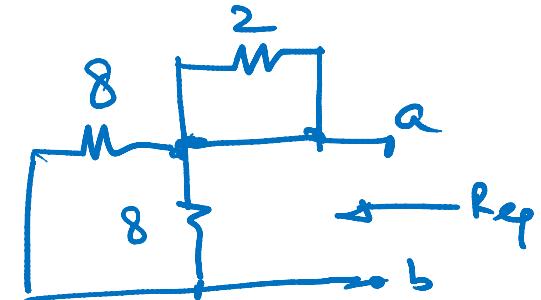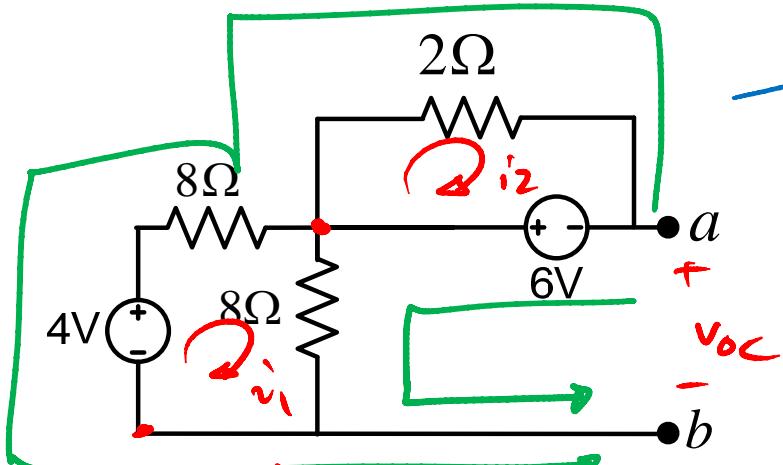

Find the Thevenin's equivalent between nodes 'a' and 'b'.  $R_{eq} = \underline{4\Omega}$


$$\text{Msh } i_1 \text{ & KVL } : -4 + 8i_1 + 8i_1 = 0 \Rightarrow i_1 = 0.25 \text{ A.}$$

$$\text{Men } i_2 \text{ KVL : } 2i_2 - 6 = 0 \Rightarrow i_2 = 3 \text{ A.}$$

$$V_{oc} = V_{ab} = -6 + 8i_1 = -6 + 8 \times 0.25 = -4 \text{ V.} = V_T.$$

$$\begin{aligned} V_{ab} &= -2i_2 - 8i_1 + 4 = -2 \times 3 - 8 \times 0.25 + 4 \\ &= -6 - 2 + 4 = -4 \text{ V.} = V_T. \end{aligned}$$

# Example 2

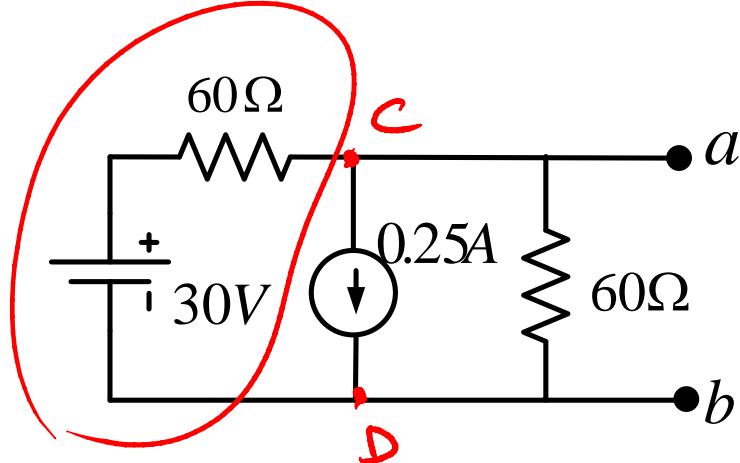

Find the Norton equivalent of the circuit between nodes 'a' and 'b'.

