

# EE1002

# Introduction to Circuits and Systems

## Midterm Test 1 Discussion

You are asked to use Node Voltage Analysis method to solve the circuit below. Identify the node voltage variables and write as many independent equations as the number of unknowns.

DO NOT SOLVE the equations!

$$i = \frac{20 - V_2}{5} \quad \text{--- ①}$$

No. of unknowns =  $i, V_1, V_2, V_3$


KCL at S.N.1.

$$\frac{V_1 - 0}{5} + \frac{V_1 - 20}{5} - 5 = 0 \quad \text{--- ②}$$

KCL at node  $V_2$ .


$$5 + \frac{V_2 - 20}{5} + \frac{V_2 - 0}{5} + \frac{V_2 - V_3}{5} = 0 \quad \text{--- ③}$$
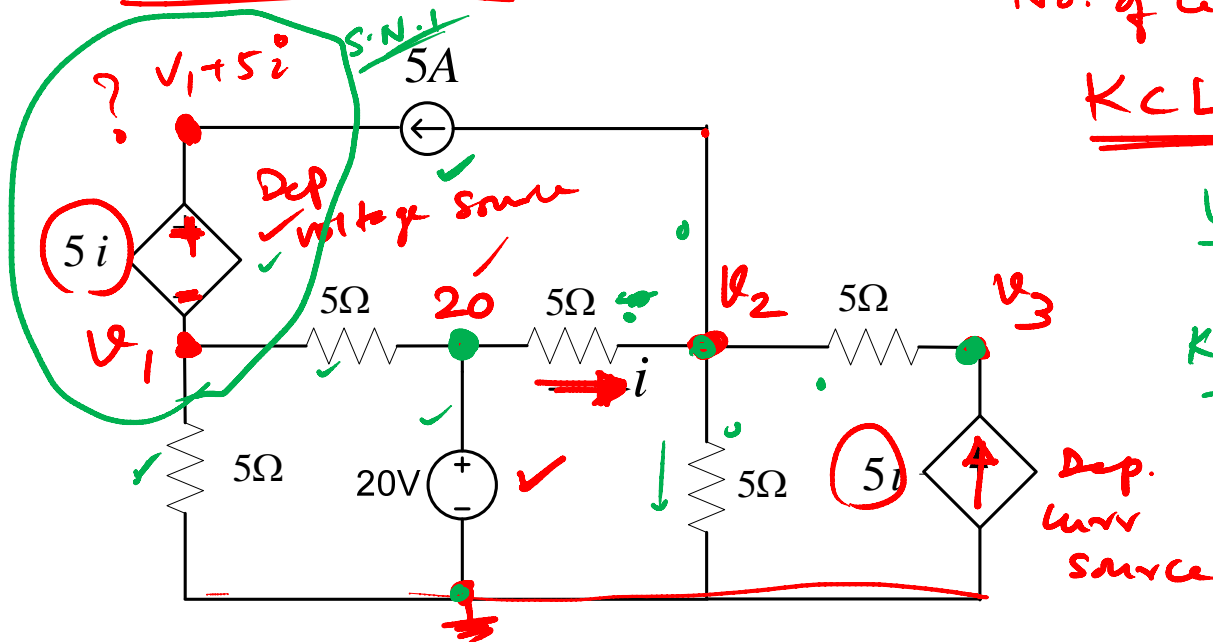
$$\frac{V_3 - V_2}{5} - 5i = 0 \quad \text{--- ④}$$



You are asked to use **Node Voltage Analysis method** to solve the circuit below. **Identify the node voltage variables** and **write as many independent equations** as the number of unknowns.

**DO NOT SOLVE** the equations!

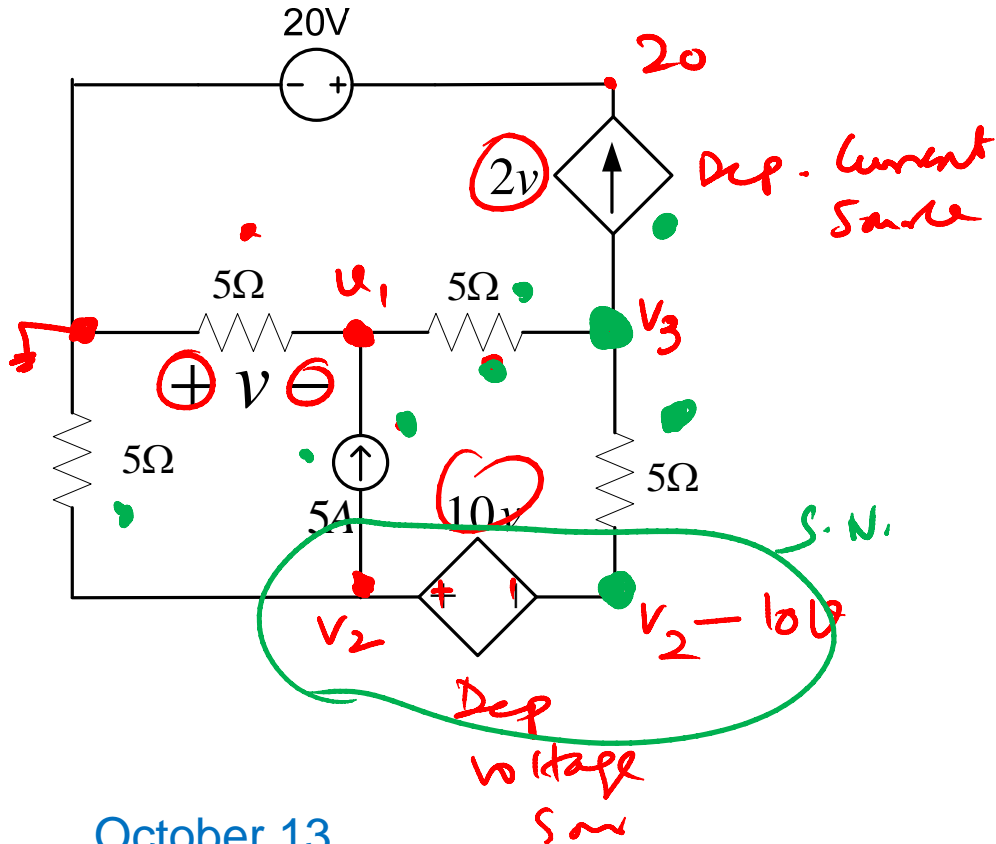

$$v = 0 - v_1 = -v_1 \quad \text{--- ①}$$

KCL at  $v_1$

$$\frac{v_1 - 0}{5} - 5 + \frac{v_1 - v_3}{5} = 0 \quad \text{--- ②}$$

KCL at S.N.

$$\frac{v_2 - 0}{5} + 5 + \frac{v_2 - 10V - v_3}{5} = 0 \quad \text{--- ③}$$


KCL at  $v_3$

$$2v + \frac{v_3 - v_1}{5} + \frac{v_3 - (v_2 - 10V)}{5} = 0 \quad \text{--- ④}$$

You are asked to solve the circuit below using Mesh Current Analysis Method. The three mesh currents are shown as  $I_1$ ,  $I_2$  and  $I_3$ . Write 3 independent equations involving the 3 mesh currents.

Express the current  $i$  in terms of the mesh currents.

**DO NOT SOLVE** the equations!

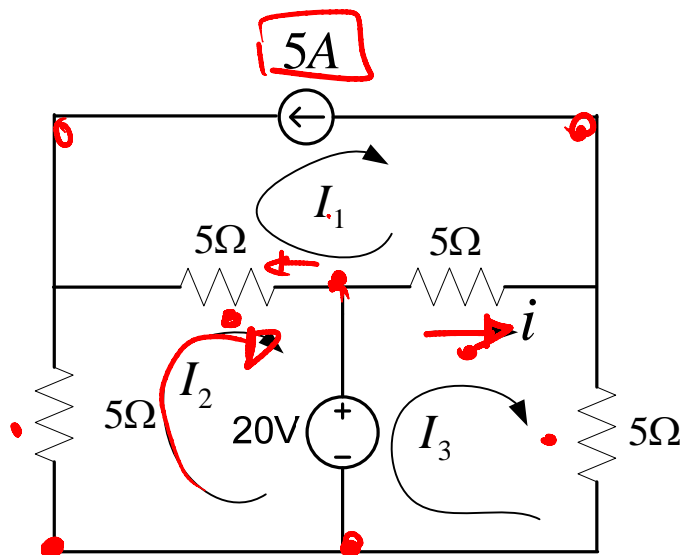

K.V.L. for mesh  $I_1$

$$\cancel{5 \times (I_1 - I_2) - 5} \times$$

$$I_1 = -5 \quad \text{--- (1)}$$

Mesh  $I_2$ :

$$5 \times I_2 + 5 \cdot (I_2 - I_1) + 20 = 0 \quad \text{--- (2)}$$

Mesh  $I_3$ :


$$-20 + 5 \times (I_3 - I_1) + 5 \cdot I_3 = 0 \quad \text{--- (3)}$$

$$i = I_3 - I_1$$

You are asked to solve the circuit below using **Mesh Current Analysis Method**. The three mesh currents are shown as  **$I_1$ ,  $I_2$  and  $I_3$** . Write **three independent equations** involving the 3 mesh currents.

Express the ~~current~~ <sup>voltage</sup>  **$v$**  in terms of the mesh currents.

**DO NOT SOLVE** the equations!

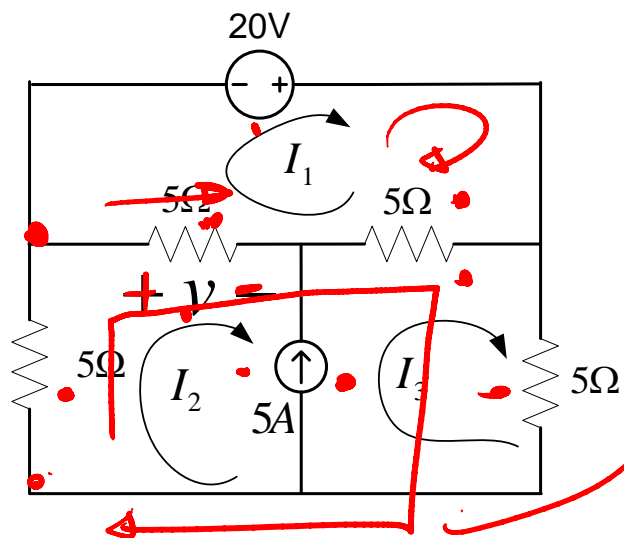

Mesh  $I_1$ :

$$-20 + 5(I_1 - I_3) + 5(I_1 - I_2) = 0 \quad \text{--- ①}$$

Mesh  $I_2$ :  $\times$

Mesh  $I_3$ :  $\times$





KCL:

$$5I_2 + 5(I_2 - I_1) + 5(I_3 - I_1) + 5I_3 = 0 \quad \text{--- ②}$$

$$I_3 - I_2 = 5 \quad \text{--- ③}$$

$$5(I_2 - I_1) = v =$$

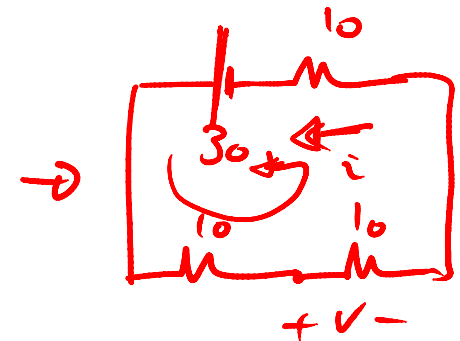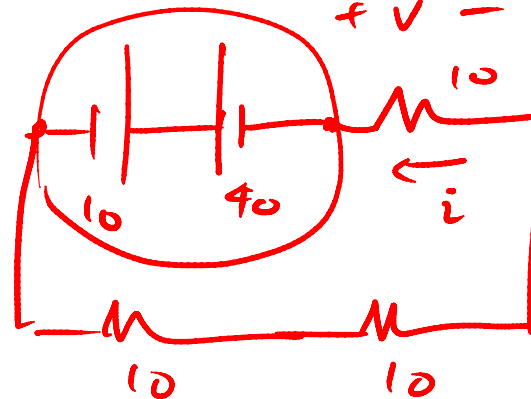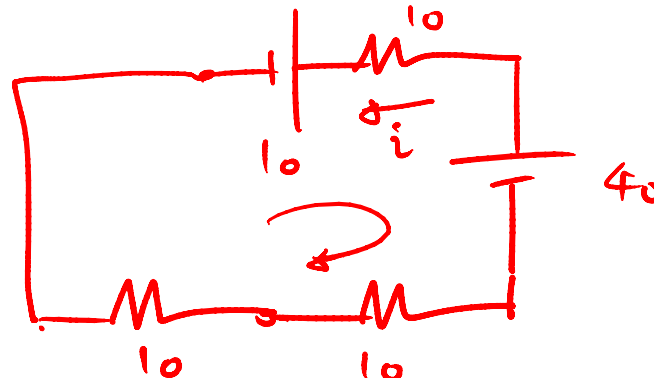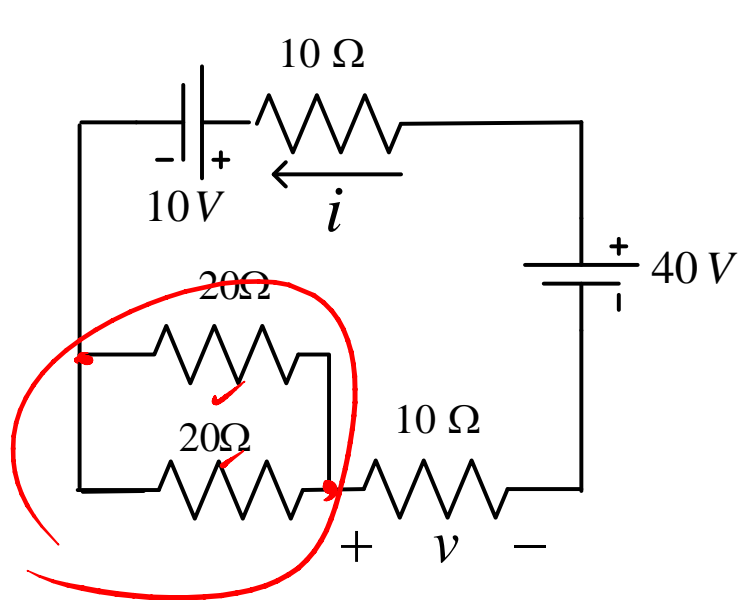For the circuit below, find the **voltage** and **current** .





Voltage divider

$$\text{rule} \Rightarrow v = \frac{10}{10+10+10} \times 30 = 10V$$

$$i = \frac{30}{10+10+10} = 1A$$

$$V = 10 \times 1 = 10V$$

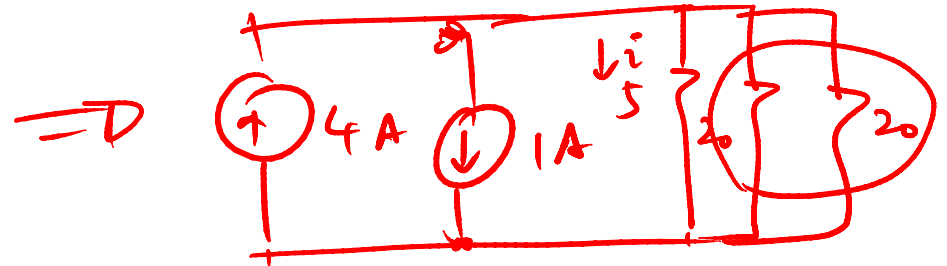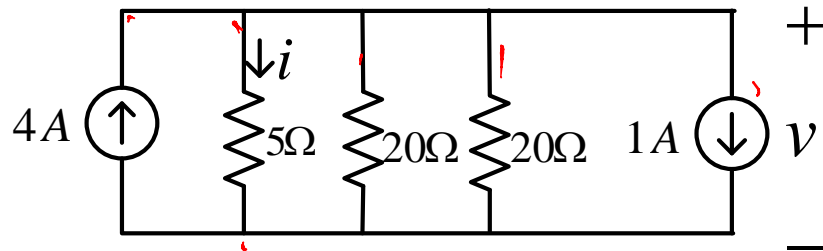
For the circuit below, find the **current  $i$**  and **voltage  $v$** .




Current divider rule.

$$i = 3 \times \frac{10}{10 + 5} = 2 \text{ A}$$
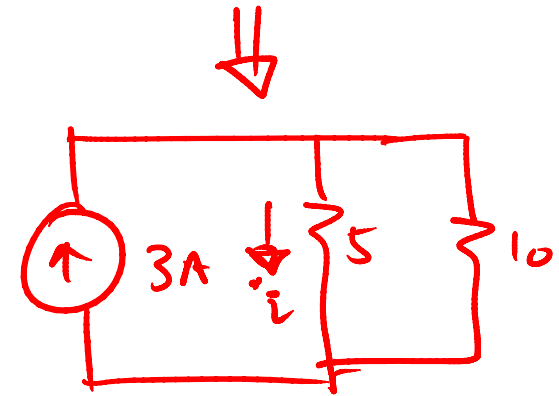
$$V = i \times R = 2 \times 5 = 10 \text{ V}$$



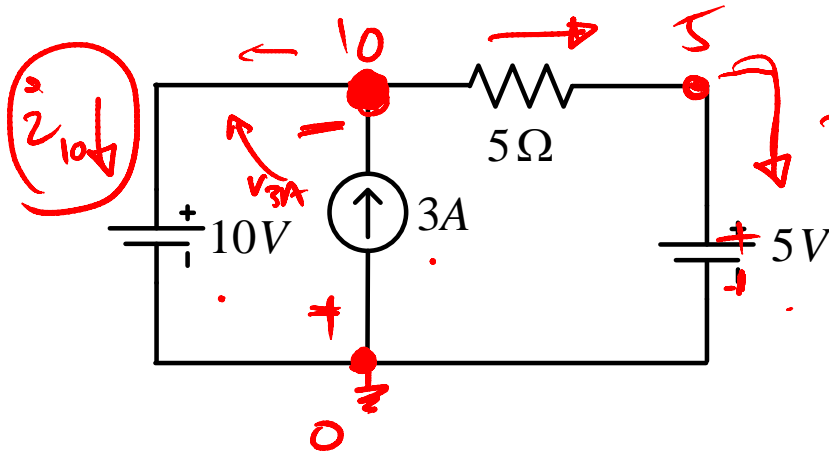Find the power associated with all the 3 sources in the circuit below.  
Mention if they are **absorbing** or **delivering** power.




$$\underline{i_{10v} = 1 \text{ A}}$$

$$i_{5v} = \frac{10 - 5}{5} = 1 \text{ A}$$

KCL at node 10v:

$$i_{10} - 3 + i_{5v} = 0$$
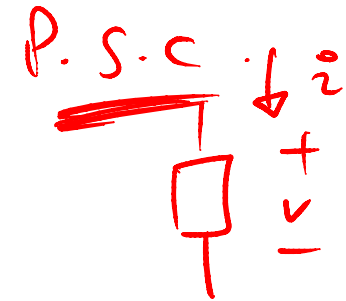
$$i_{10} = 3 - i_{5v} = 3 - 2 = 1 \text{ A}$$



$$P = v \cdot i$$

fre  $\rightarrow$  abs.

-ve  $\rightarrow$  del.


$$P_{10v} = 10 \times i_{10v} = 10 \times 2 = 20 \text{ W (abs)}$$

$$P_{3A} = V_{3A} \times 3 = (0 - 10) \times 3 = -30 \text{ W (del)}$$

$$P_{5v} = 5 \times i_{5v} = 5 \times 2 = 10 \text{ W (abs)}$$



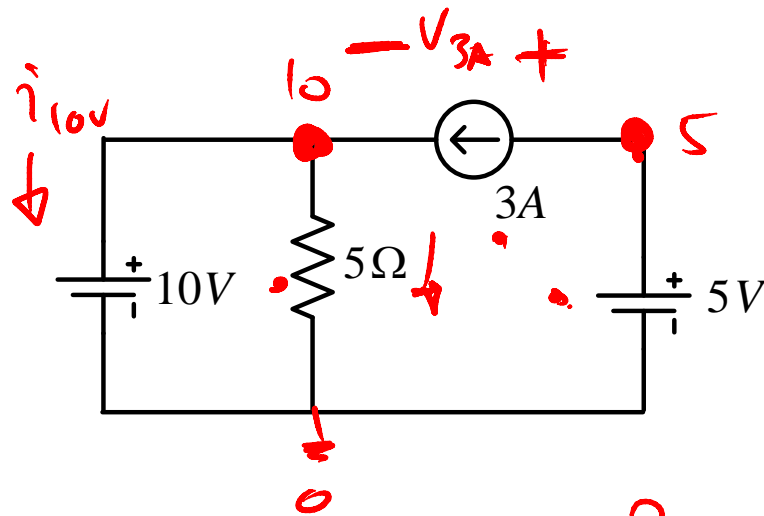Find the **power associated with all the 3 sources** in the circuit below.  
Mention if they are **absorbing or delivering power**.



$$i_{10V} + \frac{10}{5} - 3 = 0$$

$$i_{10V} = 1 \text{ A}$$

$$i_{5V} = -3 \text{ A}$$


$$V_{3A} = 5 - 10 = -5 \text{ V}$$

$$P_{10V} = 10 \times i_{10V} = 10 \times 1 = 10 \text{ W (abs)}$$

$$P_{3A} = V_{3A} \times 3 = -5 \times 3 = -15 \text{ W (del)}$$

$$P_{5V} = 5 \times i_{5V} = 5 \times (-3) = -15 \text{ W (del)}$$

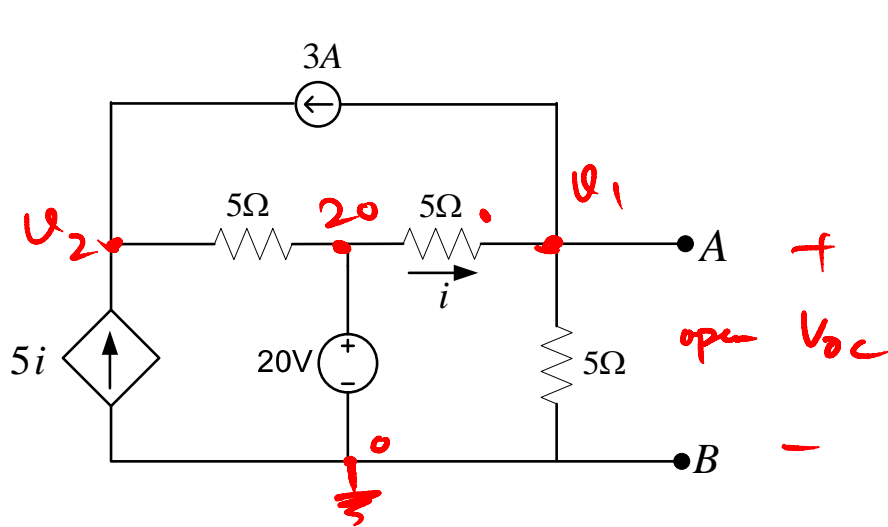For the circuit below, find the Norton's equivalent between nodes A and B.




$V_{oc}$ ,  $I_{sc}$ .  
KCL at  $V_1$ :  $V_{oc} = V_1$   

$$V_1 - \frac{20}{5} + 3 + \frac{V_1}{5} = 0 \quad \text{--- (1)}$$

$$V_1 - 20 + 15 + V_1 = 0$$
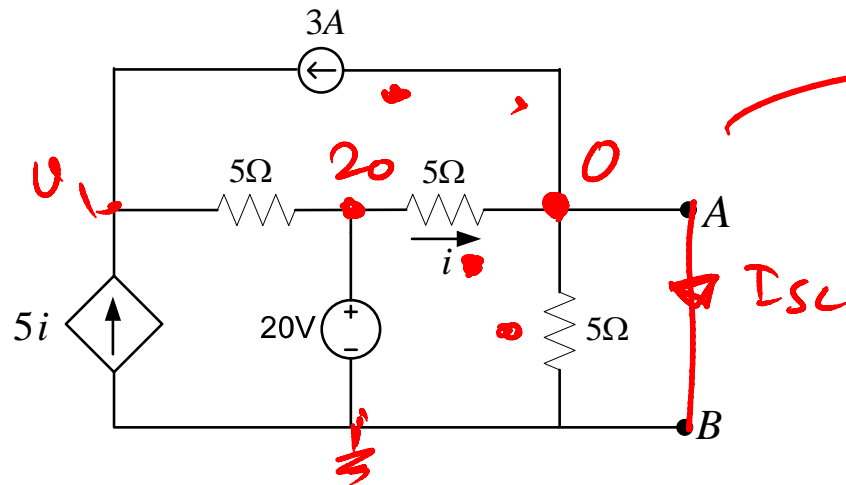
$$2V_1 = 5 \Rightarrow V_1 = 2.5V.$$
 $= V_{oc}$




KCL:  

$$+3 + \frac{0-20}{5} + \frac{0}{5} + I_{sc} = 0$$

$$+3 - 4 + I_{sc} = 0$$
 $I_{sc} = 1A$

$R_{TH} =$

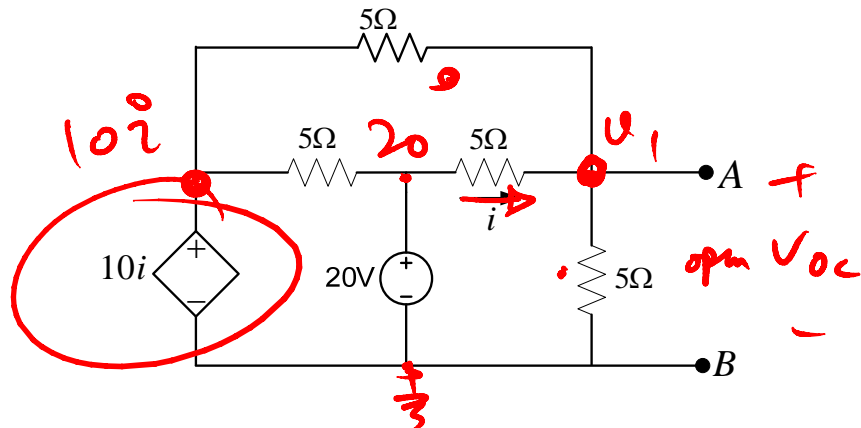For the circuit given below, find the **Thevenin's equivalent** circuit between nodes A and B.




$$i = \frac{20 - V_1}{5} \Rightarrow 10i = 2(20 - V_1) = 40 - 2V_1$$

KCL at  $V_1$ :

$$\frac{V_1 - (40 - 2V_1)}{5} + \frac{V_1 - 20}{5} + \frac{V_1}{5} = 0$$

$$V_1 - 40 + 2V_1 + V_1 - 20 + V_1 = 0$$
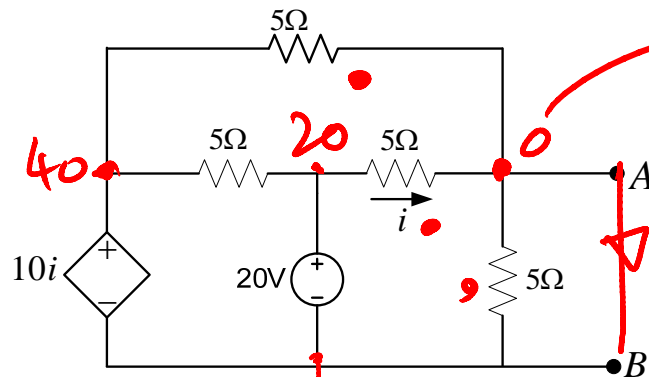
$$5V_1 = 60 \Rightarrow V_1 = 12 = V_{oc}$$



$$i = \frac{20 - 0}{5} = 4 \text{ A}$$

$$10i = 40$$

KCL:

$$\frac{0 - 40}{5} + \frac{0 - 20}{5} + 0 + I_{sc} = 0$$

$$-8 - 4 + I_{sc} = 0 \Rightarrow I_{sc} = 12 \text{ A}$$

$$R_{TH} = \frac{V_{oc}}{I_{sc}} = 1 \Omega$$

