

NATIONAL UNIVERSITY OF SINGAPORE

EXAMINATION FOR

(Semester I: 2011/2012)

EE1002 – INTRODUCTION TO CIRCUITS AND SYSTEMS

November/December 2011 - Time Allowed: 2.0 Hours

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **FOUR** (4) questions and comprises **FIVE** (5) printed pages.
2. Answer all **FOUR** (4) questions.
3. Different questions carry different marks.
4. This is a CLOSED BOOK examination but students are provided with a “Formula Sheet” that they can refer to during the course of the examination.

- Q.1(a). The circuit in Figure Q.1(a) contains one independent voltage source, one dependent voltage source and one dependent current source, where the value of voltage drop across the $1\ \Omega$ resistor is v_o .

Determine the power supplied by the 10V independent voltage source.

(10 marks)

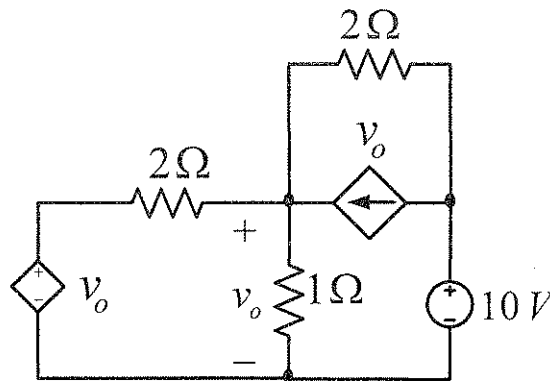


Figure Q.1(a)

- (b) In the circuit given in Figure Q.1(b), find the Thevenin's equivalent of the circuit between points A and B.

(10 marks)

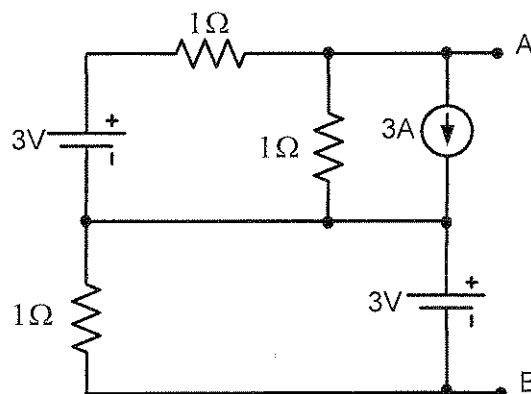


Figure Q.1(b)

Q.2(a) For the circuit given in Figure Q.2(a), switch S1 was closed and S2 was open for a long time before $t = 0$. At $t = 0$, the switch S1 is opened and S2 is closed.

- (i) Find the energy stored in the inductor before $t = 0$.
(5 marks)
- (ii) Find the energy stored in the capacitor immediately after $t = 0$.
(5 marks)
- (iii) Find the expression for the inductor current as a function of time after $t = 0$.
(5 marks)
- (iv) Find the expression for the capacitor voltage as a function of time after $t = 0$.
(5 marks)


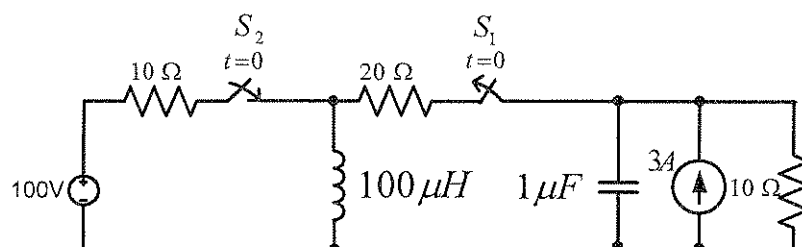


Figure Q.2(a)

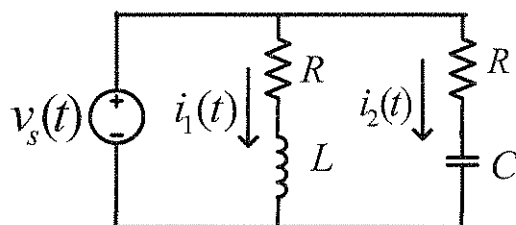(b) In the circuit given in Figure Q.2(b),



$$v_s(t) = 100 \cos\left(2000t + \frac{\pi}{12}\right)$$

$$R = 10\Omega$$

$$L = 5mH$$

$$C = 50\mu F$$

Figure Q.2(b)

- (i) Find the expressions for currents $i_1(t)$ and $i_2(t)$.
(6 marks)
- (ii) Specify the RMS values for the currents $i_1(t)$ and $i_2(t)$ and the phase difference between them.
(4 marks)

- Q.3 (a) A magnetic circuit shown in Fig. Q.3(a) has an iron core with infinite permeability. The core cross sectional area, A_c is 16 cm^2 , the air-gap length, g is 2 mm and the mean length of the magnetic flux-path, l_c is 80 cm.

The coil has 500 turns and draws a dc current of 4 A from the source. You can neglect the magnetic flux leakage and fringing effect.

Determine

- (i) the flux in the magnetic circuit,
- (ii) the flux-linkage of the coil and
- (iii) the inductance of the coil.

(10 marks)

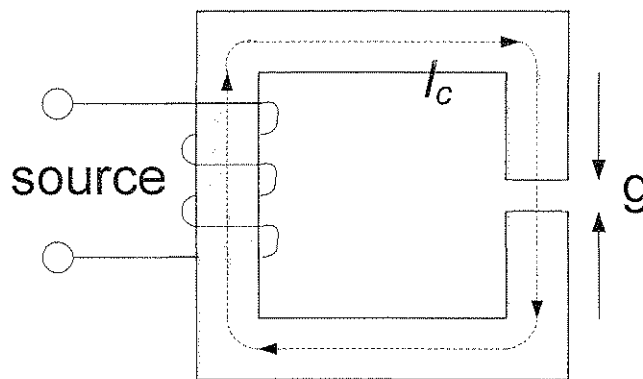


Figure Q.3(a)

- (b) A 2400/240 V, 150 kVA, and 50 Hz single-phase transformer has an equivalent circuit series impedance of $Z_{eq} = 0.5 + j 1.5 \Omega$ referring to the high-voltage side. The magnetizing impedance is large and can be ignored. The transformer is supplying the rated load at 240 V and 0.85 power factor lagging.

Determine

- (i) the voltage regulation in percentage and
- (ii) the efficiency of the transformer while supplying the above mentioned load.

(15 marks)

- Q.4(a) A linear DC machine has a constant flux-density of 0.5 Wb/m^2 directed into the page of the paper, a resistance of 0.25Ω , a conductor bar of length 0.5 m , and a battery source of 120 V as shown in Figure Q.4(a).

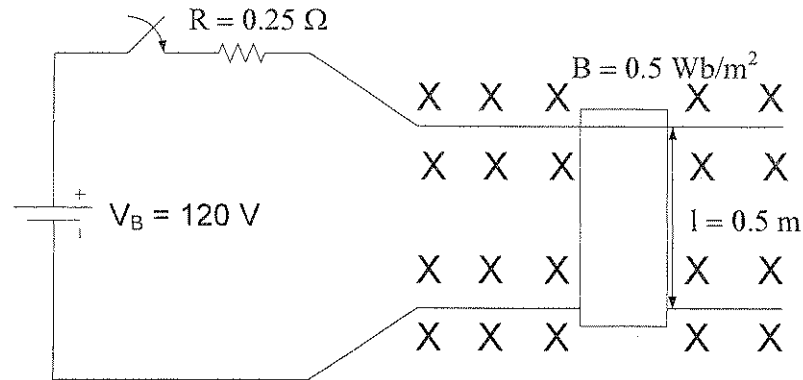


Figure Q.4(a)

- (i) Initially assume that no load is applied on the bar, determine the corresponding no-load steady-state speed of the bar. (3 marks)
- (ii) If a load of 20 N is now applied on the bar in a direction opposite to the direction of motion, determine the corresponding new steady-state speed of the bar. (5 marks)
- (iii) If the supply voltage is now reduced to 100 V while keeping the flux-density at its original value, determine the corresponding new steady-state speed of the bar.

What conclusion can you draw from the observation in part (iii)?

(5 marks)

- (b) A permanent magnet DC motor is directly and rigidly coupled to a load whose characteristic is given by

$$T_L = 5 + 0.05\omega + 0.001\omega^2$$

where T_L is in N.m , and ω is in rad/sec .

The motor has a back-emf constant of 2.42 V/(rad/s) , the armature resistance is 0.2Ω and the armature inductance is very small and can be neglected. The motor is supplied with a DC voltage of 50 V .

Determine the corresponding steady-state speed(s) of the motor.

(12 marks)

END OF PAPER