

CG1108 past year papers

Note Title

4/12/2014

Q.1 (a) Use **Mesh Current Analysis** method to find voltage V_{AB} in Fig. Q.1.a.

AY 12/13

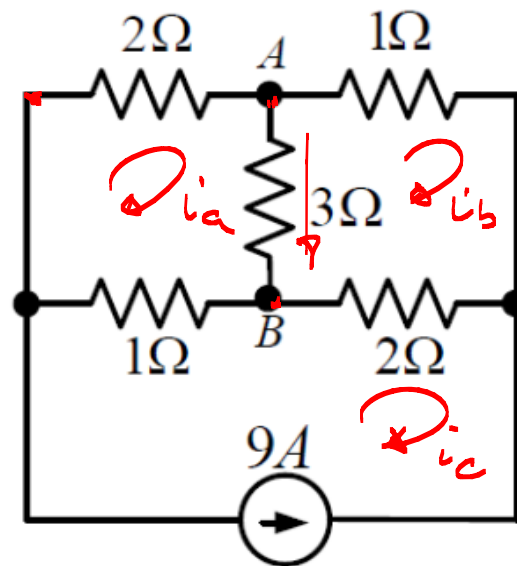


Fig. Q.1.a

(10 marks)

$$\underline{i_c = -9 \text{ A}} \quad \checkmark$$

$$2i_a + 3(i_a - i_b) + i_a = 0 \quad \text{--- (1)}$$

$$i_b + 2(i_b - i_c) + 3(i_b - i_a) = 0 \quad \text{--- (2)}$$

Find i_a, i_b, i_c .

$$V_{AB} = 3 \times (i_a - i_b)$$

Ans.

Q.1 (a) Determine i_1 , i_2 , and i_3 in Fig. Q.1.a.

AY 11/12

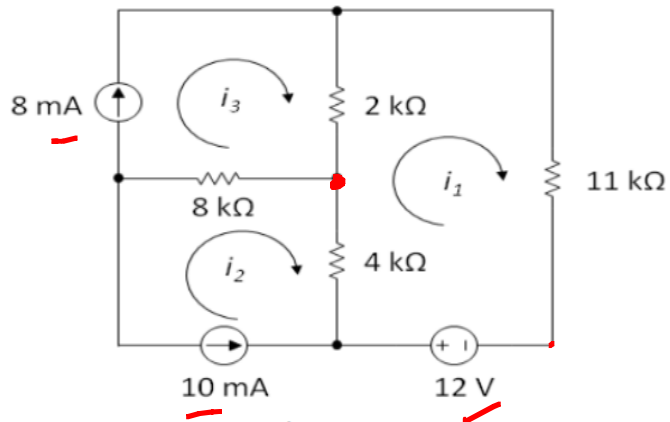


Fig. Q.1.a

(10 marks)

$$i_3 = 8 \text{ mA}$$

$$i_2 = -10 \text{ mA}$$

$$2000 \times (i_1 - i_3) + 11000 \times i_1 - 12 + 4000 (i_1 - i_2) = 0$$

$$\Rightarrow i_1$$

Q1 (b) Use Node Voltage Analysis to find the current (i) drawn from the battery in circuit given in Fig. Q.1.b.

How much power is delivered (or absorbed) by the current source?

KCL at 'x' : $-i + \frac{15}{\frac{1}{2}} + \frac{15-V}{\frac{1}{4}} = 0 \Rightarrow i$

(10 marks)

KCL at node v:

$$\frac{V-15}{\frac{1}{4}} + 3 + \frac{V}{\frac{1}{2}} = 0$$

$$\Rightarrow V:$$

$$\text{Power}_{3A} = \underline{V \times 3}$$

+ve \rightarrow abs. by the source

-ve \rightarrow del.

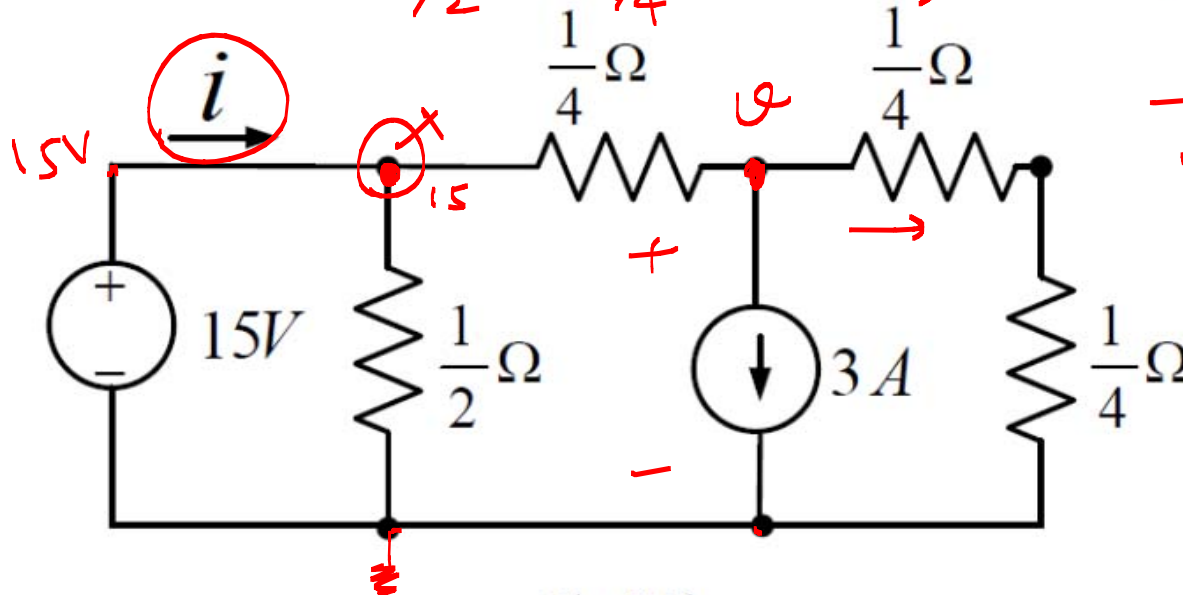


Fig. Q.1.b

AY 12/13

$\downarrow i$
+
V
-
P.S.C.

Q1. (b) Solve for the voltages at Node 1 and Node 2, as shown in Fig. Q.1.b.
 K 11/12

(10 marks)


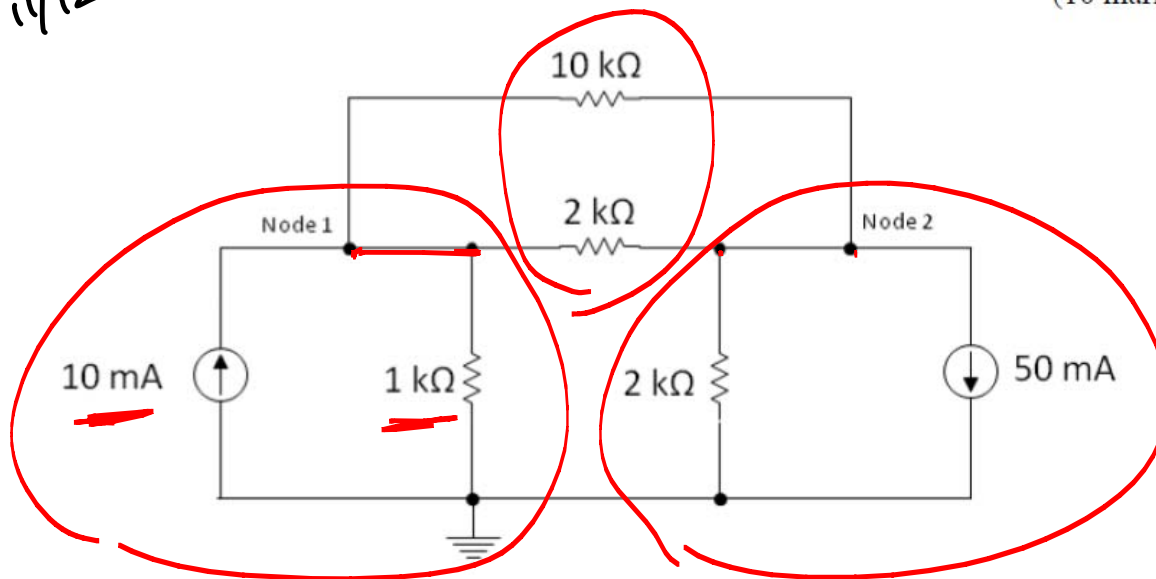
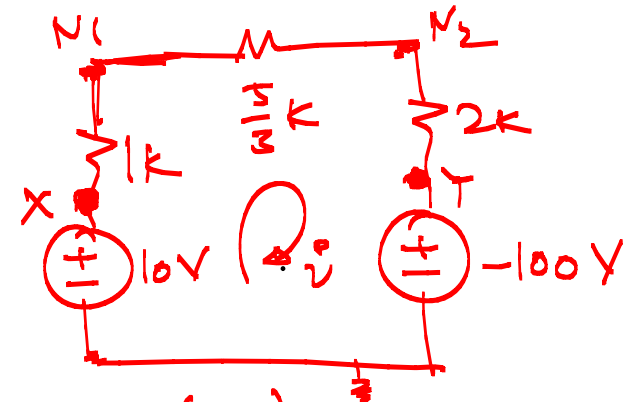


Fig. Q.1.b

$$10k \parallel 2k = \frac{10 \times 2}{12} = \frac{5}{3} k$$

$$V_{N1} = 10 - 1000 \times 23.57 \times 10^{-3} = ?, \quad V_{N2} = -100 + 2000 \times 23.57 \times 10^{-3} V.$$

Source Conversion

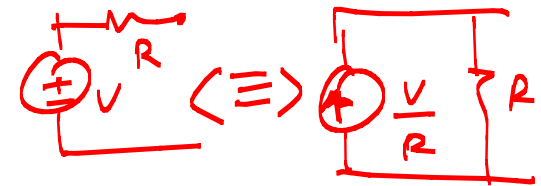

$$\frac{10 - (-100)}{1k + \frac{5}{3}k + 2k} = \frac{110}{\frac{14}{3}k} = 23.57 \text{ mA}$$

Q1. (c) In circuit shown in Fig. Q.1.c, find the output voltage v_o using Superposition principle.

AY 12/13

(10 marks)


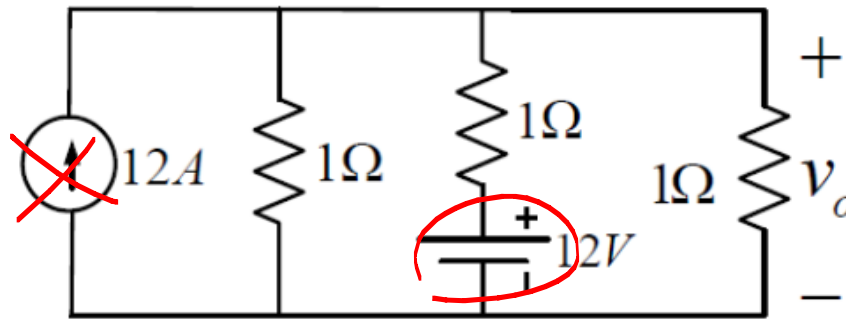


Fig. Q.1.c



①

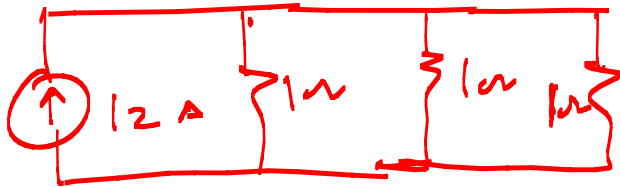Keep the current source
kill the voltage source



$$v_{o1} = 12 \times \frac{1}{3} = 4V$$

②

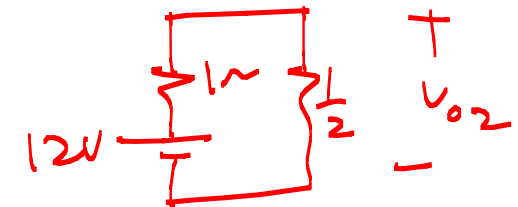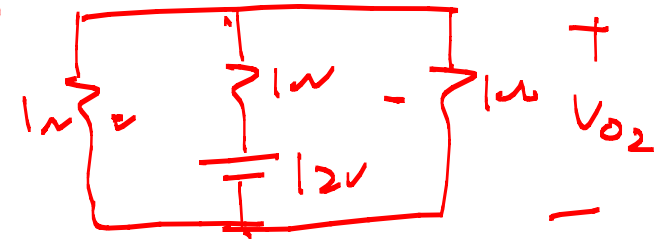


$$v_{o2} = 12 \times \frac{1}{1+1} = 4V$$

$$v_o = v_{o1} + v_{o2} = 8V$$

- Q.2 (a) The Wheatstone bridge circuit, as shown in Fig. Q.2.a, is a resistive circuit that is commonly used in measurement circuits. R_1 , R_2 , and R_3 are equivalent to $1\text{ k}\Omega$. Determine the unknown resistance R_x when V_{ab} is 10 mV .

(15 marks)

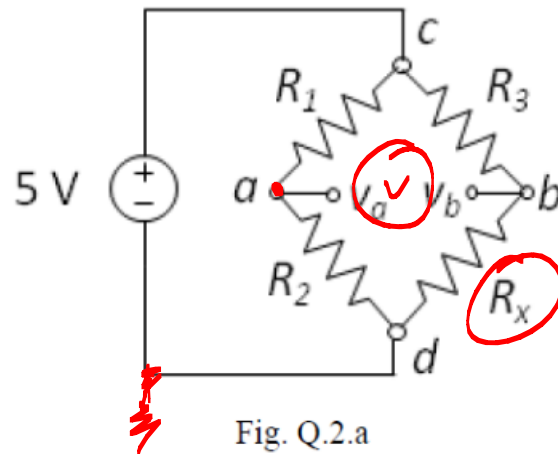

$$V_{ab} = V_a - V_b$$

$$= 5 \times \left[\frac{R_2}{R_1 + R_2} - \frac{R_x}{R_3 + R_x} \right]$$


$$10 \times 10^{-3} = 5 \times \left[\frac{1\text{k}}{1\text{k} + 1\text{k}} - \frac{R_x}{R_x + 1\text{k}} \right]$$

$$\Rightarrow R_x =$$

Q2 (b) Determine the Thevenin's equivalent for the circuit in Fig. Q.2.b.

AT 11/12

(15 marks)

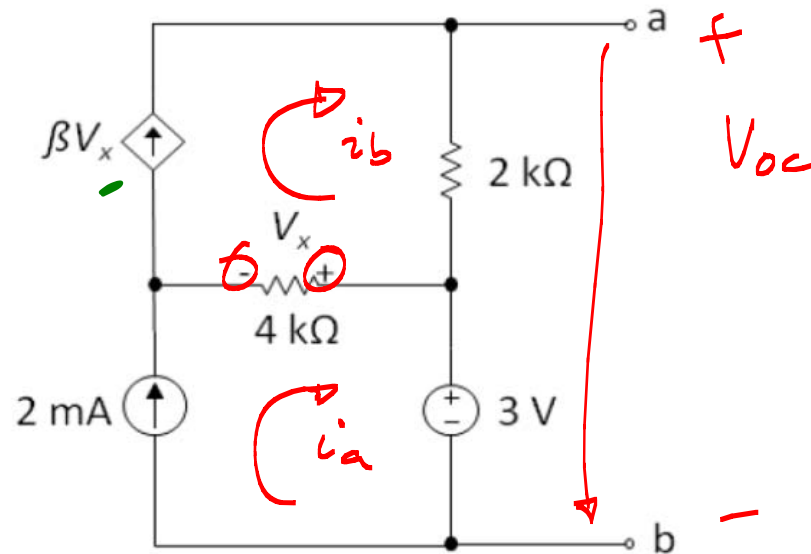

$$\beta = 1/2000$$

Fig. Q.2.b

$$R_{TH} = \frac{V_{OC}}{I_{SC}}$$

Handwritten red diagram showing the Thevenin equivalent circuit with a voltage source $V_{TH} = V_{OC}$ and a resistor R_{TH} in series with terminals a and b.

$$i_a = 2 \text{ mA}$$

$$i_b = \beta V_x = \beta \times 4000 \times (i_b - i_a)$$


$$= \frac{1}{2000} \times 4000 \times (i_b - 2 \text{ mA})$$

$$i_b = 2i_b - 4 \text{ mA}$$

$$\Rightarrow i_b = 4 \text{ mA}$$

$$V_{OC} = 2000 \times i_b + 3$$
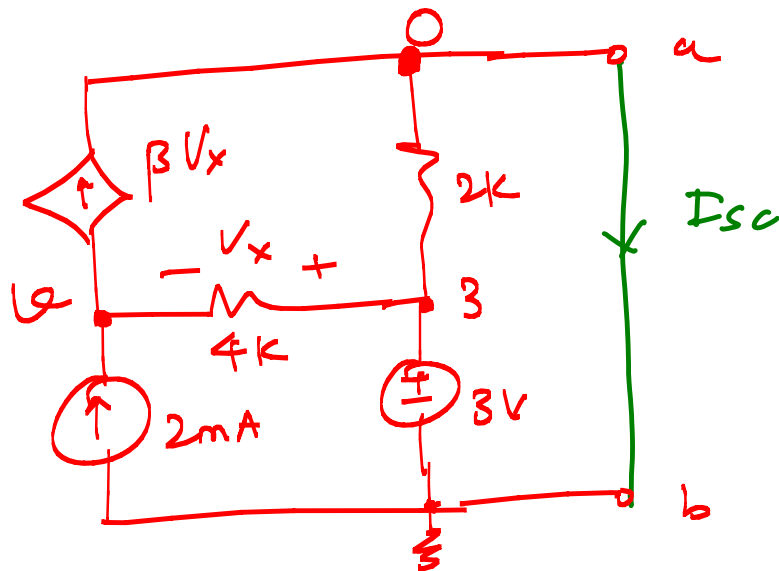
$$= 2000 \times 4 \times 10^{-3} + 3 = 11 \text{ V}$$



Node voltage analysis

KCL at 3 :

$$\beta \cdot V_x + \frac{V-3}{4000} - 2\text{mA} = 0$$

$$V_x = (3-V)$$

$$\frac{1}{2000} (3-V) + \frac{V-3}{4000} - 2 \times 10^{-3} = 0$$

$\times 4000$:

$$2(3-V) + V-3 - 2 \times 4 = 0$$

$$6 - 2V + V - 3 - 8 = 0 \Rightarrow V = 6 - 3 - 8 = -5\text{V}$$

$$\text{KCL at 'a': } -\beta \cdot V_x + \frac{0-3}{2000} + I_{sc} = 0$$

$$-\beta(3-V) + \frac{0-3}{2000} + I_{sc} = 0 \Rightarrow I_{sc}$$

- Q1. (d) In circuit shown in Fig. Q.1.d, find the **Norton's equivalent** between a and b . Find the **maximum power** that can be drawn from the circuit by the load resistance, R_L .

At 12/13

(10 marks)


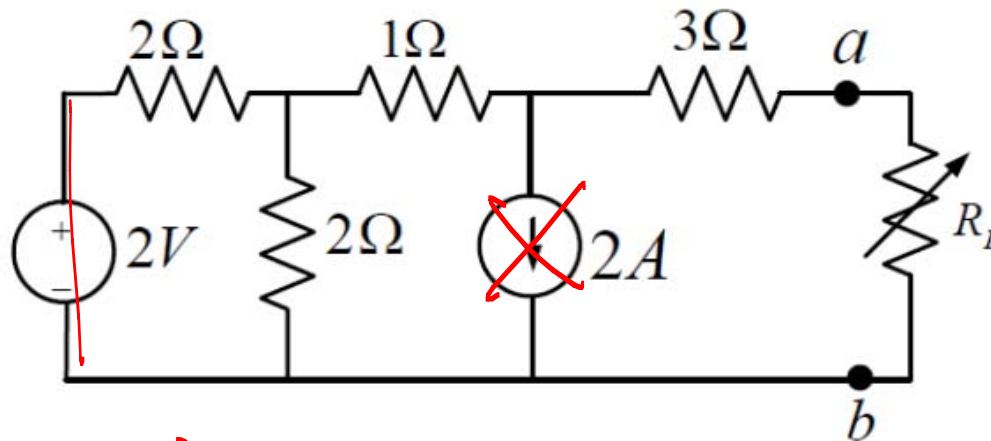
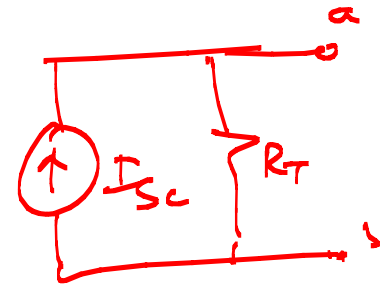


Fig. Q.1.d

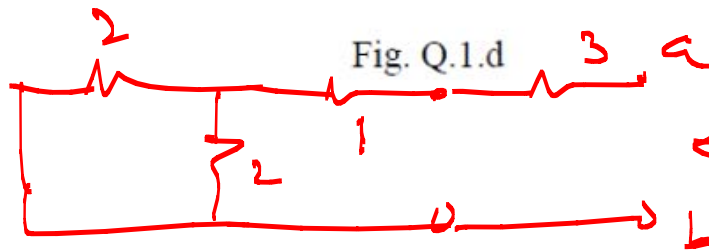

R_T can be obtained
by killing the ind.
sources

$$\leftarrow R_T = 3 + 1 + \frac{2}{2} = 5\Omega$$

Q.1.
AY 12/13

(e) In circuit shown in Fig. Q.1.e, the current source is AC sinusoidal $i_s(t) = 10 \cos 2t$ A.

Find the power dissipated by the resistor.

$\rightarrow P_R = I_{RMS}^2 \times R$ $\Rightarrow I_s = 10 \angle 0^\circ$
(10 marks)

$\omega = 2 \text{ rad/sec}$


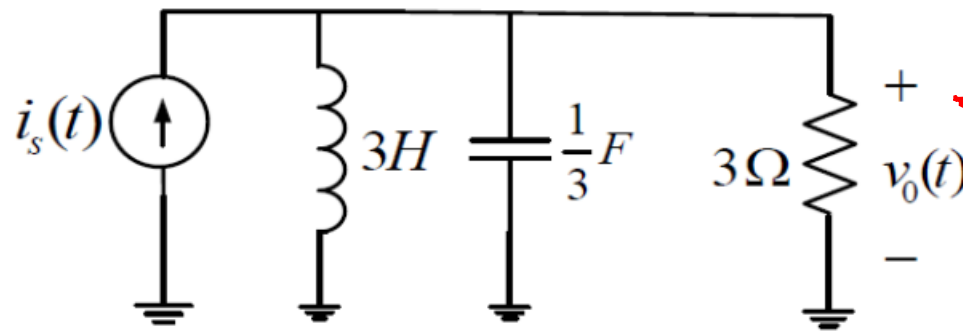


Fig. Q.1.e

Handwritten calculations for the equivalent circuit:
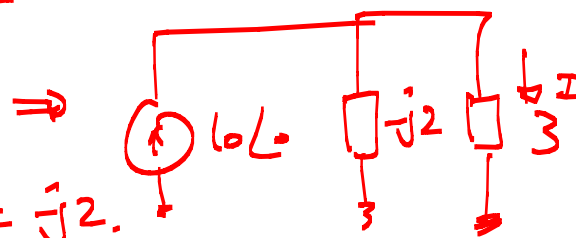
$$\frac{-j \cdot 9}{+9/2} = \frac{j6 \times (-j3/2)}{j(6 - 3/2)} = j2$$



$R = 3 \rightarrow Z_R = 3$

$I = 10 \angle 0^\circ \times \frac{-j2}{3 - j2}$

$L = 3H \rightarrow Z_L = j\omega L = j \times 2 \times 3 = j6$


$C = \frac{1}{3} F \rightarrow Z_C = -j \frac{1}{\omega C} = -j \frac{1}{2 \times \frac{1}{3}} = -j \frac{3}{2}$

$$I_{rms} = \frac{I_3}{\sqrt{2}} = \frac{5.55}{\sqrt{2}} \quad I = 5.55 \angle -56.31^\circ$$

$$P_R = I_{rms}^2 \times R = \left(\frac{5.55}{\sqrt{2}} \right)^2 \times 3 = 46.2 \text{ W.}$$

Q.2 The circuit in Figure Q.2 is that of a burglar alarm. The alarm itself is modeled by a $1k\Omega$ resistor. The alarm will not sound until the current in it exceeds $100\mu A$. Find the delay between switch being closed and the alarm sounding. Assume the capacitor to be initially discharged.

Apr 12/13

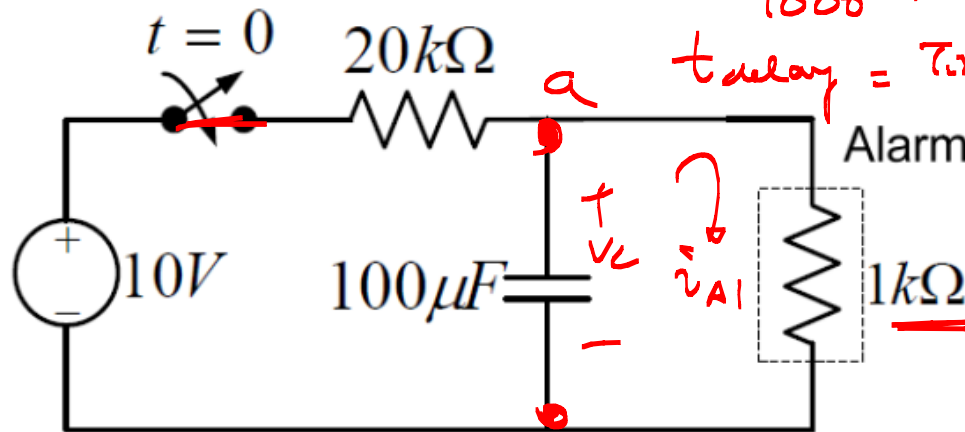

$$i_{AL} = \frac{v_C}{1000}$$


(15 marks)

$$t_{\text{delay}} = \text{Time for } v_C \text{ to reach } = 1000 \times (100 \times 10^{-6}) = 0.1 \text{ V}$$


$$\tau = R_{TH} \times C = \frac{20}{21} \times 10^3 \times 100 \times 10^{-6}$$

$$= \frac{2}{21} \text{ s}$$
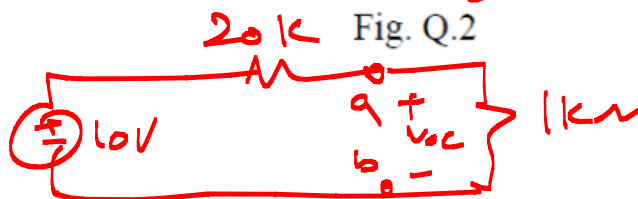
$$v_C(t) = v_C(0) \cdot e^{-t/\tau} + v_{TH} (1 - e^{-t/\tau})$$


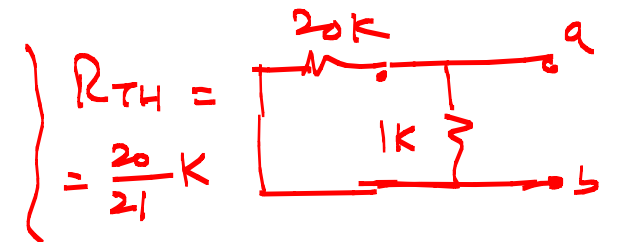
$$v_{OC} = 10 \times \frac{1}{20+1} = \frac{10}{21} \text{ V} = v_{TH}$$



$$R_{TH} = \frac{20}{21} \text{ K}$$

$$\begin{aligned} 0.1 &= \frac{10}{21} \times \left(1 - e^{-t_d \times \frac{21}{2}} \right) \\ &= \frac{10}{21} - \frac{10}{21} \cdot e^{-t_d \cdot \frac{21}{2}} \end{aligned}$$

$$\Rightarrow t_d:$$

Q.3 (a) As shown in Figure 3(a), the CMOS/TTL output of a signal generator is connected to an R-L circuit. The internal resistance of the signal generator is 200Ω .

Sketch and dimension the wave forms of the voltage at the output of the R-L circuit, for two cycles

(12 marks)


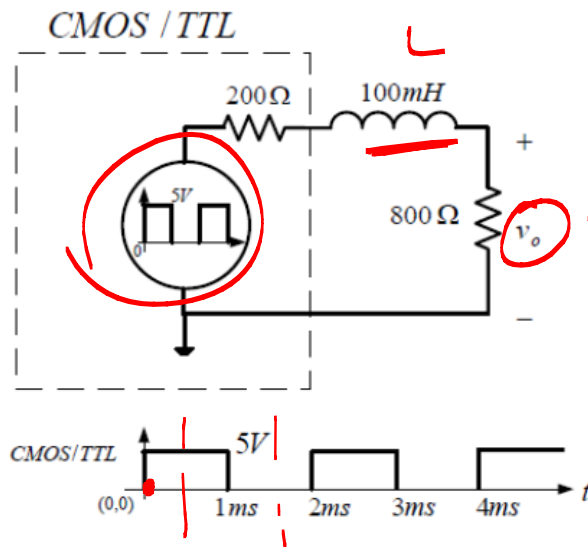


Fig. 3(a)

$$V_o(t) = 800 \times i_L(t)$$


$$i_L(t)$$

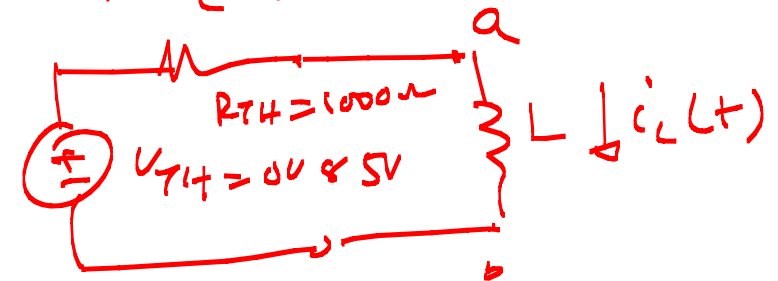

$$0V, 5V$$

$$V_S = 0, V_{TH} = 0$$

$$V_S = 5V, V_{TH} = 5V$$

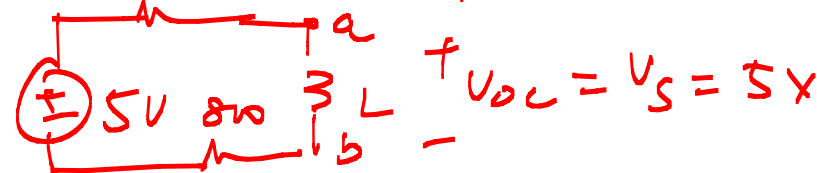


$$R_{TH} = 200 + 800 = 1000\Omega$$

$$\tau = \frac{L}{R_{TH}} = \frac{100 \times 10^{-3}}{1000} = \underline{\underline{0.1 \text{ ms}}}$$


$$i_L(\infty) = \frac{V_{TH}}{R_{TH}} = 5 \text{ mA}$$
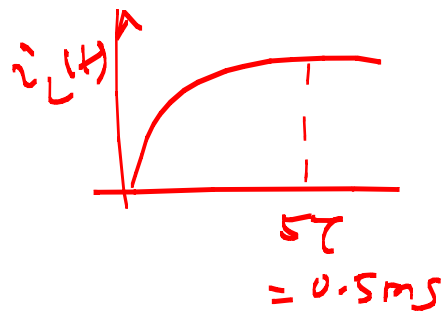
$$V_o(\infty) = 5 \times 10^{-3} \times 800 = 4 \text{ V}$$



$$V_o(t) = i_L(t) \times 800$$
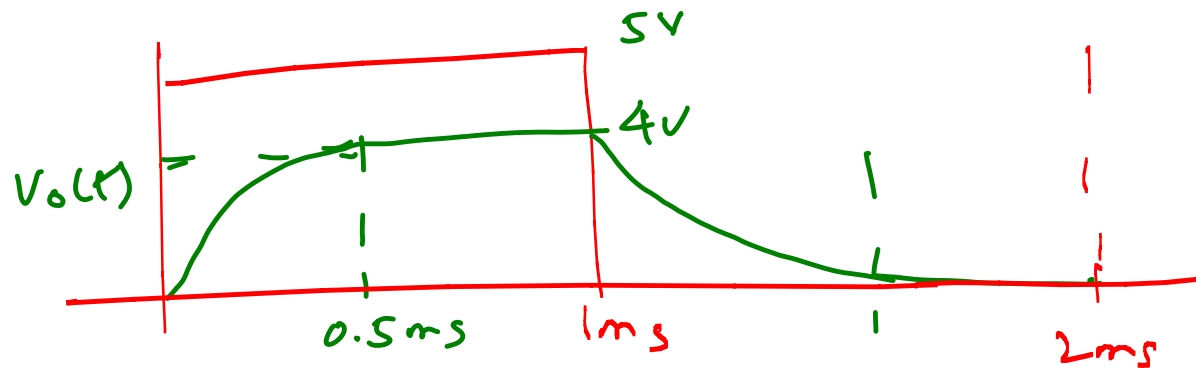
$$= \left[i_L(0) \cdot e^{-t/\tau} + \frac{V_{TH}}{R_{TH}} (1 - e^{-t/\tau}) \right] \times 800$$




Q.3 As shown in Figure Q.3, an AC sinusoidal voltage source is supplying two loads through a step-down ideal transformer. Load-1 is of 110W with a lagging power factor of 0.5. Load-2 is of 55W with a leading power factor of 0.86.

Find the **current** I_p if there is no capacitor connected to the primary side.

Find the value of the **capacitor C** to be connected at the primary of the transformer so that the source current I_p is in phase with the source voltage.

Draw a **phasor diagram** of the source voltage, primary current, capacitor current and the load currents, after capacitor is connected.

A412113

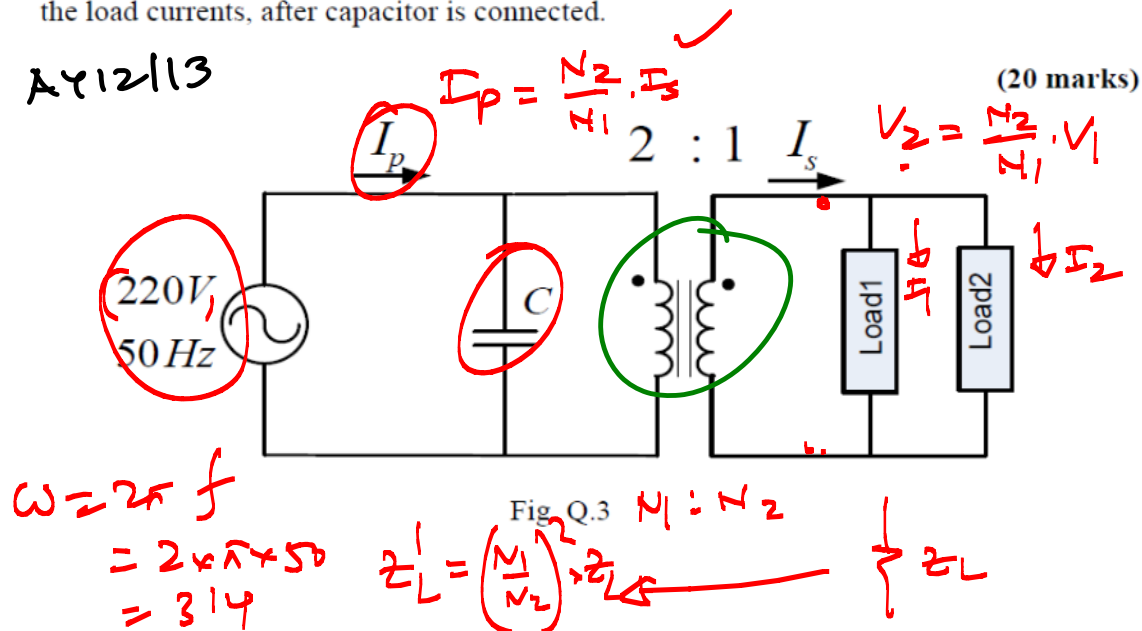

AC power

$$P = V_{rms} \times I_{rms} \times \cos \phi \text{ W}$$

$$P.f. = \cos \phi$$

ϕ is the phase difference between voltage and current.

$$Z = R + jX$$

$$= \sqrt{R^2 + X^2} \angle \phi$$

$$\phi = \tan^{-1} \left(\frac{X}{R} \right)$$

$$I = \frac{V \angle 0}{Z} = \frac{V}{|Z|} \angle -\phi$$

$$\text{Load}_1 = 110 \text{ W}, \quad \text{P.f.} = 0.5 \text{ lagging} \rightarrow I_1$$

$$\text{Load}_2 = 55 \text{ W}, \quad \text{P.f.} = 0.86 \text{ leading} \rightarrow I_2$$

$$V_1 = 220\sqrt{2} \angle 0^\circ$$

$$V_2 = \left(\frac{N_2}{N_1}\right) \cdot V_1 = \frac{1}{2} \times 220\sqrt{2} \angle 0^\circ = \underline{\underline{110\sqrt{2} \angle 0^\circ}}$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

$$P = V_{\text{rms}} \cdot I_{\text{rms}} \cdot \text{P.f.}$$

$$110 = 110 \times I_{\text{rms}} \times 0.5 \Rightarrow I_{1,\text{rms}} = 2 \text{ A.}$$

$$I_1 = 2\sqrt{2} \angle -\cos^{-1} 0.5$$

$$= 2\sqrt{2} \angle -60^\circ$$

$$55 = 110 \times I_{2, \text{rms}} \times 0.86 \Rightarrow I_{2, \text{rms}} = 0.581$$

$$I_2 = 0.581\sqrt{2} \angle +30^\circ$$

$$\begin{aligned} I_s &= I_1 + I_2 = 2\sqrt{2} \angle -60^\circ + 0.581\sqrt{2} \angle 30^\circ \\ &= 2.95 \angle -43.8^\circ \text{ A.} \end{aligned}$$

$$I_p = \frac{1}{2} \times 2.95 \angle -43.8^\circ = 1.475 \angle -43.8^\circ \text{ A.}$$


(without capacitor).

$(I_p + I_c)$ to be in phase with V_s .

$$I_c = \underline{j\omega C \cdot V_s} \quad I_p + I_c = 1.064 \left(-j1.02 + j \cancel{314 \times C \times 220\sqrt{2}} \right)$$

$$\Rightarrow C = \frac{1.02}{314 \times 220\sqrt{2}} = 10.44 \mu\text{F},$$

Phasor diagram

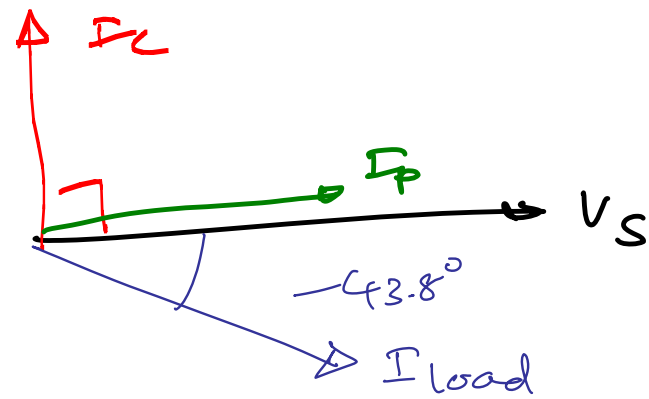

Q.3 (b) As shown in Figure 3(b), a voltage source is supplying an R-C load through a step-up ideal transformer. Also, a capacitive load and an inductive load are connected to primary side of the ideal transformer.

AY 11/12

Find currents: $i_s(t)$, $i_R(t)$, $i_c(t)$, $i_L(t)$, $i_1(t)$ as shown in the figure.

Draw the phasor diagram for the source voltage $v_s(t)$ and all the currents:

$i_s(t)$, $i_R(t)$, $i_c(t)$, $i_L(t)$, $i_1(t)$.

(13 marks)

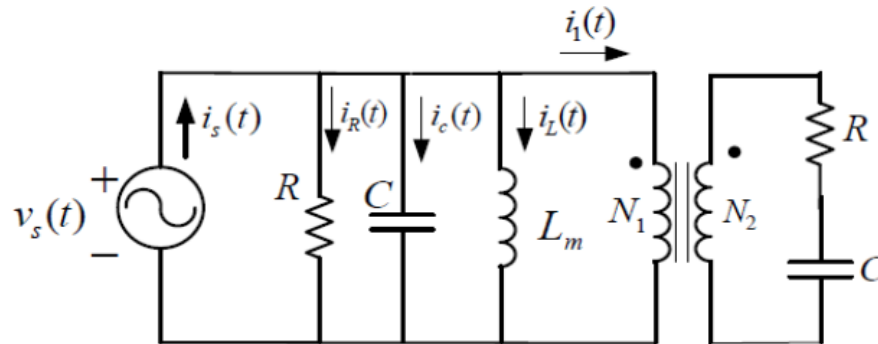


Fig. 3(b)

$$v_s(t) = 300 \cos \omega t$$

$$\omega = 300 \text{ rad / s}$$

$$L_m = 5 \text{ mH}$$

$$C = \frac{1}{900} \text{ F}$$

$$R = 3 \Omega$$

$$L = 5 \text{ mH}$$

$$N_1 = 100$$

$$N_2 = 200$$

Q.4 The magnetic circuit given in Figure Q.4 is made of sheet steel, except for the air gap between de . Find the inductance of the coil. Ignore the flux fringing effect.

Given,

$$l_{ab} = l_{bg} = l_{gh} = l_{ha} = 0.2 \text{ m}$$

$$l_{bc} = l_{fg} = 0.1 \text{ m}$$

$$l_{cd} = l_{ef} = 0.099 \text{ m}$$

$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$

$$\mu_r (\text{sheet steel}) = 4000$$

Ans 12/13


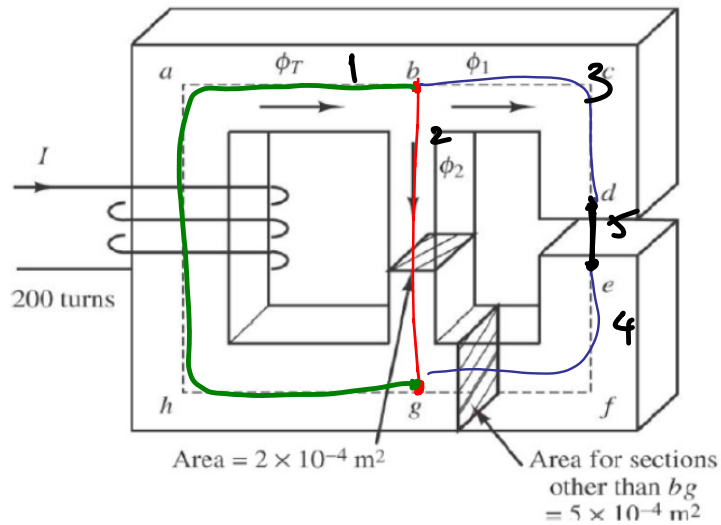


Fig. Q.4

(15 marks)

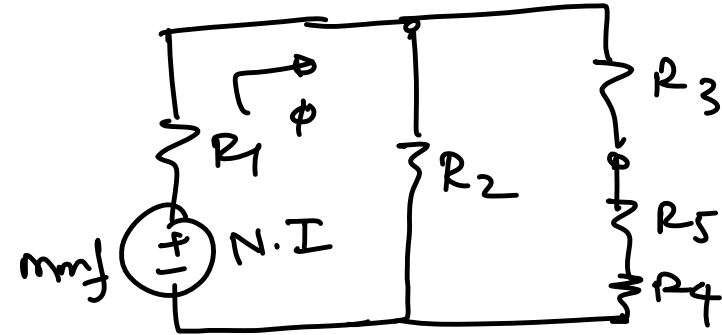


$$R = \frac{l}{\mu A}$$

$$\text{mmf} = NI$$

$$R_{\text{eff}} = R_1 + R_2 \parallel (R_3 + R_5 + R_4)$$

$$\Phi = \frac{NI}{R_{\text{eff}}}$$

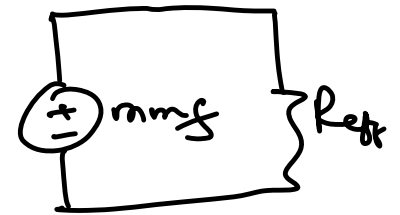

$$L = \frac{\lambda}{H} = \frac{N \cdot \Phi}{I} = \frac{N \cdot (NI/R_{eff})}{I}$$

$$= \frac{N^2}{R_{eff}}$$

$$N = 200 \text{ turns}$$

CG1108

- ✓ 1. Node Voltage Analysis Method
- ✓ 2. Mesh Current Analysis Method
- ✓ 3. Super position principle

1. Thevenin / Norton Equivalent

- 1. Maximum power Transfer
- 2. Nonlinear Element - Graphical Analysis Method.

- L, C →
- DC Transients Analysis
- AC steady state Analysis Impedance, phase
- AC power ✓
- Magnetic Circuits.
- Transformers ✓
- Diodes and DC power Supply
- DC Motors.