

EE1002

Introduction to Circuits and Systems

Part 1 : Lecture 9



AC Steady-state Analysis

AC Steady-state Analysis

- Time varying periodic voltage and current
- Complex number
- Sinusoidal sources
- Phasors for sinusoids
- Impedances for R,L and C
- AC Circuit Analysis with phasors and Impedances
- Examples of AC Circuit analysis

Lab5 Studying AC signals

periodic

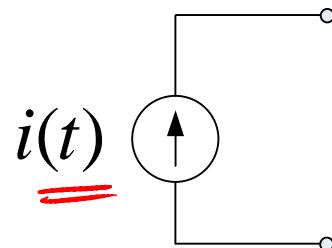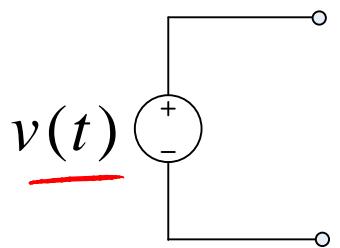

$$\checkmark f = \frac{1}{T} \checkmark, \omega = \frac{2\pi}{T} = 2\pi f, \theta = \omega t$$

Angular frequency

RMS : Root Mean Square


$$\checkmark V_{RMS} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

sq root, mean of the squared signal


October 13

R . M . S.


→ zero-average

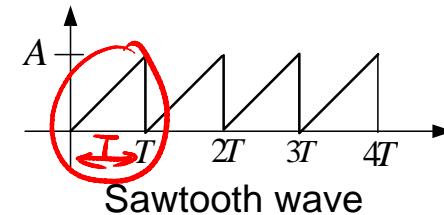

Sawtooth wave

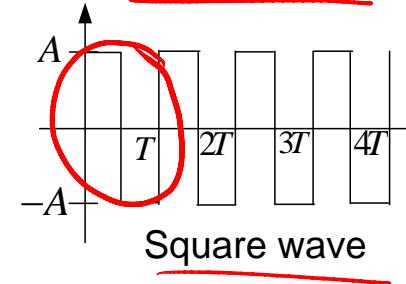

Square wave

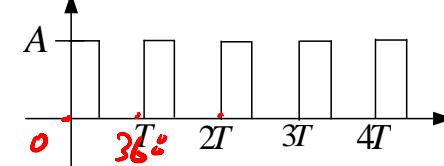

Pulse train



Triangle wave

pure AC


t →

(\omega t = \theta)

*Purely
AC sign*


3

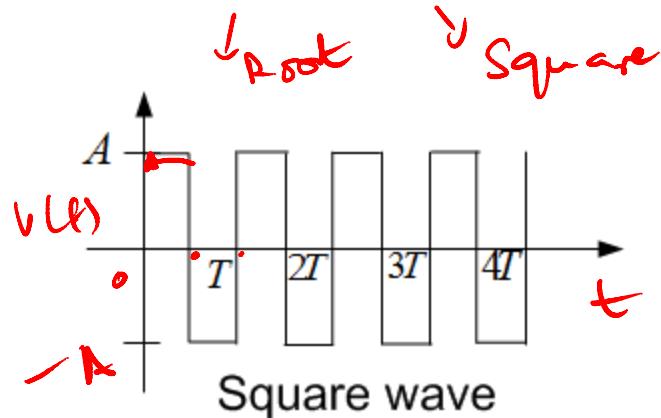$\overline{V}^{\text{mean}}$ RMS value for AC Signals



$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$
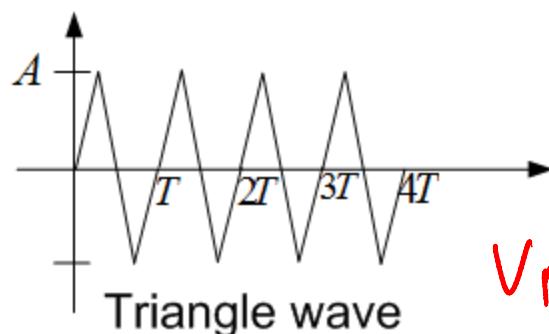
$$\begin{aligned} v(t) &= A \quad 0 \leq t \leq \frac{T}{2} \\ &= -A \quad \frac{T}{2} \leq t \leq T \end{aligned}$$



V_{RMS}
triangular
wave form

$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \left[\int_0^{T/2} v^2(t) dt + \int_{T/2}^T v^2(t) dt \right]}$$

$$= \sqrt{\frac{1}{T} \left[\int_0^{T/2} A^2 dt + \int_{T/2}^T (-A)^2 dt \right]}$$

$$= \sqrt{\frac{1}{T} \cdot A^2 \cdot (T/2 + T - T/2)}$$

$$= A$$


RMS value for AC Sinusoidal

Sinusoidal : $V_m \cos(\omega t + \theta)$

$$\begin{aligned} V_{rms} &= \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = \sqrt{\frac{1}{T} \int_0^T V_m^2 \cos^2(\omega t + \theta) dt} \\ &= \sqrt{\frac{1}{T} \frac{V_m^2}{2} \int_0^T (1 + \cos 2(\omega t + \theta)) dt} = \sqrt{\frac{V_m^2}{2}} = \frac{V_m}{\sqrt{2}} \xrightarrow{\text{Peak}} \\ (\cos^2(\omega t + \theta)) &= \frac{1}{2} [1 + \cos 2(\omega t + \theta)] \\ &= \frac{1}{2} + \frac{1}{2} \cdot \overline{\cos 2(\omega t + \theta)} \\ &\quad \text{Int} \rightarrow 0 \end{aligned}$$

Complex Numbers

Complex number – Euler's Formula

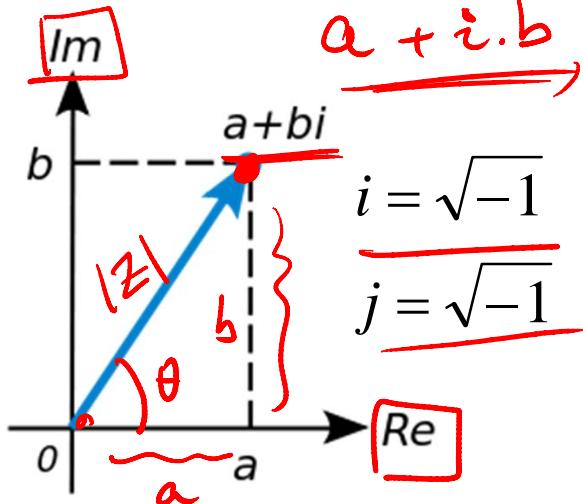

$a + jb$: Rectangular

- Addition/Subtraction
 - Done in rectangular form
- Multiplication/Division
 - Done in polar form

$$a + ib = |z| \angle \theta$$

$z \rightarrow$ Complex number

$$\textcircled{1} |z| = \sqrt{a^2 + b^2}, \tan \theta = \frac{b}{a}$$

$$\left. \begin{array}{l} a = |z| \cdot \cos \theta \\ b = |z| \cdot \sin \theta \end{array} \right\}$$

$$\textcircled{2} \theta = \tan^{-1}\left(\frac{b}{a}\right)$$

$$(a+ib) \pm (c+id) = (a \pm c) + i(b \pm d)$$

$$(a+ib) \times (c+id) = |z_1|(\theta_1 + \theta_2) |z_2|$$

$$= |z_1| |z_2| \underbrace{e^{i(\theta_1 + \theta_2)}}_7$$

Example – Complex Numbers

$$z_1 = \underline{2+3i} = \sqrt{2^2 + 3^2} \cdot \underline{\tan^{-1} \frac{3}{2}} = 3.60 \angle 56.3^\circ$$

$$z_2 = \underline{3+4i} = \sqrt{3^2 + 4^2} \cdot \underline{\tan^{-1} \frac{4}{3}} = 5 \angle 53.13^\circ$$


$$\begin{aligned} z_1 + z_2 &= 2+3i + 3+4i = (2+3) + (3+4)i \\ &= 5+7i \end{aligned}$$

$$z_1 * z_2 = 3.60 \angle 56.3^\circ * 5 \angle 53.13^\circ = 18 \angle 109.43^\circ$$

$$\frac{z_1}{z_2} = \frac{3.60 \angle 56.3^\circ}{5 \angle 53.13^\circ} = \frac{3.60}{5} \angle 56.3 - 53.13^\circ = 0.72 \angle 3.17^\circ$$

Example – Complex Numbers

Sinusoidal AC signals

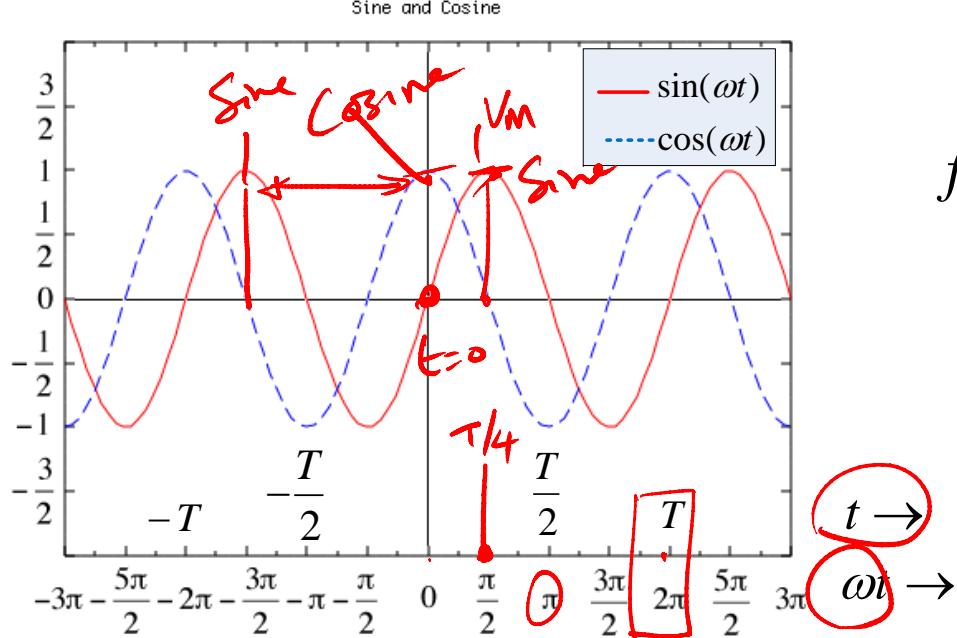

$$v(t) = V_m \cos(\omega t + \theta),$$

V_m is the peak value of voltage

ω is the angular frequency

θ is the phase angle

$$f = \frac{1}{T}$$

$$\omega = \frac{2\pi}{T} = 2\pi f$$

$$\sin \omega t = \underline{\cos (\omega t - 90^\circ)}$$

$\cos (\omega t)$

$\sin(\omega t)$ has a phase angle $\theta = -90^\circ$

$\cos \omega t$ has $\theta = 0^\circ$

$$\underline{\cos \theta - \sin \theta = \cos(-90^\circ) = 90^\circ}$$


$$\omega = 2\pi \times f = 2\pi \times \frac{1}{T}, \quad \omega t = \theta, \text{ rad}$$

Phase difference $\underline{(\theta_1 - \theta_2)}$


$$V(t) = V_m \cdot \cos(\omega t + \theta_1), i(t) = I_m \cdot \cos(\omega t + \theta_2)$$

- The signal that reaches the peak earlier is said to be leading. Thus, cosine leads sine. or lag
- However, one may say that sine leads cosine as it peaks much earlier..
- To resolve this confusion, if the phase difference ($\theta_1 - \theta_2$) is positive and less than 180 degree, then v1 is leading v2.
Else, v1 is lagging v2.

Phase Difference

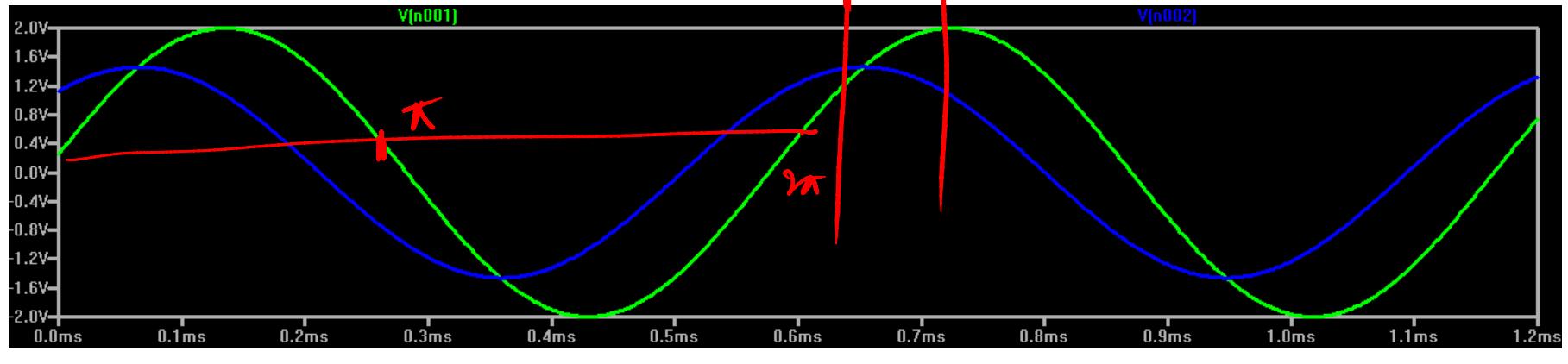

$t_1 < t_2$
 t_1
 t_2

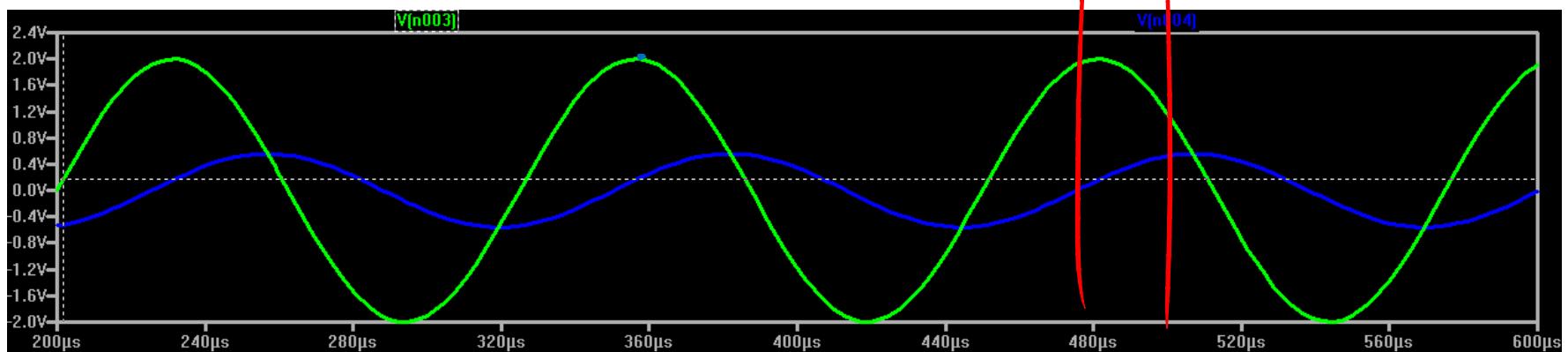

EE1002

Introduction to Circuits and Systems

Part 1 : Lecture 9

AC Steady-state Analysis (second half)

Phasor Definition

- For a sinusoidal voltage of


$$v_1(t) = V_m \cos(\omega t + \theta)$$

The frequencies of all sinusoids must be same.

- Phasor : $V_m \angle \theta$
 - Phasor is a complex number
 - Absolute value equal to the peak
 - Argument same as the phase angle

- Example: $v(t) = 200 \cos(300t + 45^\circ) \Rightarrow 200 \angle 45^\circ$
 $i(t) = 10 \cos(300t - 60^\circ) \Rightarrow 10 \angle -60^\circ$

Euler's formula and phasor

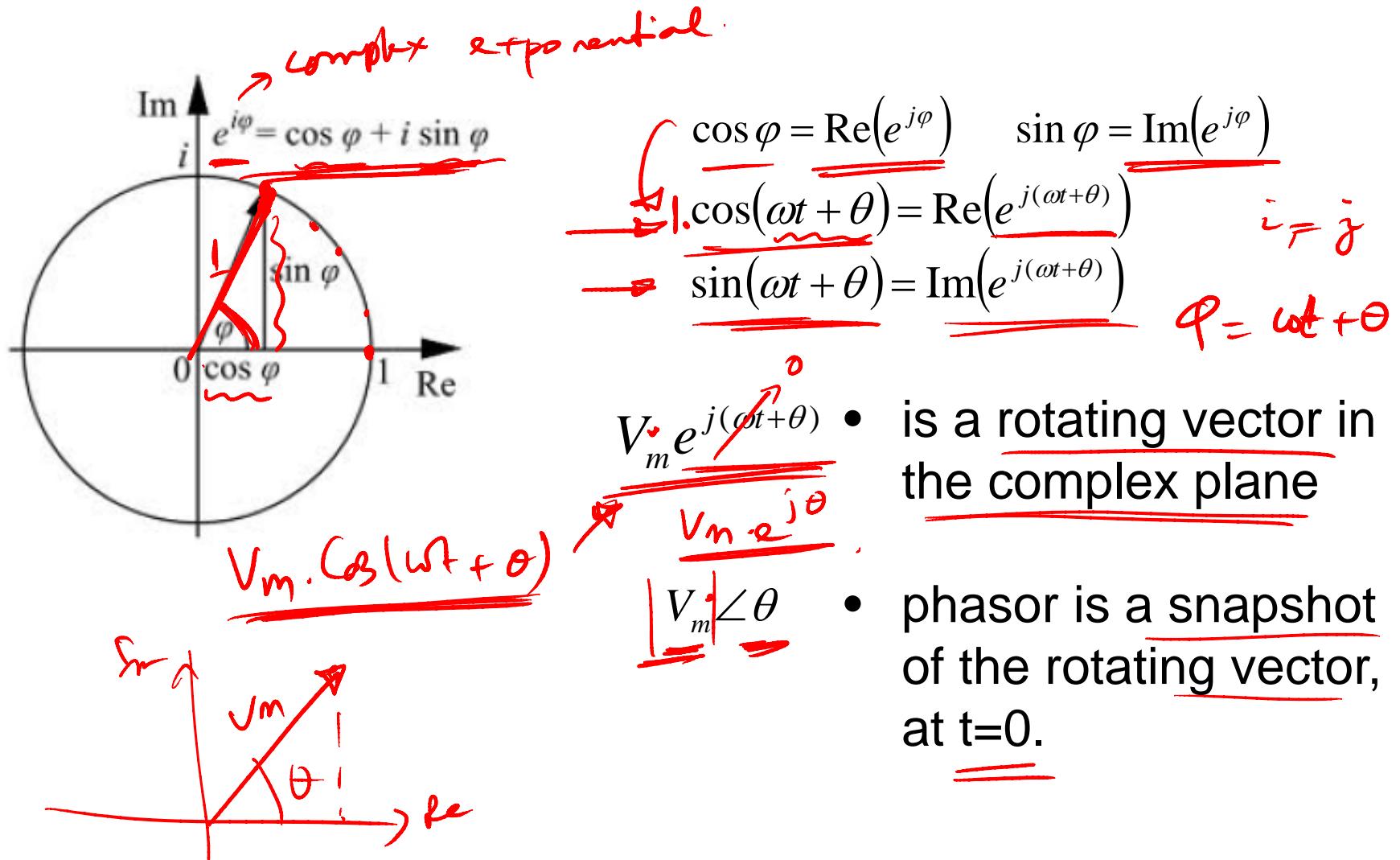

Phasor diagram

$$v_1(t) = 3 \cos(\omega t + 40^\circ) : 3 \angle 40^\circ$$


$$v_2(t) = 4 \cos(\omega t - 20^\circ) : 4 \angle -20^\circ$$

$$v_3(t) = 5 \sin(\omega t - 20^\circ)$$

$$= 5 \cos(\omega t - 20 - 90^\circ) = 5 \cos(\omega t - 110^\circ) : 5 \angle -110^\circ$$

$$v_4(t) = 10 \sin(\omega t + 80^\circ)$$
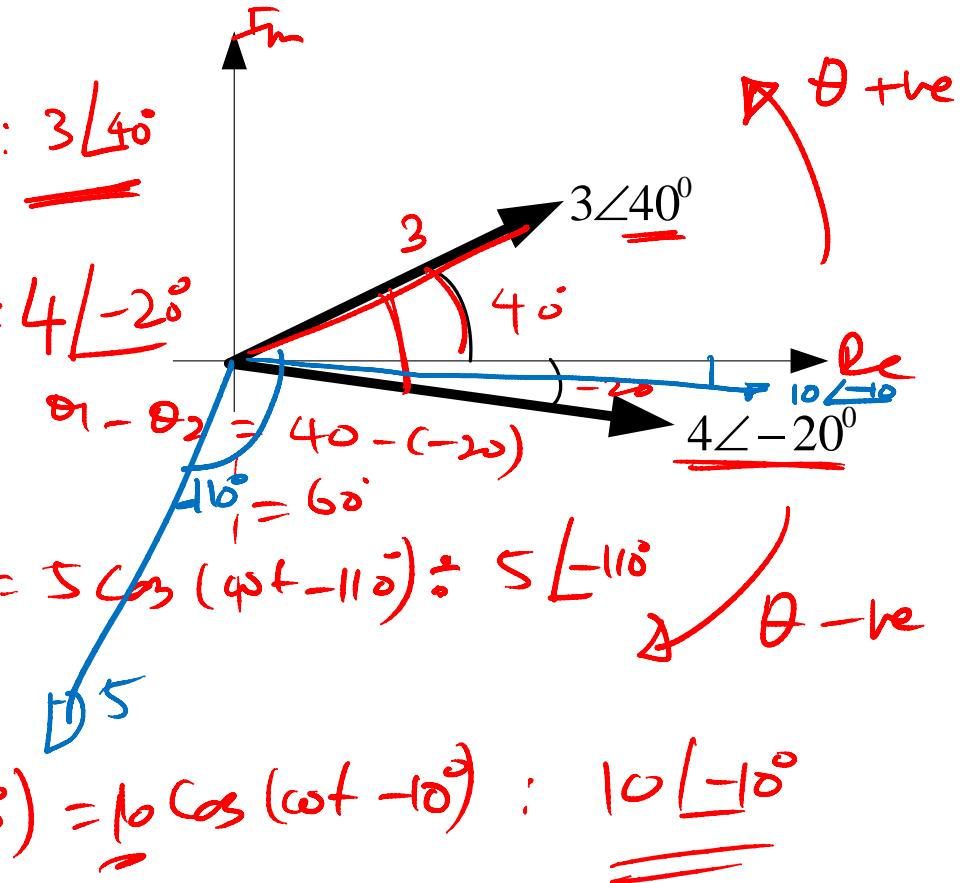
$$= 10 \cos(\omega t + 80 - 90^\circ) = 10 \cos(\omega t - 10^\circ) : 10 \angle -10^\circ$$



Impedances

- Also known as complex resistance,
frequency-dependent resistance.
- Ratio of voltage phasor to current phasor

$$\text{In DC resistance } R = \frac{V}{I} \quad (\text{Ohm's law})$$

In AC : phasors $\begin{cases} \text{Voltage phasor vs } V(t) \\ \text{Current phasor vs } i(t) \end{cases}$

$$\boxed{\frac{\text{Voltage phasor}}{\text{Current phasor}} = \text{Impedance}}$$

Impedance of Inductance


$$i_L(t) = \underline{I_m} \cdot \sin(\omega t + \theta) = \underline{I_m} \cdot \cos(\omega t + \theta - 90^\circ) : I_m | \theta - 90^\circ$$
$$v_L(t) = L \frac{di_L(t)}{dt} = \underline{(L\omega I_m)} \cos(\omega t + \theta) : L\omega I_m \cdot | \theta$$

Writing the phasors for the current and the voltage

$$Z_L = \frac{V_L \text{ (phasor)}}{I_L \text{ (phasor)}} = \frac{L \cdot \omega \cdot I_m | \theta}{I_m | \theta - 90^\circ}$$
$$= \frac{L \omega \cdot I_m}{Z_m} \cdot | \theta - (\theta - 90^\circ)$$
$$= \underline{L\omega | 90^\circ} = j L\omega \cdot$$

$$\underline{L} \equiv \underline{j L\omega}$$

Capacitance

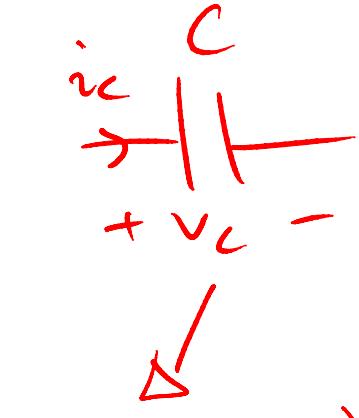

$$i_C = C \cdot \frac{dV_C}{dt}$$

$$V_C(t) = V_m \sin(\omega t + \theta) = \underline{V_m \cos(\omega t + \theta - 90^\circ)}$$


$$\left. \begin{aligned} i_C(t) &= C \cdot \frac{d}{dt} (V_m \sin(\omega t + \theta)) \\ i_C(t) &= C \cdot \underline{\omega \cdot V_m \cdot \cos(\omega t + \theta)} \\ \underline{j \omega C} &= \underline{-j \frac{1}{\omega C}} \end{aligned} \right\}$$

$$\text{Voltage phasor} = V_m \underline{[\theta - 90^\circ]}$$

$$\text{Current phasor} = C \cdot \underline{\omega \cdot V_m \cdot [\theta]}$$

$$\begin{aligned} Z_C &= \text{Impedance of Cap} = \frac{V_m \underline{[\theta - 90^\circ]}}{C \cdot \underline{\omega \cdot V_m \cdot [\theta]}} = \frac{1}{C \omega} \underline{[-90^\circ]} \\ &= \underline{\frac{1}{j C \omega}} \end{aligned}$$

Resistance

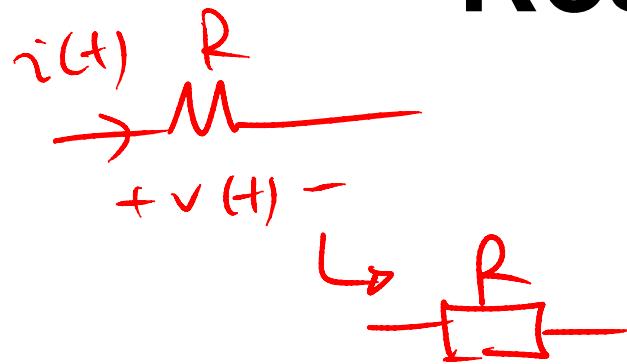



$$v(t) = R \cdot i(t)$$


$$i(t) = I_m \cos(\omega t + \theta) : I_m \angle \theta$$

$$v(t) = R \cdot I_m \cdot \cos(\omega t + \theta) : R I_m \angle \theta$$

$$Z_R = \text{Impedance of resistance} = \frac{R \cdot I_m \angle \theta}{I_m \angle \theta} = R .$$

Impedances for R, L and C

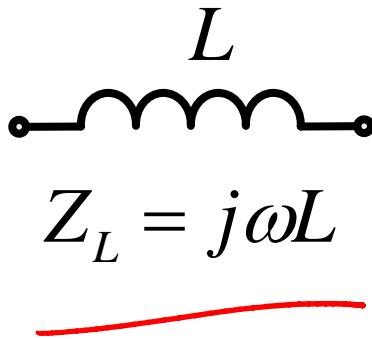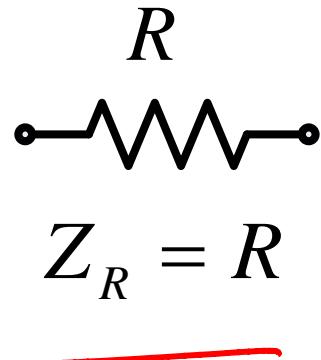

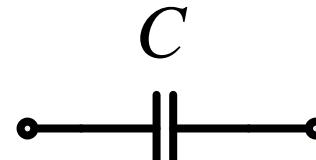

A circuit diagram symbol for a capacitor, consisting of two vertical terminals connected by a single vertical line representing the capacitor element.


$$C$$
$$Z_C = \frac{1}{j\omega C} = -j\frac{1}{\omega C}$$

Circuit Analysis with phasors and Complex Impedances


- Replace the sinusoidal voltage and current sources with the corresponding phasors.
- Replace the resistance, inductance and capacitance with their respective impedances.
- Analyze the circuits as before with DC sources and resistances only.
- Convert phasors back to the sinusoidals.

$$I_L = \frac{10 \angle 45^\circ}{Z_L + Z_{eq}}$$
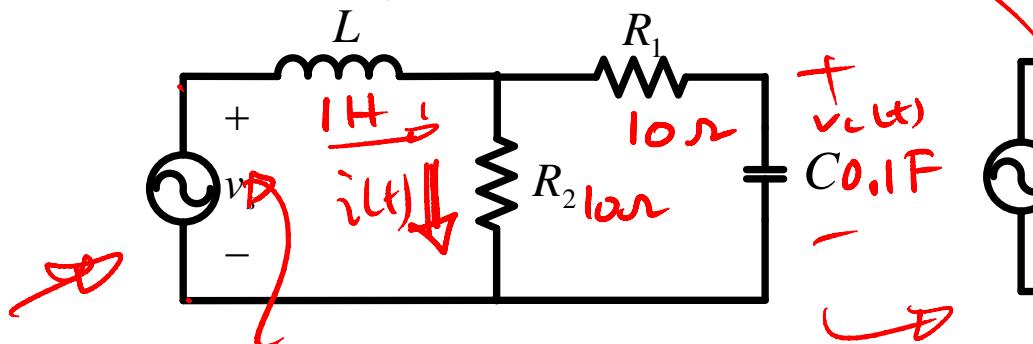
$$I = I_L \times \frac{Z_R + Z_C}{Z_R + Z_L + Z_C}$$



Example

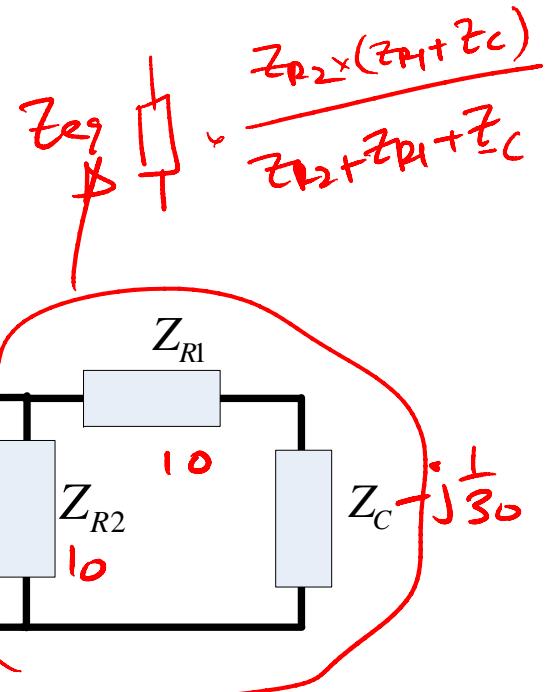

$$\omega = \frac{10 \cos(300t + 45^\circ)}{300 \text{ rad/sec}}$$


$$L \rightarrow 1H \quad Z_L = \omega L \angle 90^\circ = j\omega L \\ = 300 \times 1 = j300 \angle 90^\circ$$

$$C = 0.1\text{F} \quad Z_C = -j\frac{1}{\omega C} = -j\frac{1}{300 \times 0.1} = -j\frac{1}{30}$$

$$Z_{R1} + Z_C = 10 - j\frac{1}{30} \angle 0^\circ,$$

$$I = I_x \angle 0^\circ \quad i(t) = I_x \cdot \cos(300t + \theta_x) \\ = -j\frac{1}{30}$$

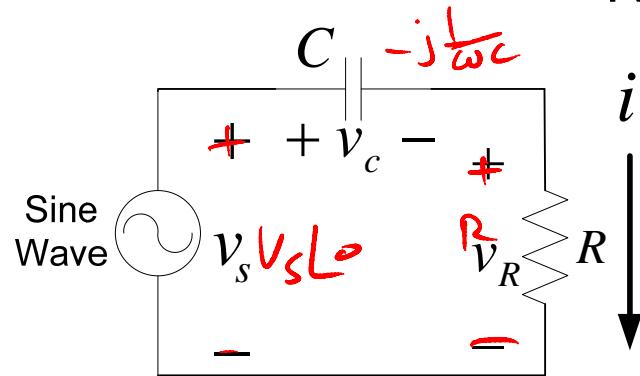Phase difference between V_R and V_s in RC circuit




V_R, V_s

$$|V_R| \angle \theta_r, |V_s| \angle \theta_s$$

$$\theta_r - \theta_s$$
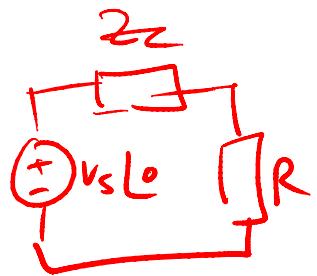
$$\text{say } \theta_s = 0, \Rightarrow \theta_r ?$$



$$\theta = 90 - \tan^{-1}(\omega RC) = 90 - \tan^{-1}(2\pi f RC)$$

$$\theta = \Delta\Phi = \frac{\Delta t}{T} \times 360^\circ$$

$$|V_s| \angle 0$$

$$V_R = |V_s| \angle 0 \left(\frac{1}{R + j \frac{1}{\omega C}} \right) = |V_s| \angle 0 \cdot \frac{R \angle 0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \times \angle 0$$



V_R leads V_s

$$\theta = \tan^{-1}\left(\frac{1}{\omega C R}\right) = -\tan^{-1}\left(\frac{1}{\omega C R}\right)$$

$$V_R = |V_s| \angle -\theta \Rightarrow \theta_r = -\theta = +\tan^{-1}\frac{1}{\omega C R}$$

$$\Delta\phi =$$

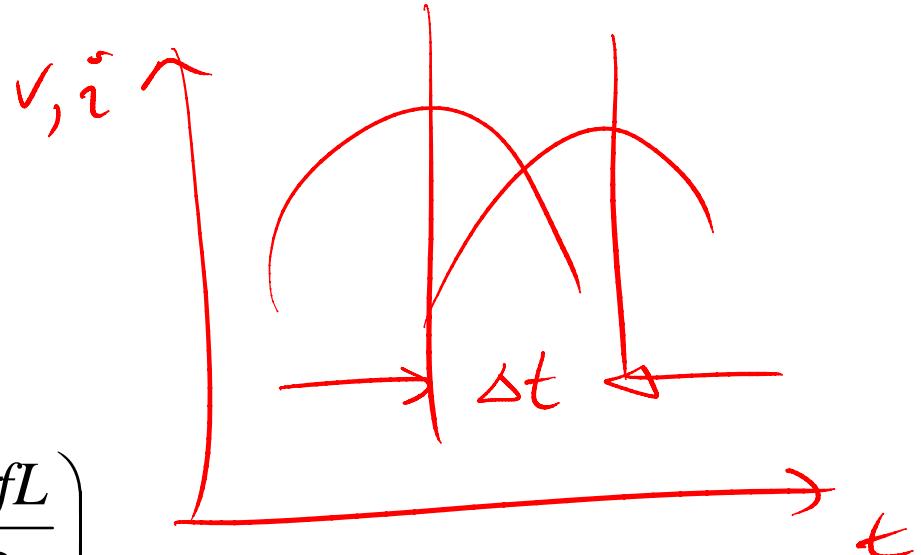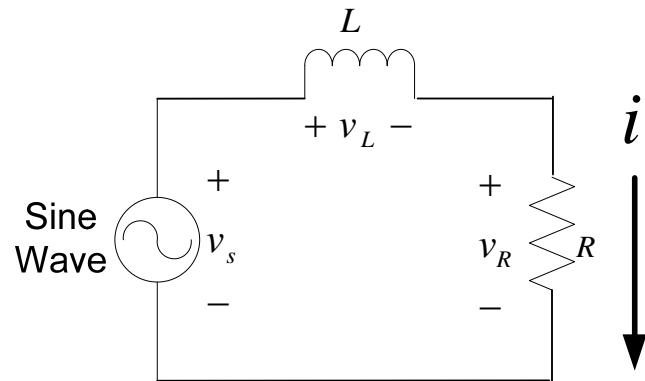Phase difference between V_R and V_s in RL circuit



$$\theta = -\tan^{-1}\left(\frac{\omega L}{R}\right) = -\tan^{-1}\left(\frac{2\pi f L}{R}\right)$$

$$\theta = \Delta\Phi = \frac{\Delta t}{T} \times 360^\circ$$

$$\frac{t \rightarrow T}{t \rightarrow 2\pi} \cdot \frac{\Delta t}{T} \times 2\pi = \Delta\Theta$$

Lab 5

- RMS voltage can be measured both by the oscilloscope and the multimeter
 - Multimeter not so accurate at frequency beyond 1kHz
- Take note of Oscilloscope probe GND
 - Can not have more than one GND in circuit
- The last lab before the lab test
- Finish it early and practice the last labs if you get time