

EE1002

Introduction to Circuits and Systems

Part 1 : Lecture 1

Learning Outcomes for EE1002

- a) To be able to **apply** various **circuit theories** in **analysis** of **electrical** and **magnetic** circuits.
- b) To be able to use electrical and electromechanical devices such as **transformer**, **electrical machines**, **power semiconductor switches**, **digital logic ICs** for building an **integrated system**.

Learning outcomes

- c) To be able to choose appropriate values of circuit components to meet specifications and conduct experiments to demonstrate the circuit operation.
- d) To be able to verify the functionality of circuits using circuit simulation software LTspice.

Learning outcomes

- d) To be able to **use equipment** such as **DC power supply, signal generator, digital oscilloscope, multi-meter** for prototyping circuits in the laboratory.
- e) To follow **safe working practices** and proper waste disposal for recycling.
- f) To be able to work in groups by **communicating well with team members** and supervisors for project implementation.

Assessment

- Assessment (50% hands-on +50% theory)
- Labs (5 expt. (10%) + lab test (10%))
- Project (3 labs + final demo)(30%)
- Midterm test (10%)
- Final Exam (40%)

Learning Resources

- Lecture notes (concise version of text books)
- Lecture slides and in-class discussions
- Tutorials
- Extra questions/Past year papers
- Text books
- Internet...

Introduction

Part1 Syllabus

- Fundamentals of Electric circuits
- Circuit Analysis Techniques

Circuit Analysis

1.

- DC Analysis (Sources are constant in time)
- AC Analysis (Sources are time-varying & periodic)

2.

- Steady-state analysis (constant in time)
- Transient analysis (time-varying)

Circuit Theory

- Ohm's Law
- Kirchhoff's voltage law
- Kirchhoff's Current law
- Faraday's Law

Circuit Analysis (steady-state)

- DC Circuit analysis
 - Node voltage Analysis
 - Mesh Current Analysis
 - Superposition technique
 - Equivalent circuit method
 - Thevenin's equivalent
 - Norton's equivalent
- AC circuit analysis
 - Same as DC circuit analysis but in complex domain

AC steady-state analysis

- Complex algebra
- Phasor
- Impedance

Equipment

- DC Power supply
- Multimeter
- Ammeter
- Signal Generator
- Oscilloscope
- Bread-board
- Soldering PCB
- Misc. wiring tools

Circuit Elements

- Source (Active Element)
 - Voltage source or Current source
 - Independent source or Dependent source
- Load (Passive Element)
 - Resistor
 - Inductor
 - Capacitor


Simulation-Analysis- Experimentation

- Computer Simulation using LT Spice

Part1_A Syllabus

- Fundamentals of Electrical Circuits
 - What is meant by electrical circuit?
 - Circuit terminology
 - Electrical quantities
 - Circuit elements

A circuit diagram showing a battery, a switch, a fan, and a light bulb connected in a loop. The battery is on the left, with a red '+' sign above it and a black '-' sign below it. A red wire connects the positive terminal to a red switch. The switch is connected to a blue fan. The fan is connected to a yellow light bulb. The light bulb is connected back to the negative terminal of the battery via a red wire.

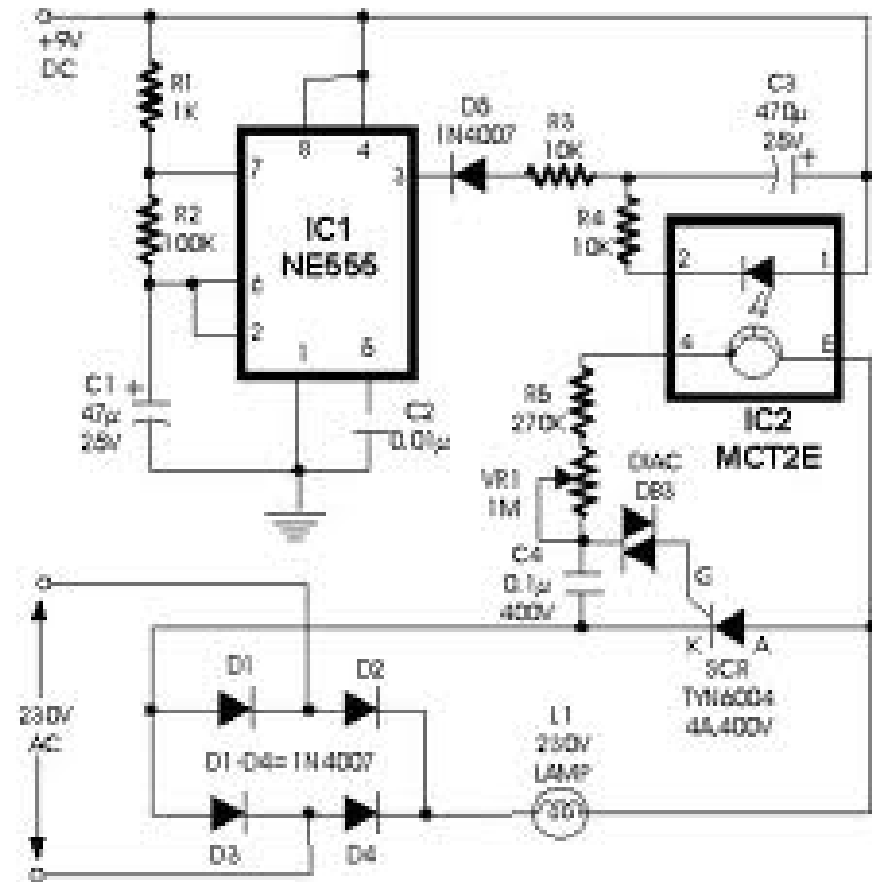

Circuit Terminology

- Node
- Branch
- Mesh
- Loop
- Super node


Electrical Quantities

- Charge
- Current
- Voltage
- Power
- Energy

Electrical quantities


Charge

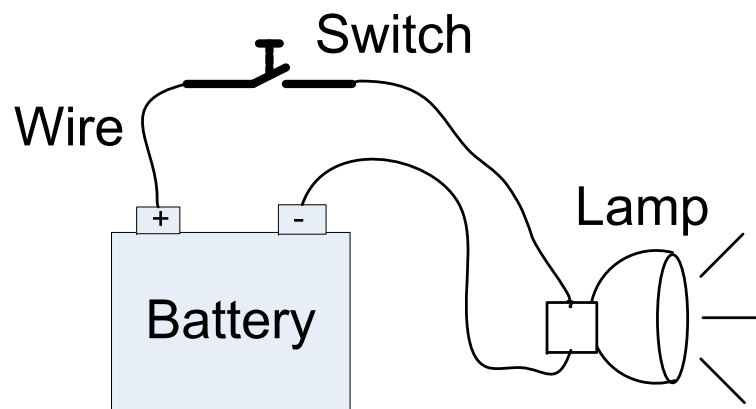- Electrons are the most common charge carriers
 - Charge of electron $q_e = -1.602 \times 10^{-19} C$
- Unit : Coulomb, Symbol - Q
- Charge carriers move around in closed paths, to carry useful **information** or **energy**



Current

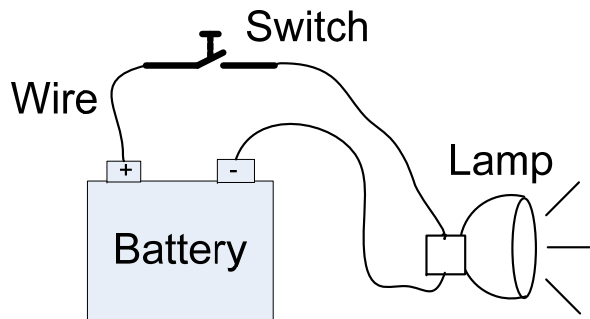- Electric current is the time **rate of flow of electrical charge** through an element



$$i(t) = \frac{dq(t)}{dt}$$

$$q(t) = q(t_0) + \int_{t_0}^t i(t) dt$$

- Unit – Ampere, symbol - /
- Current has a **direction** (that of positive charge)
- DC – direct current (unidirectional)
- AC – alternating current (bidirectional and periodic)

Voltage

- Voltage is electrical potential difference (is a measure of the **energy transferred per unit charge between two points**).
- Unit – Volt, symbol - V
- Energy can be gained or lost, thus voltage has **polarity**: positive and negative
 - $V_{ab} = -V_{ba}$

$$V_{ab} = P_a - P_b \\ = V_a - V_b$$

Electric Power

- Voltage = Energy per unit charge ✓
- Current = Charge per unit time ✓
- Voltage x current = Energy per unit time
- Electric Power = Voltage x Current

$$P = V \times I$$

Derive SI units for Voltage

Quantity	Unit	Symbol
Length	Meter	m
Mass	Kilogram	Kg
Time	Second	s
Electric Current	Ampere	A
Temperature	Kelvin	K
Luminous intensity	Candela	cd

$$\text{Voltage} = \frac{\text{Work done}}{\text{charge}} = \frac{\text{Force} \times \text{distance}}{\text{charge}}$$

$$\text{Force} = \text{Mass} \times \text{Accn} = \text{kg} \times \text{m} \times \text{s}^{-2}$$

$$\text{charge} = \text{A} \cdot \text{s}$$

$$\text{Voltage} = \frac{\text{kg} \cdot \text{m} \cdot \text{s}^{-2} \times \text{m}}{\text{A} \cdot \text{s}} = \underline{\underline{\text{kg} \cdot \text{m}^2 \cdot \text{s}^{-3} \text{A}^{-1}}}$$

- Circuit Elements
 - Source
 - Resistance
 - Conductor

Sources



- Various sources of electrical energy
 - Batteries
 - Electric Generators
 - Fuel Cells
 - Solar panels
- All electrical sources have voltage and current at their output, which is a measure of the power output
- Sources are classified as either **voltage source** or **current source**

$$\text{power} = \frac{\text{Energy}}{\text{time}}$$

↳ $V \times I$



Independent Voltage source

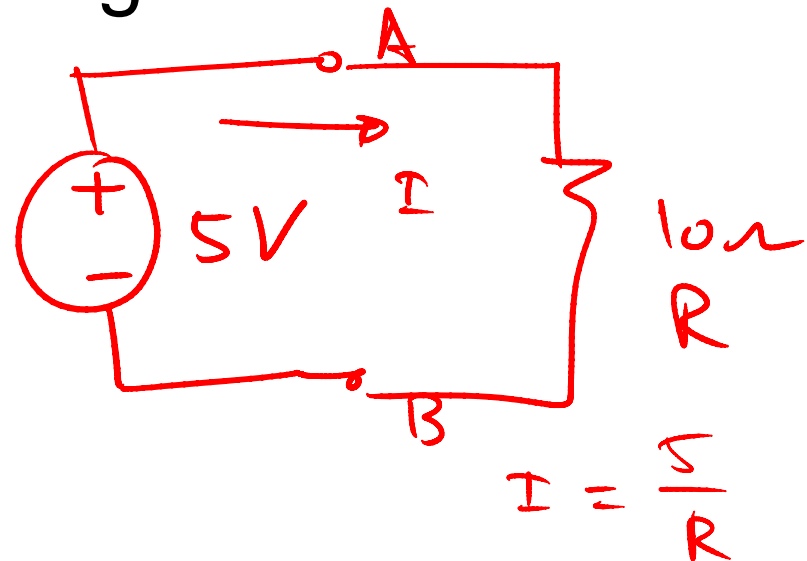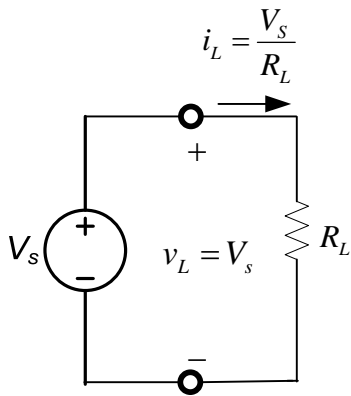- An ideal **voltage source** maintains the **voltage across its terminals** irrespective of the current flowing through it.




Independent Current source

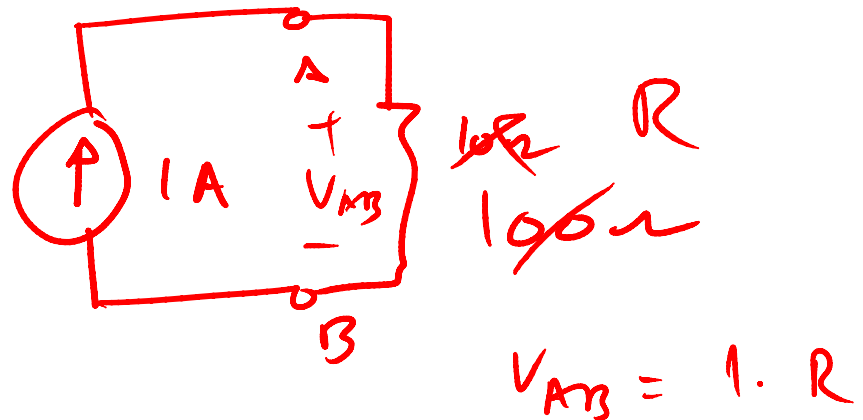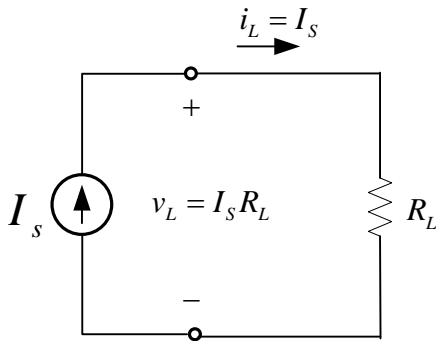- An ideal current source forces a specified current to flow through itself, irrespective of the voltage across it.



V-I Curve

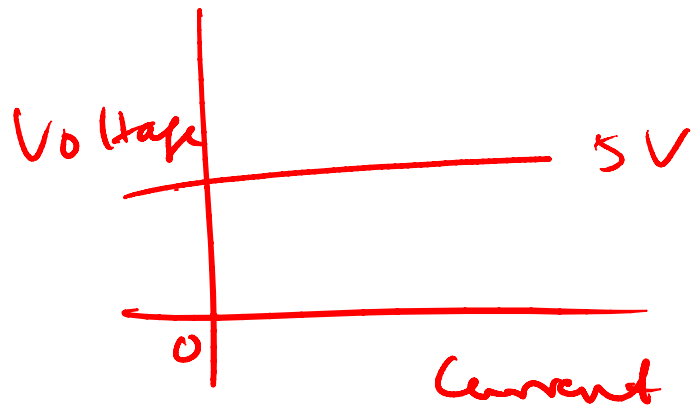

Ideal
Voltage Source




Ideal
Current Source


Dependent source

- If the characteristic output of the source is **dependent on any other variable** (current or voltage) in another part of the circuit, then it is known as dependent source.



Dependent voltage source

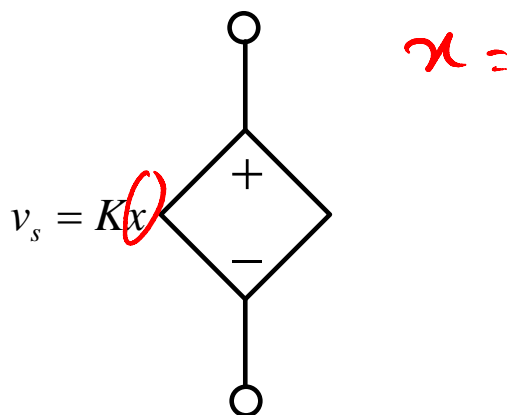

Dependent current source

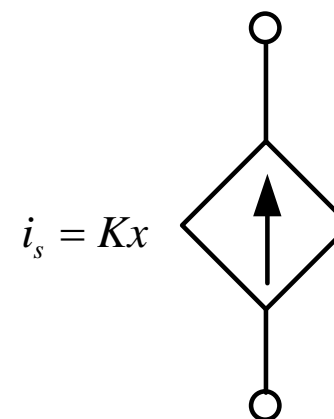



Examples of Dependent source

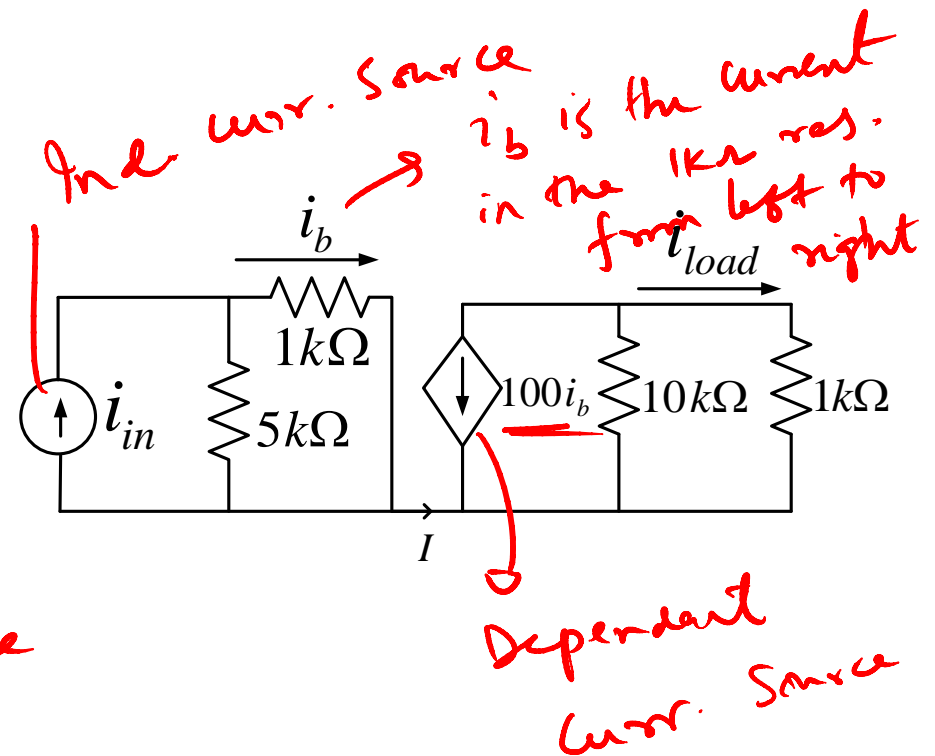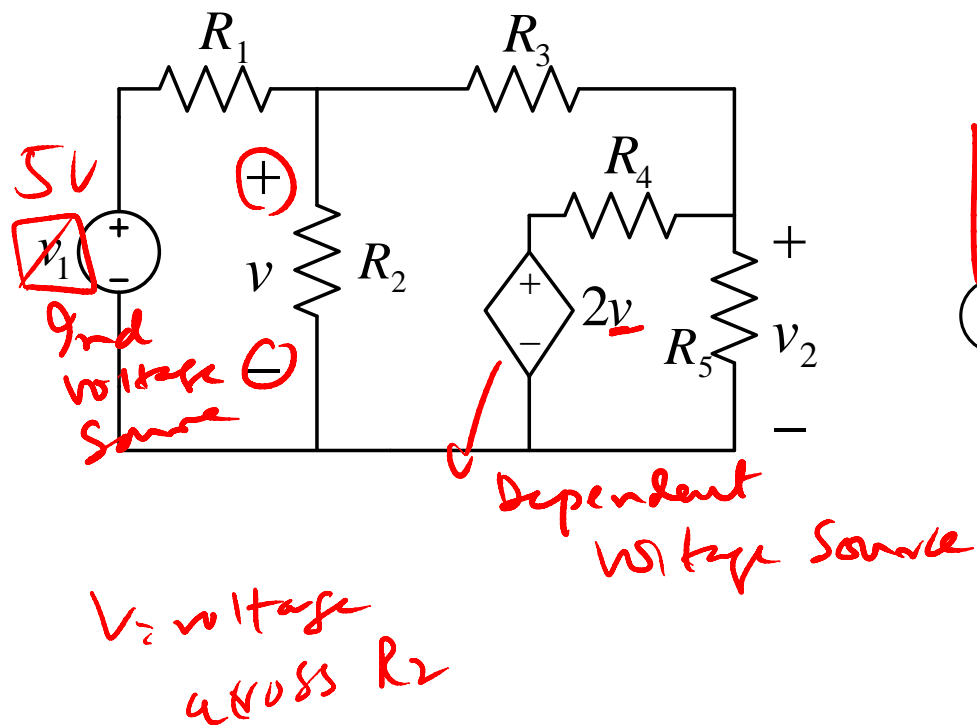

Source and Load

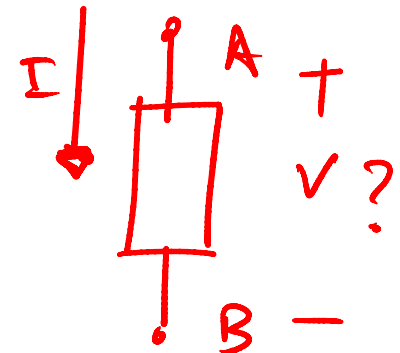
- Source(Active Element)
 - Charge moves from negative voltage polarity to positive polarity, it gains energy.
 - Current leaves the positive polarity
- Load (Passive Element)
 - Charge moves from positive voltage polarity to negative polarity, it losses energy.
 - Current enters the positive polarity



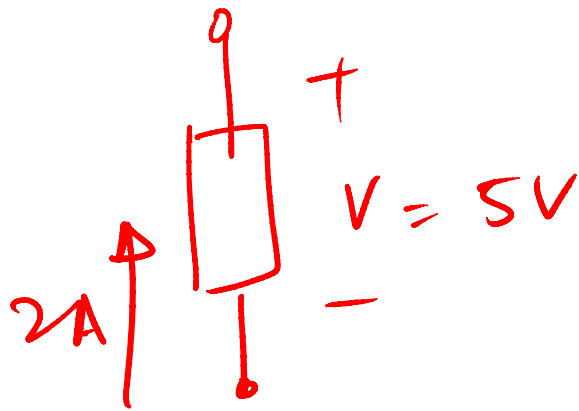

Source

Active Element

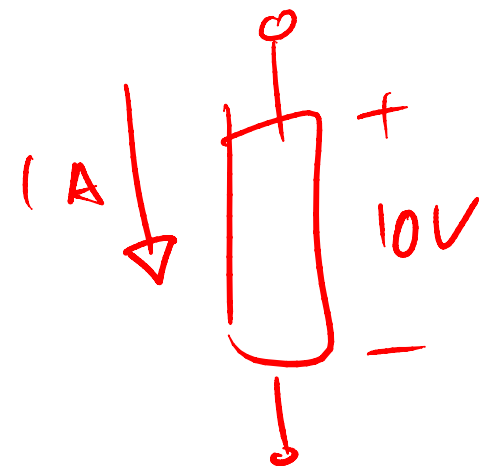

Load

Passive
element

1. Converts to
other form of

→ absorbs, ^{energy} dissipates