

EE1002/CG1108 Tutorial 1

1. Use Kirchoff's current law to determine the unknown currents in the circuit of the Figure 1.
Assume that $I_0 = -2A$, $I_1 = -4A$, $I_3 = 8A$ and $V_s = 12V$.

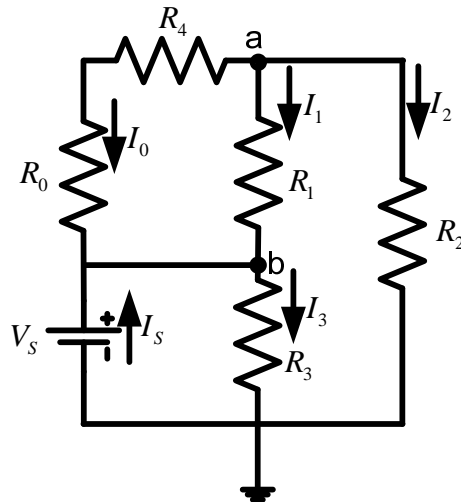


Figure 1

Ans. $I_2 = 6A$, $I_3 = 2A$

2. Apply KVL to find the voltages v_1 and v_2 in the Figure 2.

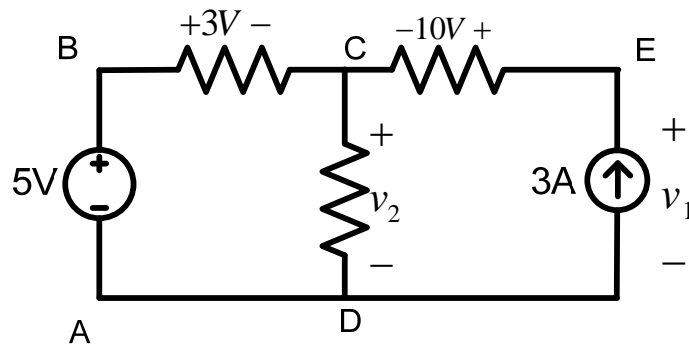


Figure 2

Ans. $v_1 = 12V$, $v_2 = 2V$

3. For the circuit given in Figure 3,
- Determine which components are absorbing power and which are delivering power.
 - Is conservation of power satisfied? Explain your answer.

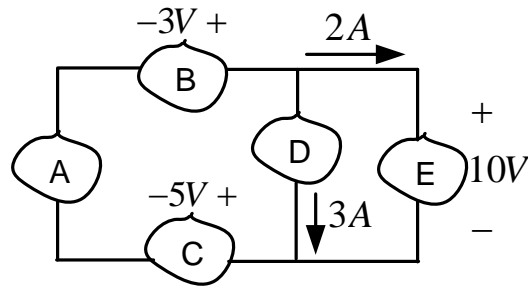


Figure 3

Ans: **Absorbing power: C,D,E; Delivering power: A,B**

4. In the circuit given in Figure 4, the power absorbed by the 15-Ohm resistor is 15W. Find R.

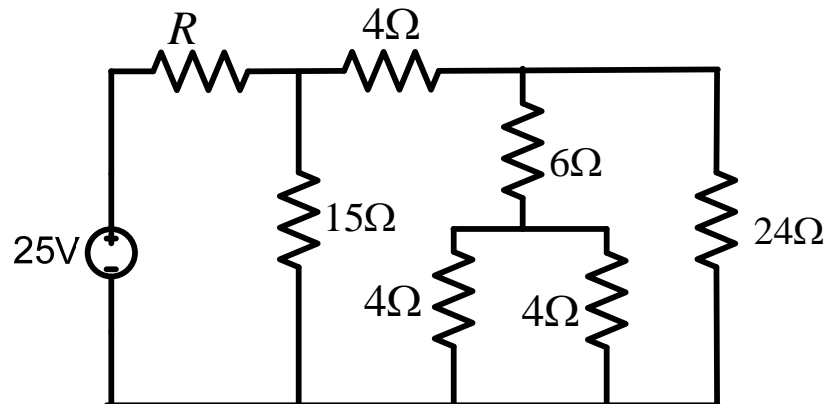


Figure 4

Ans. $R = 4\Omega$

EE1002/CG1108 Tutorial 2

5. For the circuit shown in Figure 4, find:

i) The currents i_1 and i_2 .

Ans. $i_1 = -1.8A, i_2 = -1.2A$

ii) The power delivered by the 3A current source and by the 12V voltage source.

Ans. 279W, 6.17W

iii) The total power dissipated by the circuit.

Ans. 285.17W

Given $R_1=25\text{ ohm}, R_2=10\text{ ohm}, R_3=5\text{ ohm}, R_4=7\text{ ohm}$.

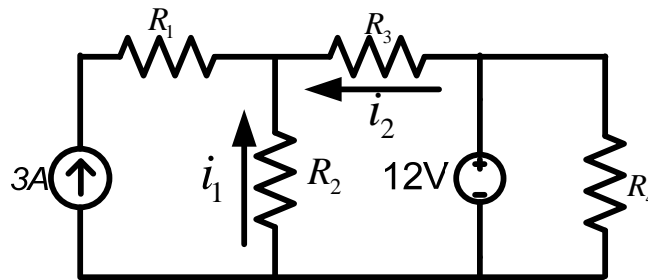


Figure 5

6. Given the circuit of Figure 6:

i) Determine the power delivered by the dependent current source.

Ans. 108W

ii) Determine the power delivered by the voltage source.

Ans. 0W

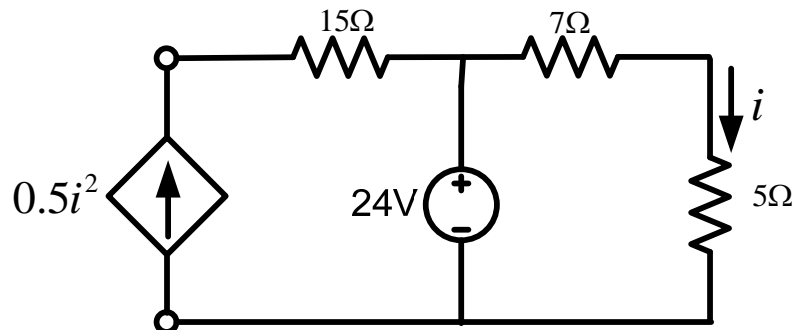


Figure 6

7. Consider NiMH hobbyist batteries shown in the circuit of Figure 7:
- If $V_1=12.0\text{V}$, $R_1=0.15\text{ ohm}$, $R_L=2.55\text{ ohm}$, find the load current I_L and the power dissipated by the load.
 Ans. $I_L = 4.44\text{A}$, $P_L = 50.4\text{W}$
 - If we connect a second battery in parallel with battery 1 that has voltage $V_2=12\text{V}$ and $R_2=0.28\text{ ohm}$, will the load current I_L increase or decrease? By how much?

Use mesh current analysis method.

Ans. *Increases by 0.09A*

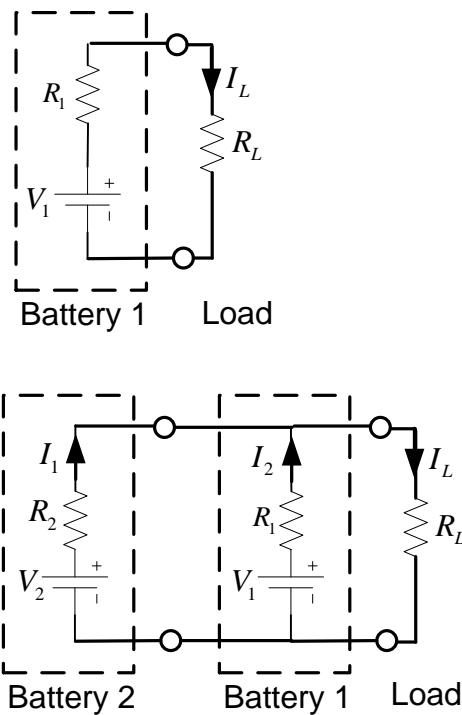


Figure 7

8. Using node voltage analysis in the circuit of Figure 8, find the current i through the voltage source.

Ans. $i=8.03A$

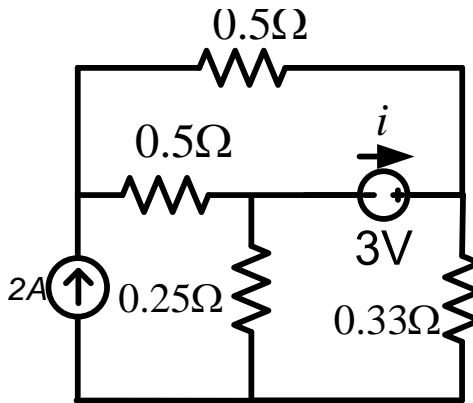


Figure 8

9. Using KCL, perform node analysis in the circuit shown in Figure 9 and determine voltage across R_4 . Note that one source is a controlled voltage source

$V_s=5V$, $A_v=70$, $R_1=2.2k\Omega$, $R_2=1.8k\Omega$, $R_3=6.8k\Omega$, $R_4=220\Omega$.

Ans. $8.757mV$

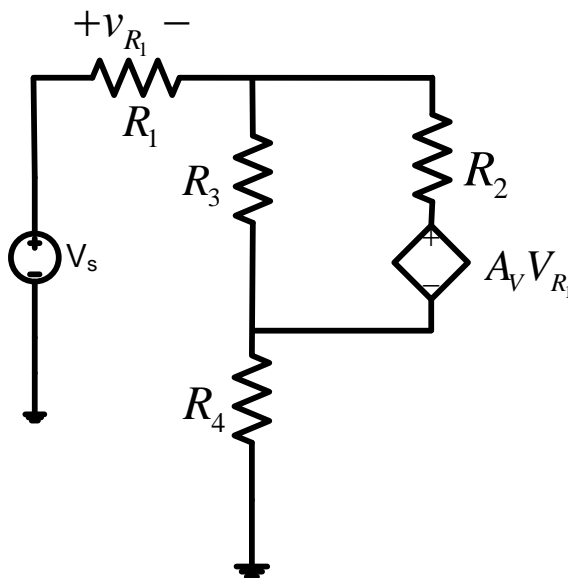


Figure 9

EE1002/CG1108 Tutorial 3

10. Determine, using superposition, the voltage v across R in the circuit of Figure 10.

$$I_B = 3A, R_B = 1\Omega, V_G = 15V, R_G = 1\Omega, R = 2\Omega$$

Ans. $v=7.2V$

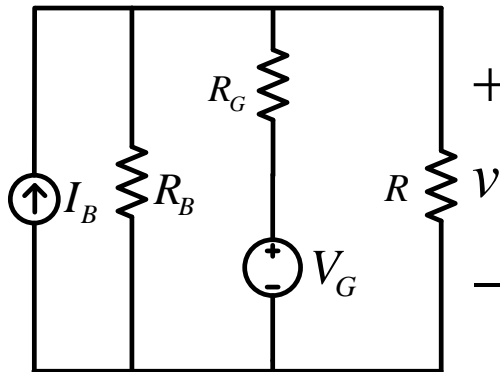


Figure 10

11. Find the Thevenin equivalent circuit that the load (R_L) sees for the circuit of Figure 11.

Ans. $V_{th}=4.499V$, $R_{th}=504\text{ ohm}$

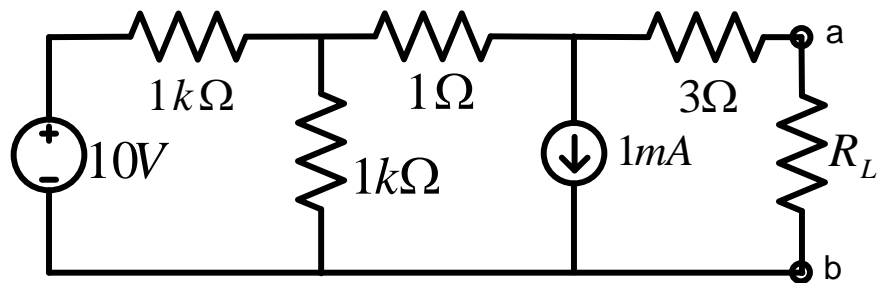


Figure 11

12. For the circuit given in Figure 12:

- i) Obtain the Thevenin's equivalent for the circuit which contains a dependent voltage source.

Ans. $V_{th}=30V$, $R_{th}=10\ \Omega$

- ii) What should be the optimum value of a load resistor R_L to be connected between a and b so that the power delivered to it by the network is maximum?

Ans. $R_L=10\ \Omega$

- iii) What is the maximum power?

Ans. $22.5W$

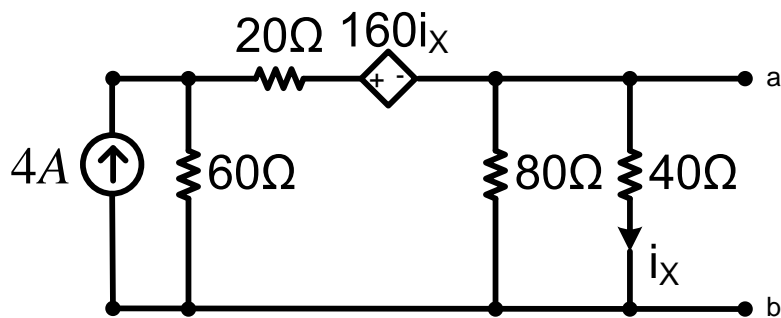


Figure 12

EE1002/CG1108 Tutorial 4

13. In the circuit of Figure 13, assume that the capacitor is initially uncharged. If the switch is closed at $t=0$,

i) Determine the current flow through the resistors and the capacitor when $t=0+$.

Ans. $i_1 = 5A, i_2 = 0A, i_3 = 5A$

ii) What will be the current flow under steady state condition?

Ans. $i_1 = i_2 = 2.5A, i_3 = 0A$

iii) Determine the voltage across the capacitor under steady state condition.

Ans. $50V$

iv) Find an expression for the capacitor voltage as a function of time $t>0$.

Ans. $50(1 - e^{-\frac{t}{20 \times 10^{-6}}})$

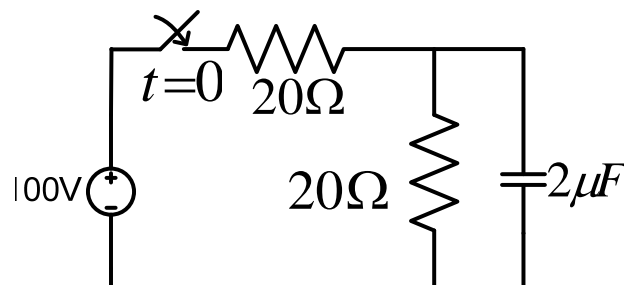


Figure 13

14. For the circuit shown in Figure 14, assume that switch S1 was closed and switch S2 was opened for a long time. Then, at time $t=0$, switch S1 is opened and switch S2 is closed.

i) Find the capacitor voltage $v_c(t)$ at $t=0+$.

Ans. $20V$

ii) Find the time constant τ for $t \geq 0$.

Ans. $56\mu s$

iii) Find an expression for $v_c(t)$, and sketch the function.

Ans. $12 + 8e^{-\frac{t}{56 \times 10^{-6}}}$

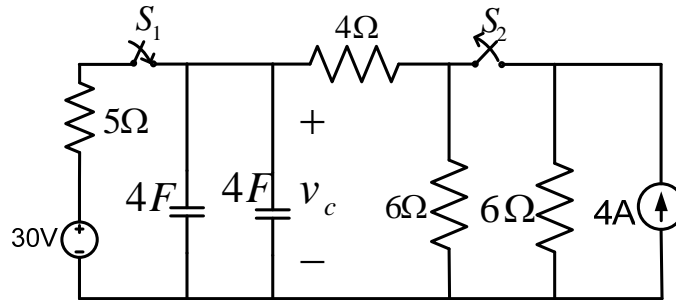


Figure 14

15. For the circuit given in Figure 15, switch S_2 was closed for a long time before $t=0$. At $t=0$, the switch S_1 is closed and S_2 is opened.

i) Find the inductor current $i(t)$ at $t=0^+$.

Ans. 2A

ii) Find the time constant τ for $t \geq 0$.

Ans. $1\mu s$

iii) Find an expression for $i(t)$.

Ans. $0.5 + 1.5e^{-\frac{t}{1 \times 10^{-6}}}$

iv) Find $i(t)$ for each of the following values, the time constant, twice the time constant, five times the time constant and ten times the time constant. Sketch the function.

Ans. $i(\tau) = 1.05A, i(2\tau) = 0.70A, i(3\tau) = 0.55A, i(5\tau) = 0.51$

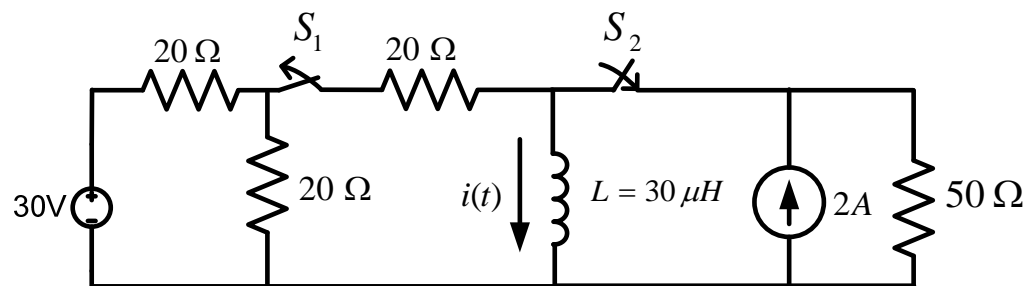


Figure 15

EE1002/CG1108 Tutorial 5

16. For the circuit in Figure 16,

- Find the expression for $v_R(t)$.
- If the sinusoidal has a frequency of 10 kHz, and the inductor is 1 mH, what is the value of R for phase difference between $v_s(t)$ and $v_R(t)$ to be 45 deg?

Ans. 62.832 ohm

- Draw the phasor diagram showing the $v_s(t)$ and $v_R(t)$ for part (ii).

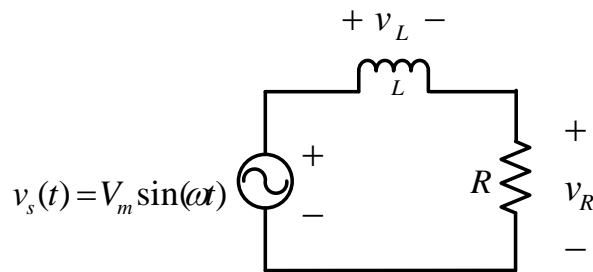


Figure 16

17. Determine the current $i(t)$ in the circuit shown in Figure 17.

$$v_s(t) = 636 \cos\left(3000t + \frac{\pi}{12}\right)$$

$$R_1 = 2.3k\Omega, R_2 = 1.1k\Omega$$

$$L = 190mH, C = 55nF$$

Ans. $i(t) = 0.2814 \cos(3000t + 22.56^\circ) A$

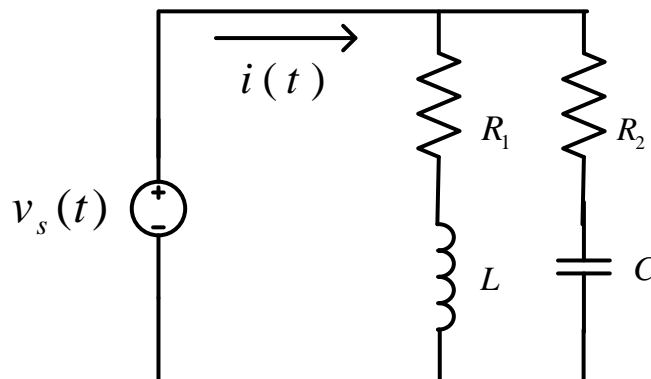


Figure 17

18. Find the Thevenin equivalent of the circuit as seen from terminals a-b for the circuit shown in Figure 18.

Ans. $V_{th} = 5\sqrt{2}\angle 15^\circ, Z_{th} = 8 - j8$

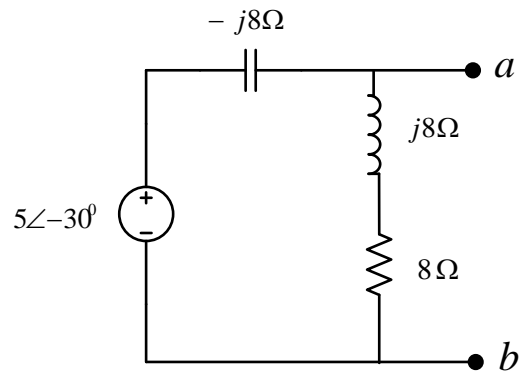


Figure 18