

# EE1002


# Introduction to Circuits and Systems

## Part 1 : Lecture 3

# Node, branch, etc. defined

- A **node** in an electrical circuit is a point at which **two or more elements are joined** together.
- A **super node is a closed surface** enclosing part of a circuit. It may contain some sources and other nodes.


# Terms of Circuit/Network Analysis

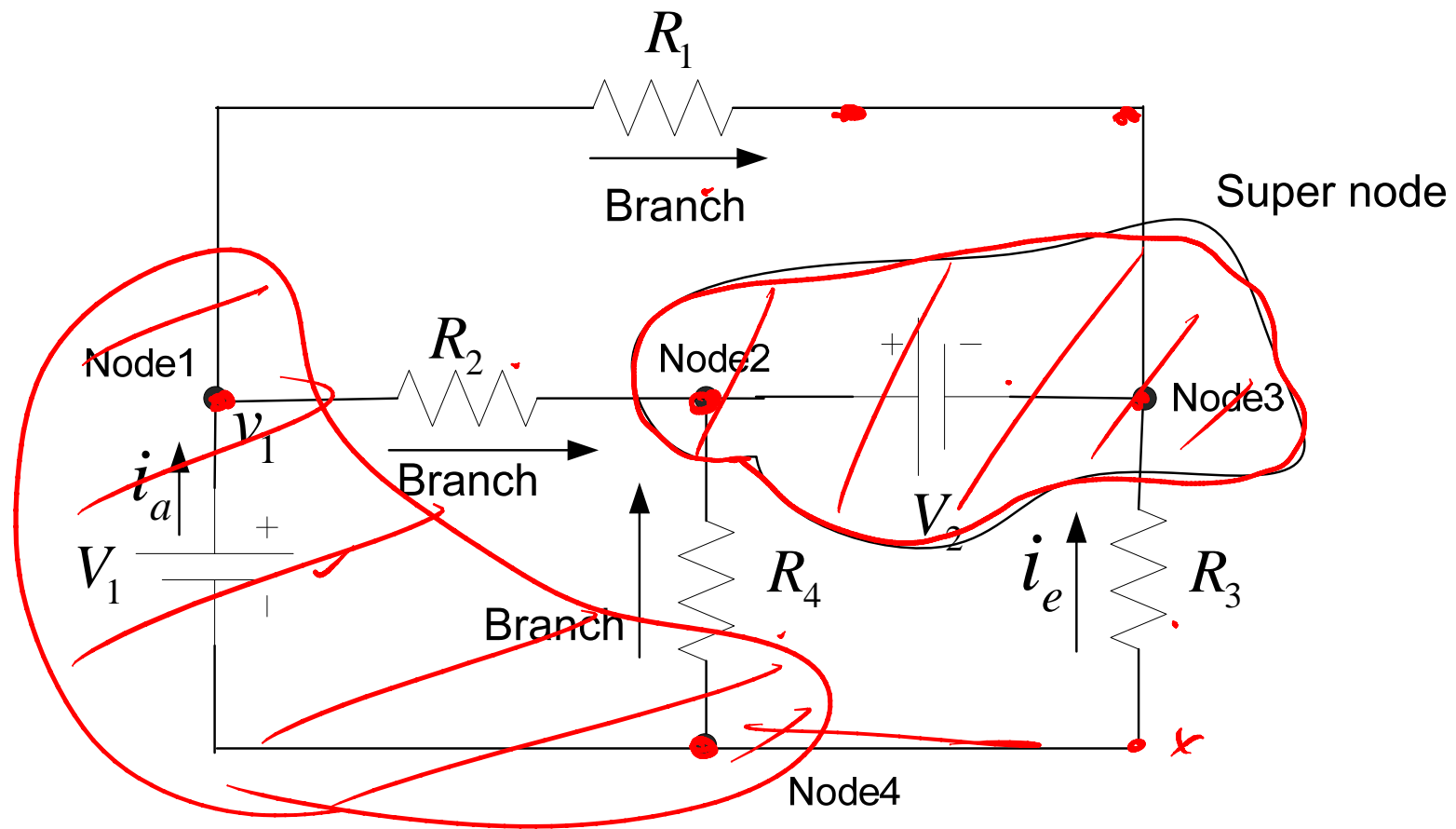

# Mesh, Loop


- A mesh is a closed path in the circuit.
- A loop is also a closed path in the circuit.
- A mesh cannot have any other mesh or loop inside it.
- A loop can have meshes inside it.

# Mesh and Loop

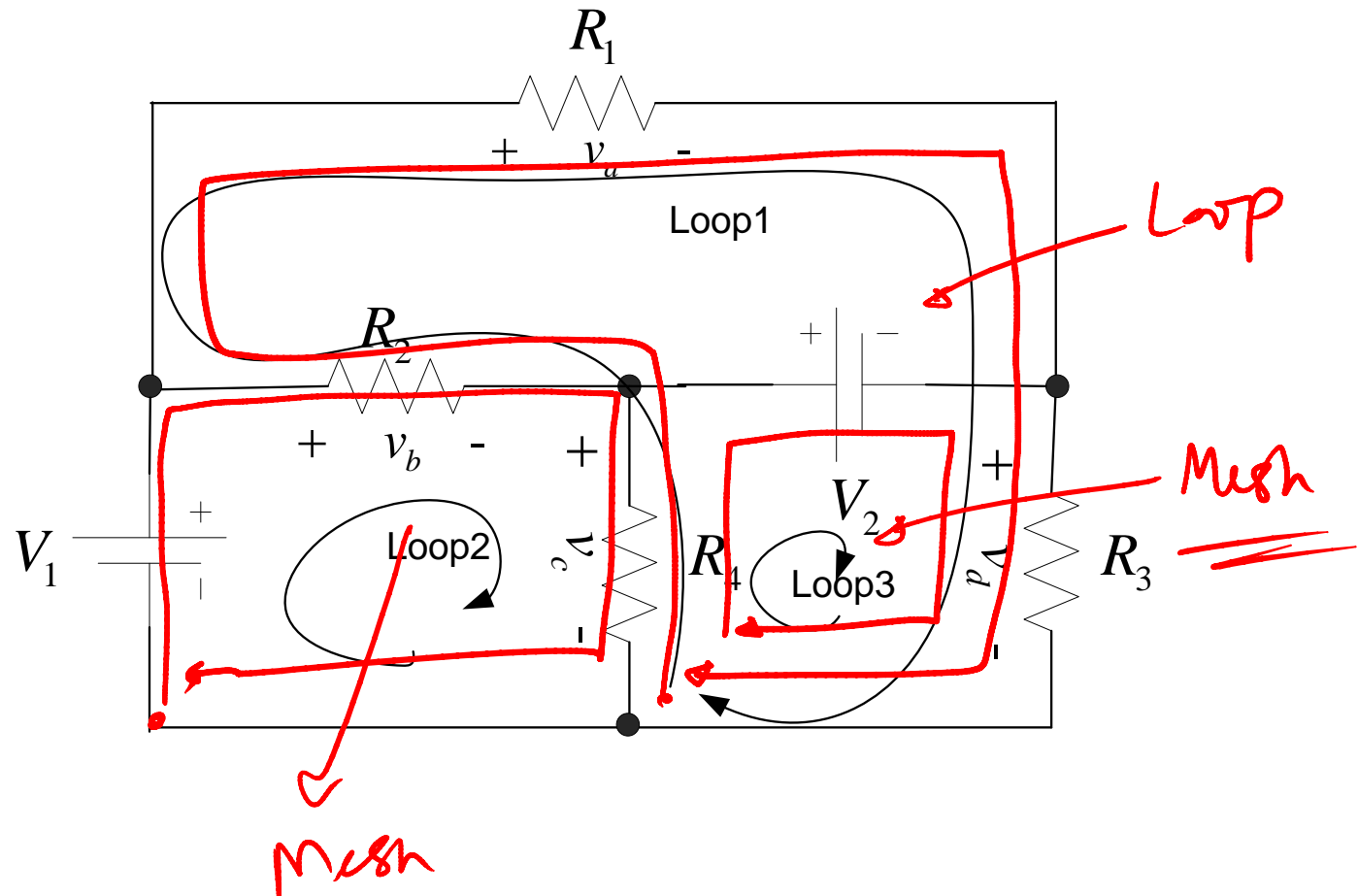
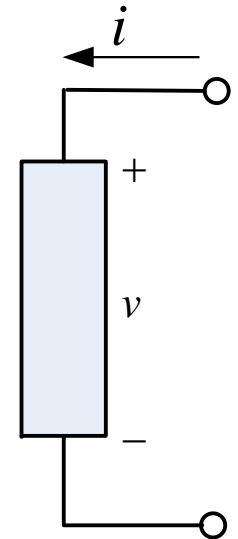
# Passive sign convention

- Reference direction (positive current direction) for current is to enter into the positive voltage terminal of the element
- If power is positive, the element is passive (dissipating energy)
- We shall follow the passive sign convention while solving circuits



# Kirchoff's Laws

# Kirchoff's Voltage Law (KVL)

- Net voltage fall around a closed path is zero
  - Voltage rises when we go from negative polarity to positive polarity
  - Voltage falls when we go from positive polarity to negative polarity
- We shall use KVL in Mesh Current Analysis Method




# Kirchoff's Current Law (KCL)

- Net current leaving a node/supernode is zero
- We shall use KCL in Node Voltage Analysis Method

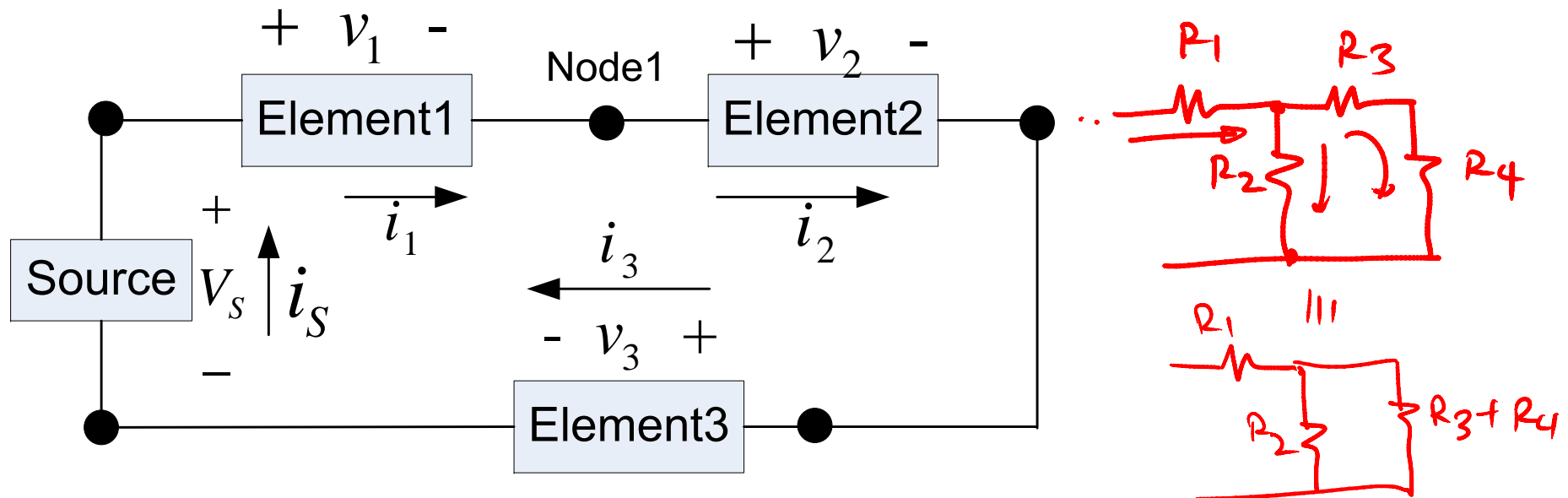
# Series Connection

- When elements are **connected end to end**
- they **carry the same current**
  - Apply KCL at any node to find this



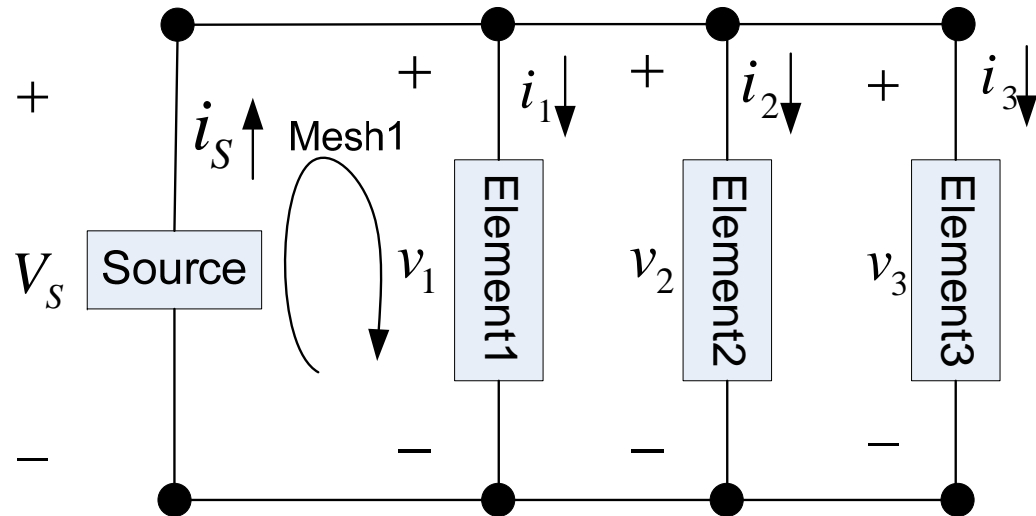
# Parallel Circuit

- If both ends of one elements are connected to the corresponding ends of the other element
- Voltages across all the elements are identical



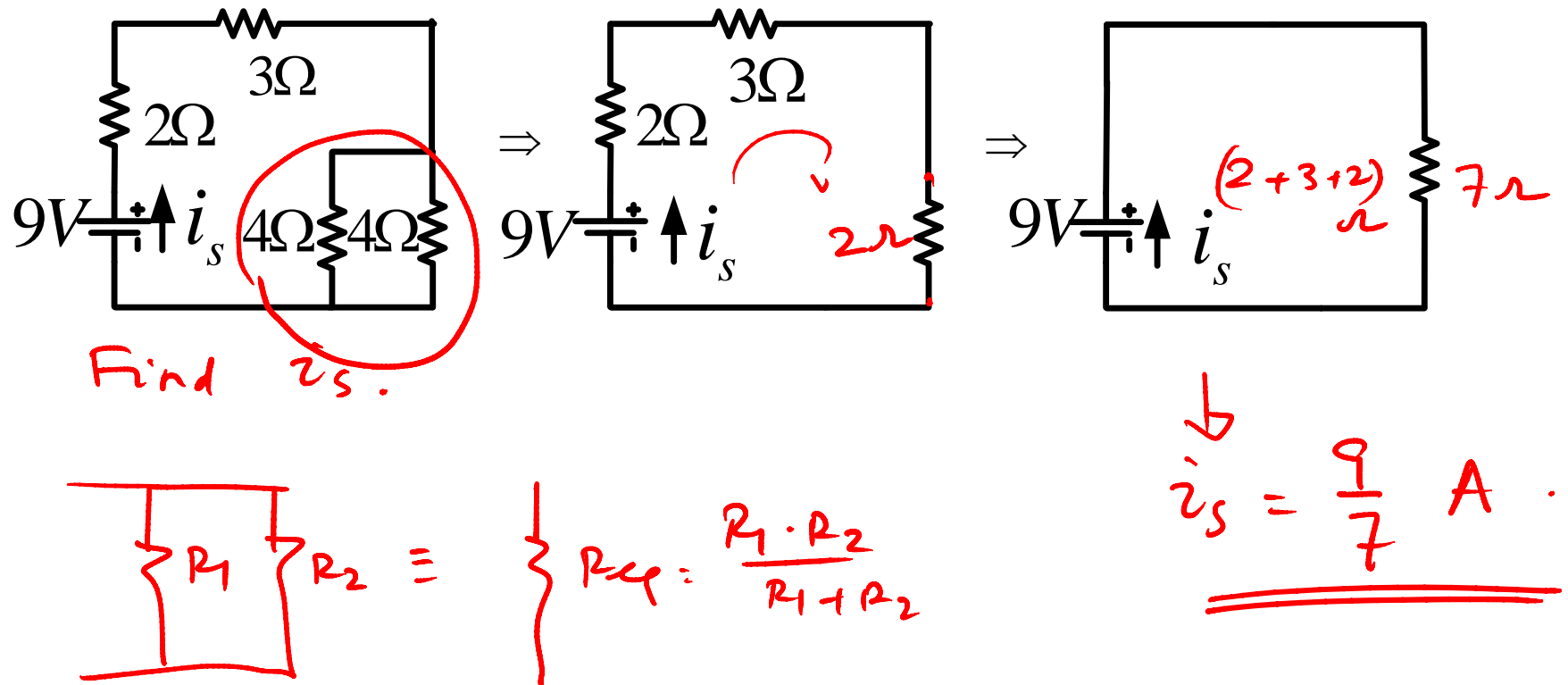
# Network analysis by series and parallel rules for resistance




- Voltage divider rule
- Current divider rule

# Voltage Divider rule

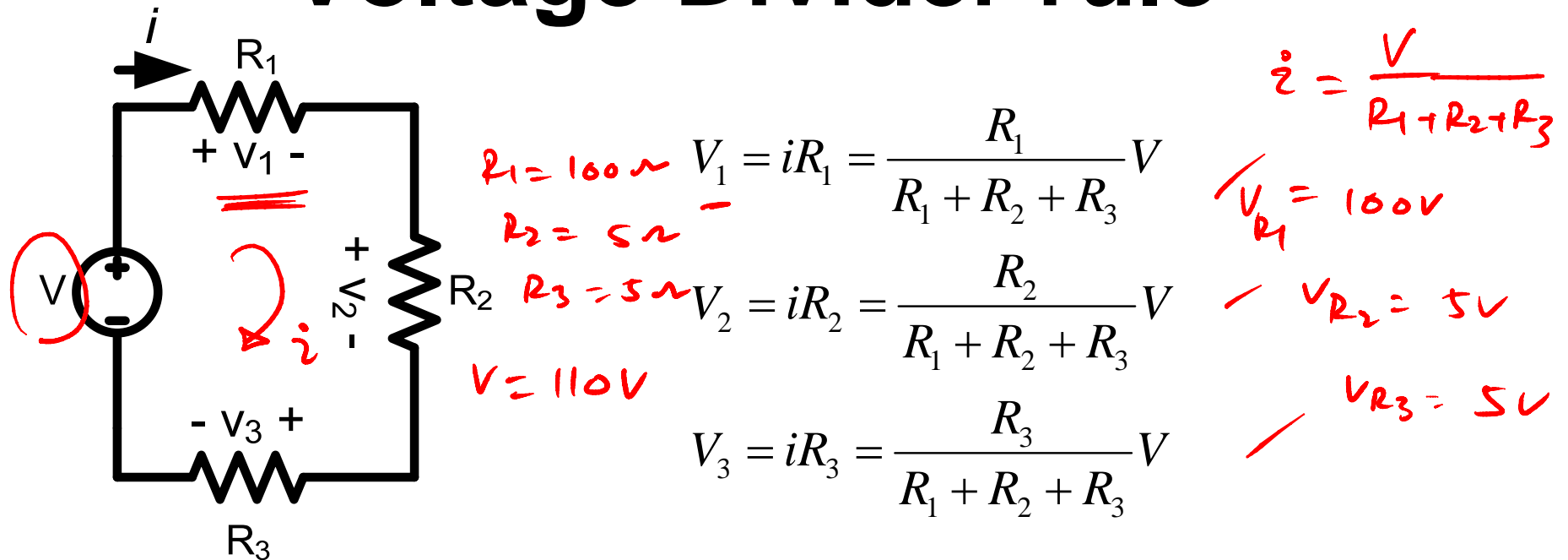



In a series circuit, the voltage across each resistance is a fraction of the total voltage, which is equal to the ratio of the concerned resistance to the total resistance.

# Current Divider Rule

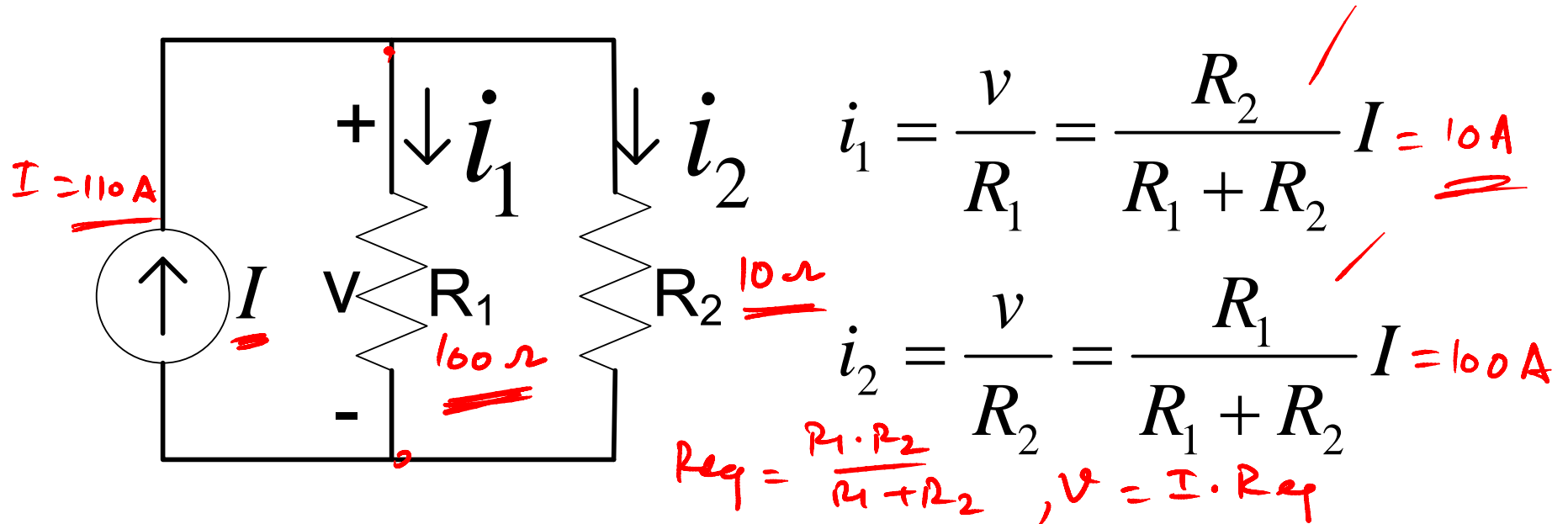

For the **two resistances in parallel**, the current flowing in each resistance is a fraction of the total current equal to the **ratio** of the **other resistor** to the **sum** of both the resistors.

# Example

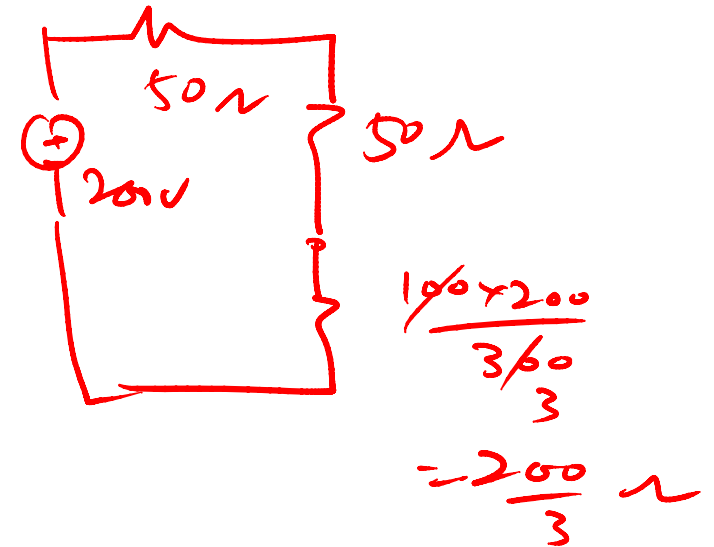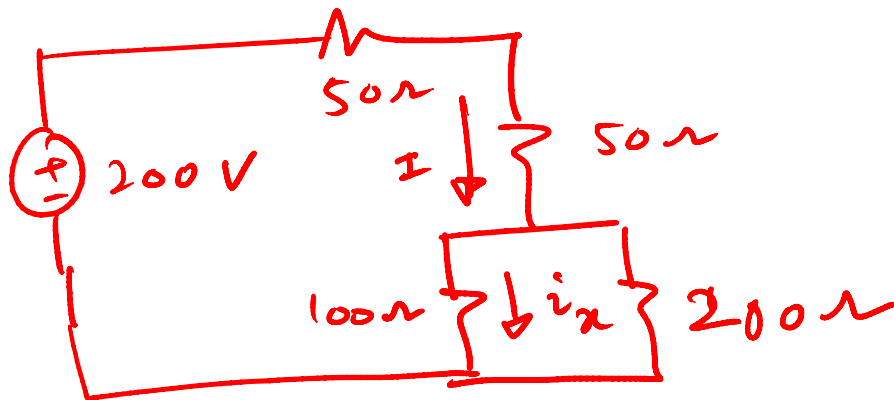

$$I = \frac{200}{50 + 50 + \frac{200}{3}} \text{ A}$$

$$i_x = I \times \frac{200}{100 + 200} \times \frac{200}{100 + \frac{200}{3}}$$




- Measuring Electrical quantities

# Measuring Devices

- Ohm meter – for resistance measurement
- ✓ Ammeter – for current measurement
- Voltmeter – for voltage measurement


✓ Multi-meter

# Ohmmeter

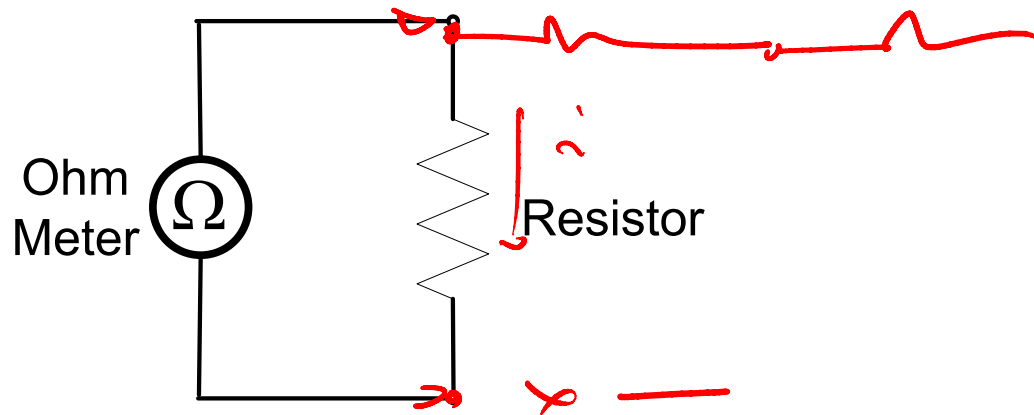

The element should be removed from the circuit when resistance is measured (at least one end of the element should be removed from the circuit and the circuit should be de-energised. )




# Ammeter

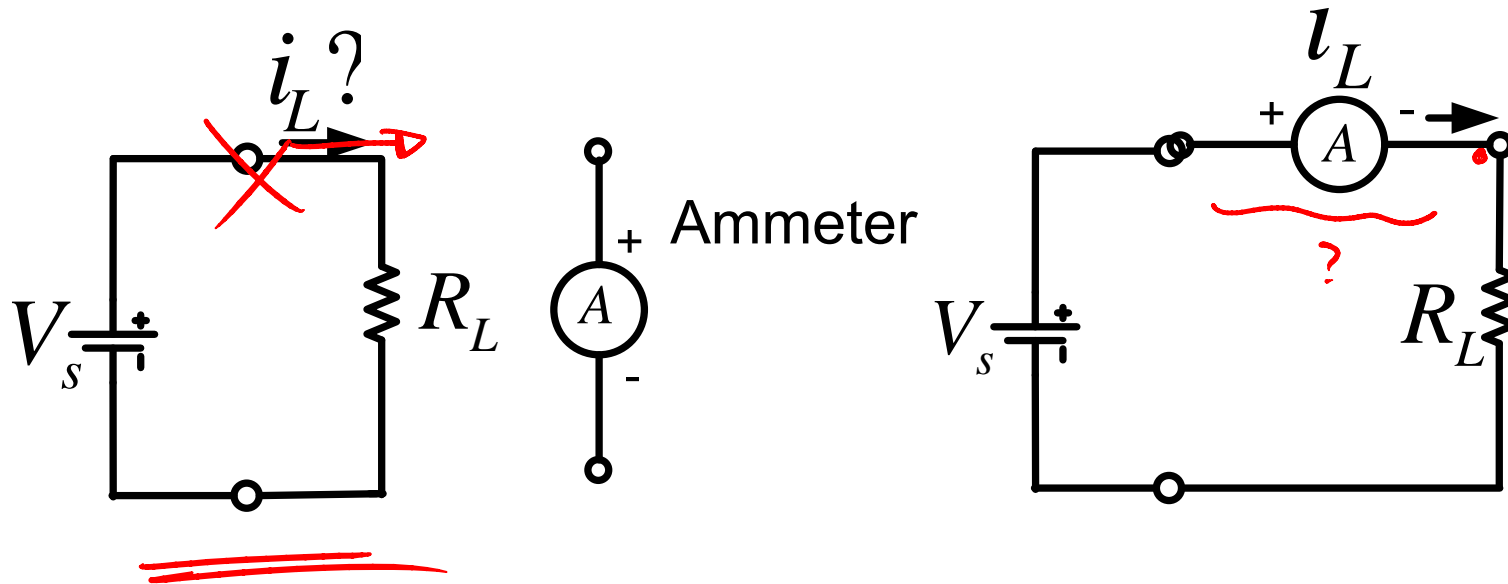

- Ammeter is **connected in series** with the element so that the same current passes through both the ammeter
- Ideal ammeter has **zero resistance**

# Voltmeter

+ve - Red  
-ve - Black

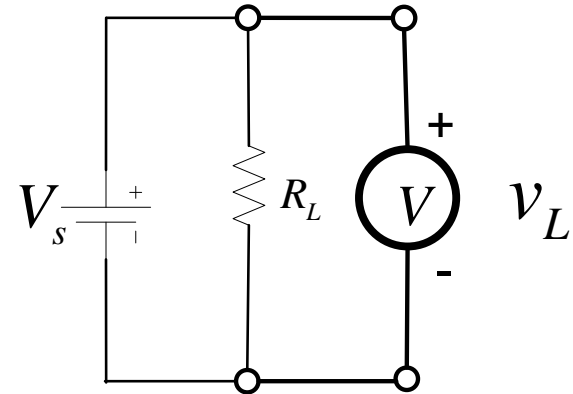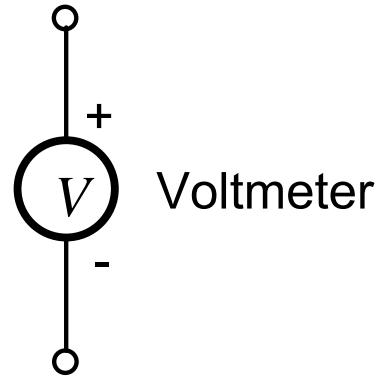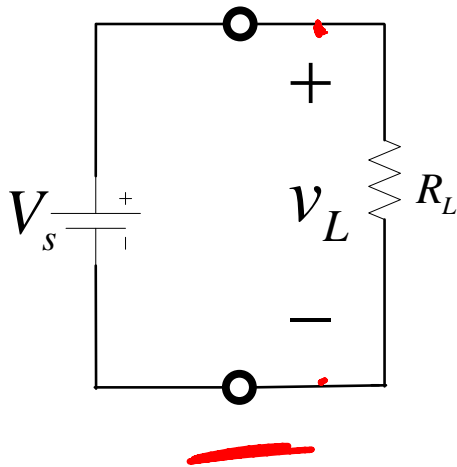


- Voltmeter is **connected in parallel** to the two points
- ideal voltmeter has **infinite resistance**

# Node Voltage Analysis

# Mesh Current Analysis

\_\_\_\_\_

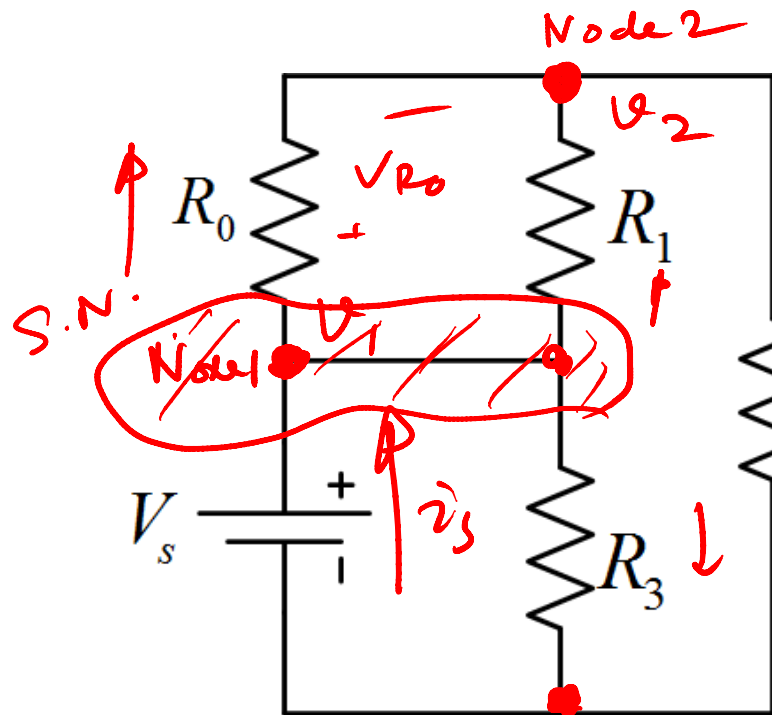

$$1) \quad V_1 - V_2 = V_{R_0}$$

$$(V_1 - V_{ref}) - (V_2 - V_{ref})$$

$$= V_1 - V_2$$


$$I_{R_2} = \frac{\text{voltage across } R_2}{R_2}$$

$$= \frac{(V_2 - V_{ref}) - 0}{R_2}$$

$$) \quad V \text{ Ground (GND)} = \frac{V_2}{R_2}$$

- If voltage at all the nodes are known, then all the voltages and currents can be obtained -

# Intro to mesh current Analysis

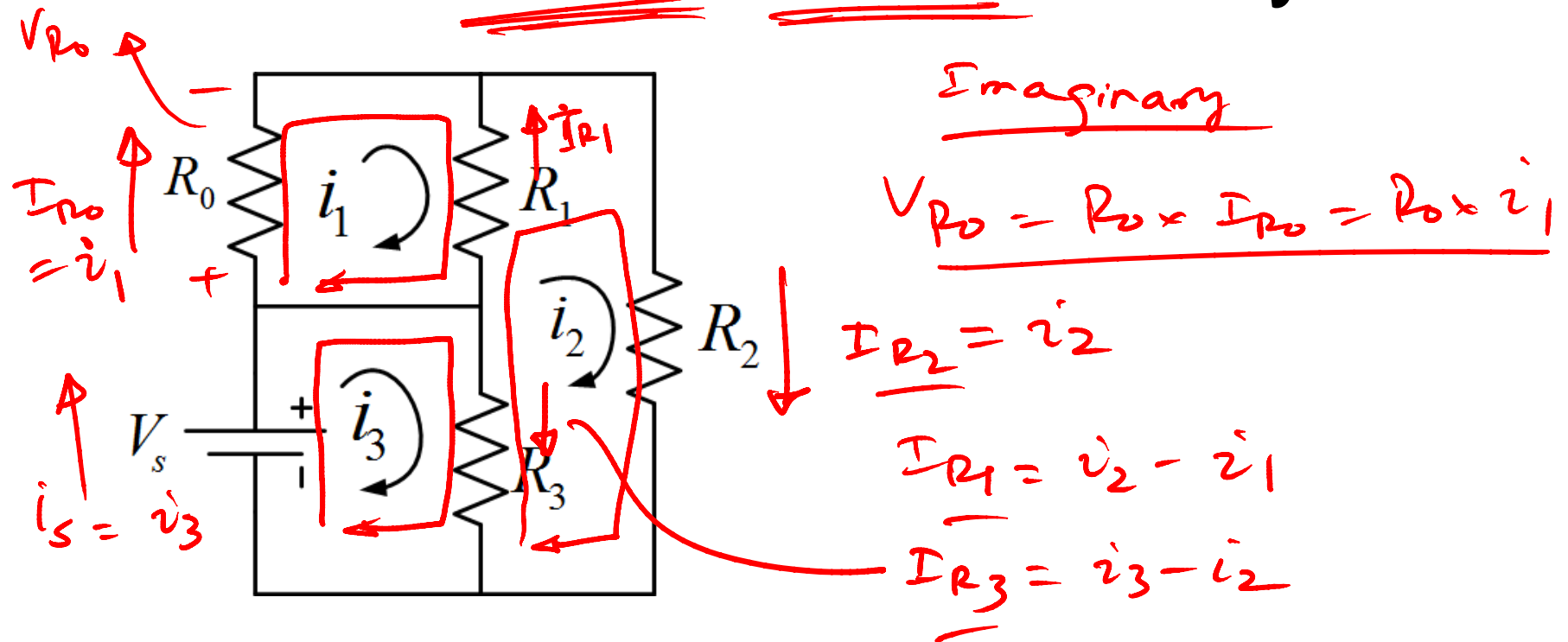

- If currents in the meshes are known, then all the other currents and voltages can be obtained.



# Steps of Node Voltage Analysis method

1. Select a reference node (Usually the ground of a voltage source.)
2. For each voltage source connected to the reference node, the other end is a known constant.   
*Handwritten note: -ve of voltage source as ref.*
3. For all other voltage sources, one end is tied to the other. So only one unknown variable for each such voltage source.




# Steps of Node Voltage Analysis method

4. Define the remaining node voltages as unknown variables.


5. Apply KCL at the nodes to obtain as many equations as the number of unknown variables.

6. Express each current in a resistive branch in terms of the adjacent node voltages.

7. Solve the linear system of equations.

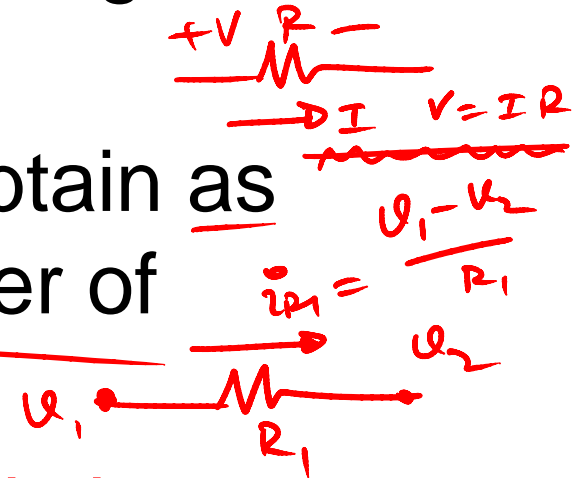
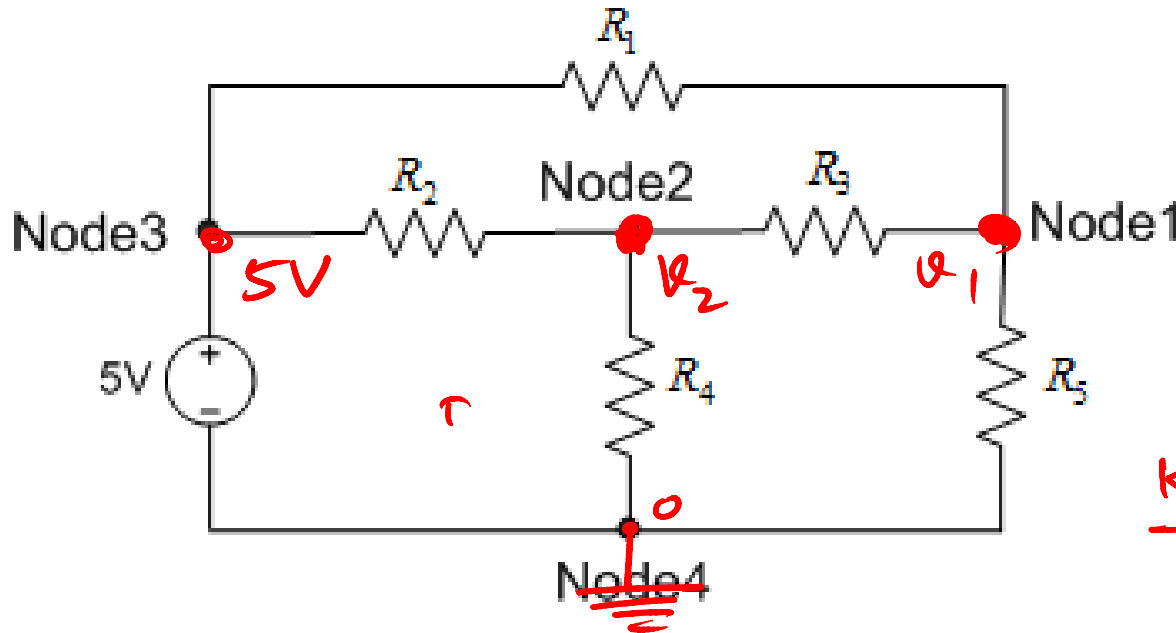
# Case 1: Node analysis with one Ideal Voltage Source



KCL at node 1

$$\frac{V_1 - 5}{R_1} + \frac{V_1 - V_2}{R_3} + \frac{V_1}{R_5}$$

KCL at node 2

$$= 0$$


①

$$\frac{V_2 - 5}{R_2} + \frac{V_2 - V_1}{R_3} + \frac{V_2}{R_4} = 0$$

②

- Choose reference node (GND)
- Identify unknown node voltages as variables
- Express each current in a resistive branch in terms of the adjacent node voltages.
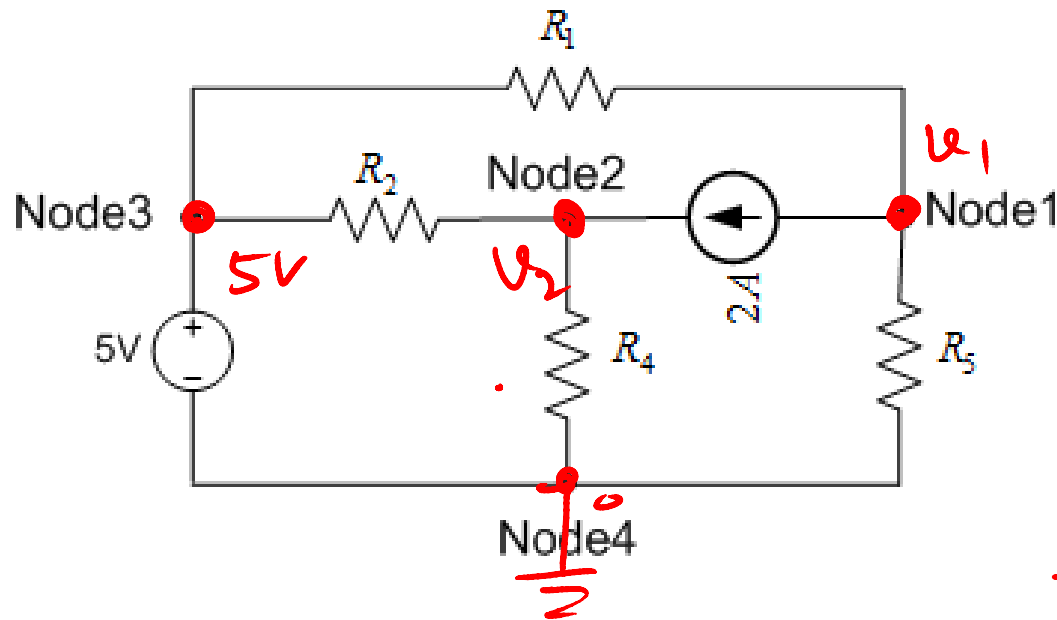
# Case 2: Having an additional Ideal Current source in the circuit




KCL at node 1

$$\frac{v_1 - 5}{R_1} + \frac{v_1}{R_5} + 2 = 0 \quad \text{--- (1)}$$

KCL at node 2

$$\frac{v_2 - 5}{R_2} + \frac{v_2}{R_4} - 2 = 0 \quad \text{--- (2)}$$
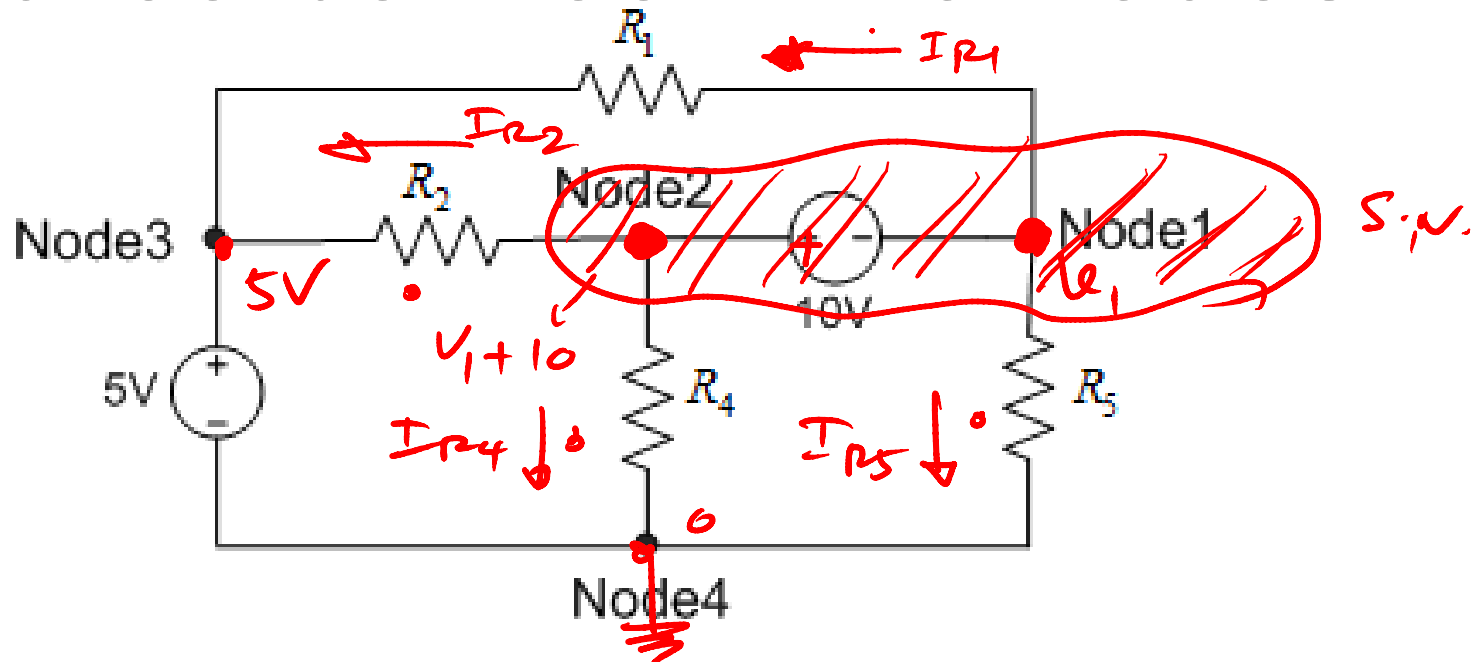
# Case 3: With an Ideal Voltage source between two nodes



- Out of the two nodes across the voltage source, only one node voltage is an unknown variable.

$$\frac{V_1 - 5}{R_1} + \frac{V_1 + 10 - 5}{R_2} + \frac{V_1 + 10}{R_4} + \frac{V_1}{R_5} = 0 \quad \text{--- (1)}$$