

EE1002

Introduction to Circuits and Systems


Part 1 : Lecture 5

Superposition Principle

Equivalent Circuits

Example 1

Find the currents shown in the circuit.

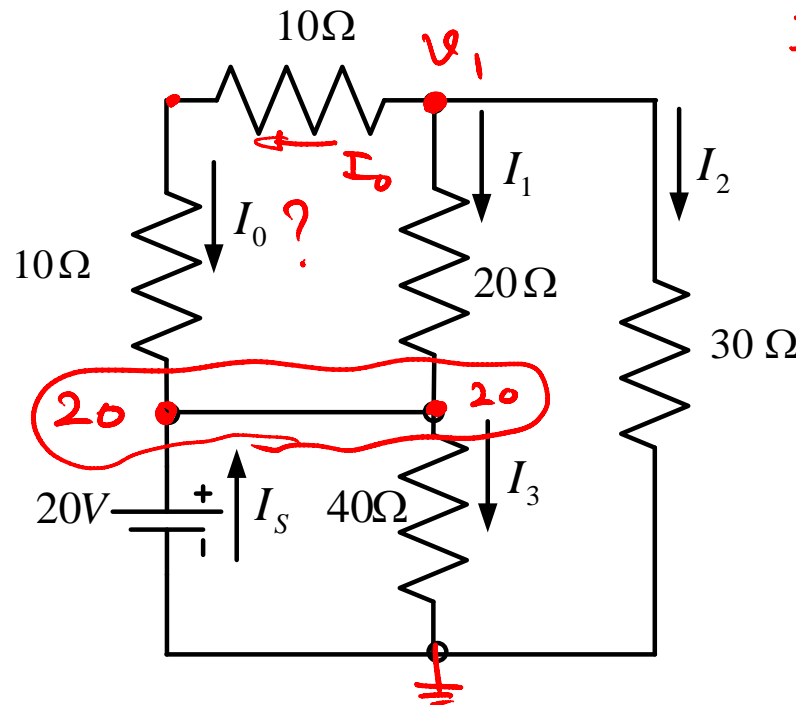

KCL at S.N.

$$-I_S - I_0 - I_1 + I_3 = 0$$

$$I_0 = \frac{V_1 - 20}{10 + 10}$$

KCL at node V_1 :

$$\frac{V_1 - 20}{20} + \frac{V_1 - 20}{20} + \frac{V_1}{30} = 0$$

$$3V_1 - 60 + 3V_1 - 60 + 2V_1 = 0$$

$$8V_1 = 120 \Rightarrow V_1 = 15 \text{ V}$$

$$I_0 = \frac{15 - 20}{20} = -0.25 \text{ A}$$


$$I_1 = \frac{15 - 20}{20} = -0.25 \text{ A}$$

$$I_2 = \frac{15}{30} = 0.5 \text{ A}$$

$$I_3 = \frac{20}{40} = 0.5 \text{ A}$$

$$\Rightarrow I_3 = -I_0 - I_1 + I_2 = 0.25 + 0.25 + 0.5 = 1 \text{ A}$$

Example 2

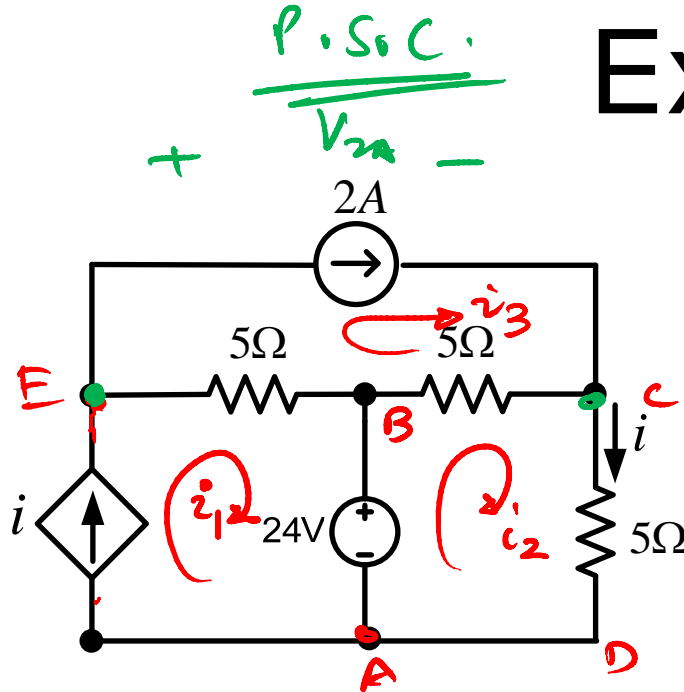

(absorbed)

$$P_{2A} = V_{2A} \times 2 = 14 \times 2 = \underline{\underline{28W}}$$

Use **Mesh Current Analysis** to find the **power associated with the 2A current source** in the circuit in Figure Q2. Is the power **delivered or absorbed** by the current source?

Mesh i_1 : $i_1 = i_2$ — ①

Mesh i_2 : AB CDA

KVL: $-24 + 5 \times (i_2 - i_3) + 5 \times i_2 = 0$

② $\Rightarrow -24 + 5(i_2 - 2) + 5i_2 = 0$ — ②

Mesh i_3 :

$i_3 = 2A$ — ③

$\Rightarrow i_2 = 3.4A$
 $= i_1$

V_{EC} = Find a path from E to C and add all voltage drops along the path

$$\begin{aligned} &= 5 \times (i_1 - i_3) + 5(i_2 - i_3) \\ &= 5(3.4 - 2) + 5(3.4 - 2) \\ &= 14V \end{aligned}$$

The principle of Superposition

- The total response in a linear circuit is the sum of responses to each of the independent sources acting individually.

$$r_T = r_1 + r_2 + \dots + r_N$$

r_T - total response

*Circuit has
N sources.*

r_n - the response due to the n^{th} source,
acting individually.

$y = mx + c$? **Linearity**

Ans: No

① $f(x_1 + x_2) = f(x_1) + f(x_2)$ Additivity

② $f(\alpha \times x) = \alpha \times f(x)$

Homogeneity

$$y = kx$$

$$y(x_1) = k \cdot x_1$$

$$y(x_2) = k \cdot x_2$$

$$v = f(i)$$

$$v = R \cdot i$$

$$i = \frac{1}{R} \cdot v$$

①

$$\begin{aligned} y(x_1 + x_2) &= k \cdot (x_1 + x_2) \\ &= kx_1 + kx_2 \\ &= y(x_1) + y(x_2) \end{aligned}$$

- Resistor, inductor, capacitor are linear elements.

②

$$\begin{aligned} y(\alpha \cdot x) &= k \cdot \alpha x \\ &= \alpha \cdot kx \end{aligned}$$


- Diode, MOSFET are nonlinear elements.

Superposition to solve circuits

- ‘Kill’ all the other **independent sources** but one. **DO NOT kill dependent sources.**
- This should result in a simpler circuit
- Use network analysis to find the required response (voltage/current)
- Do this one by one for all independent sources
- Add up the responses to find the total response


Killing a voltage source

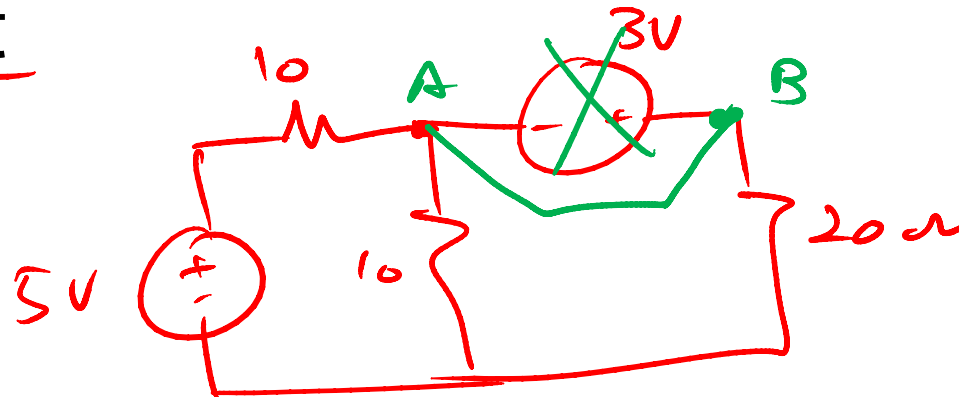- To kill a voltage source, we make its output voltage equal to zero.
- Replace the voltage source with a short circuit




Killing a current source

- To kill a current source, we make its output current equal to zero.
- replace the current source with an open circuit

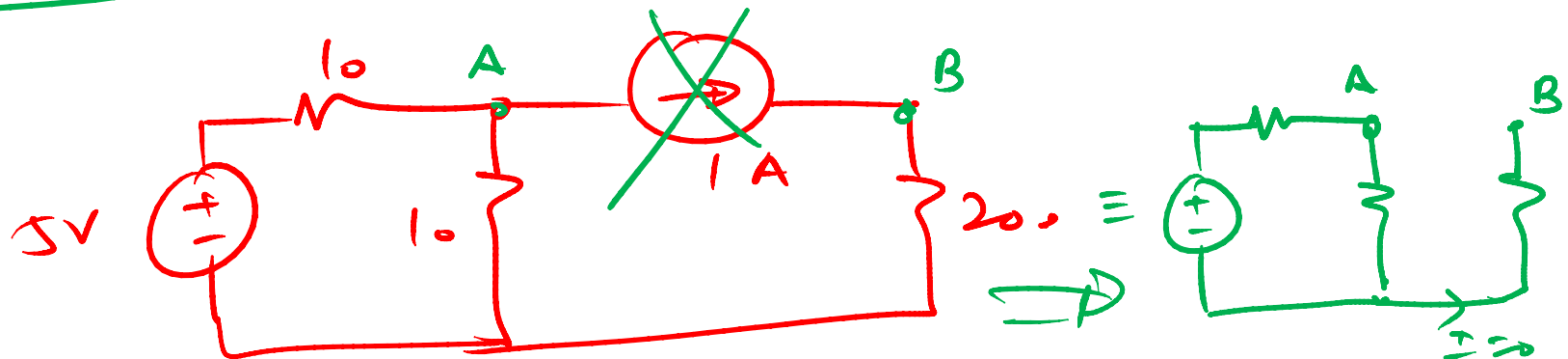

Example 1

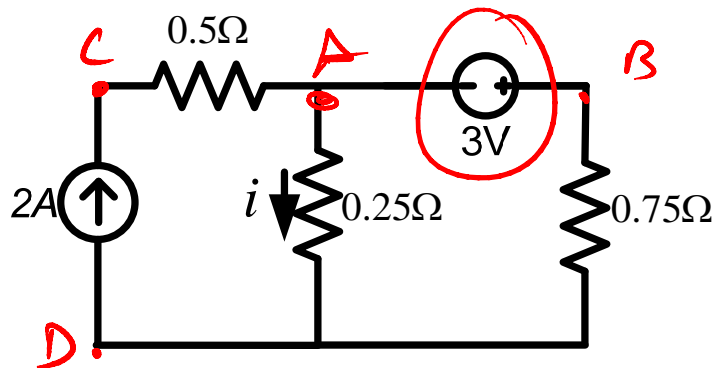


Circuit with two independent sources


$$i_1 = 2 \times \frac{0.75}{0.25 + 0.75} = 1.5 \text{ A}$$

$$i_2 = -\frac{3}{0.25 + 0.75} = -3 \text{ A}$$
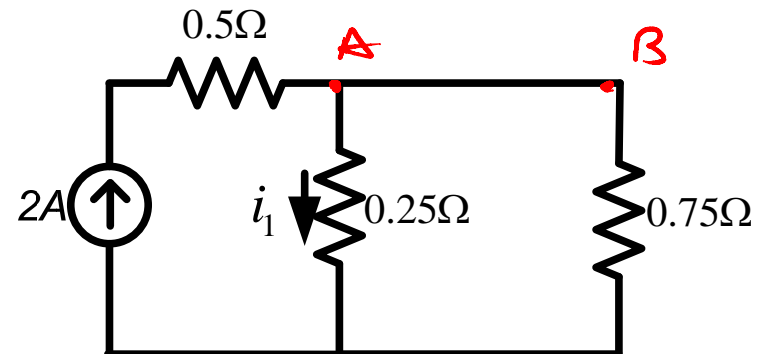
$$i = i_1 + i_2 = 1.5 - 3 = \underline{\underline{-1.5 \text{ A}}}$$





Circuit with only the current source

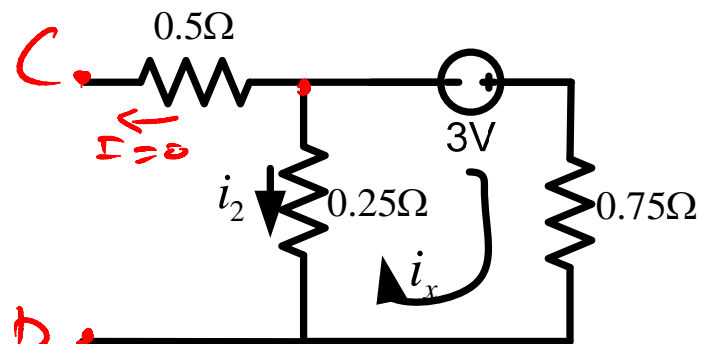


Circuit with only the voltage source

Example 2

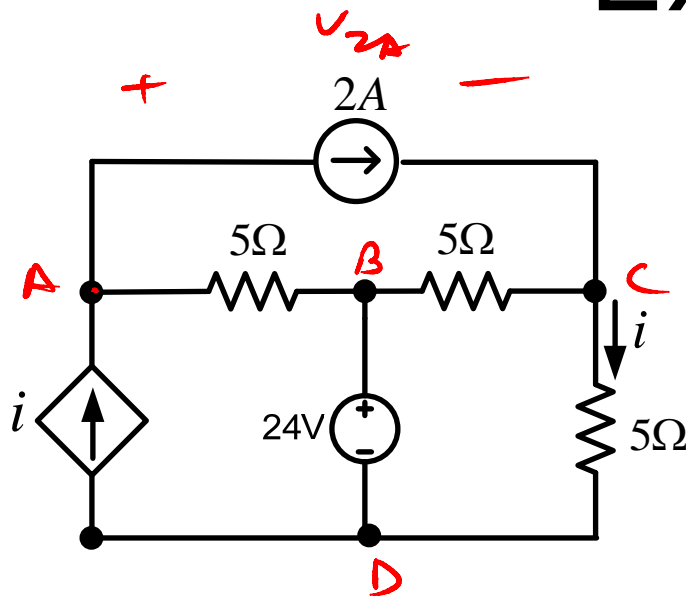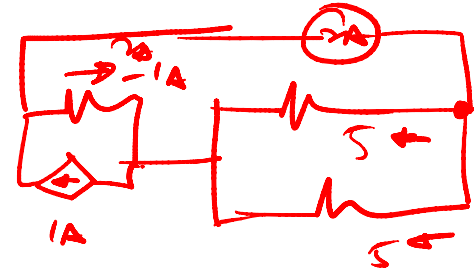

Use Superposition principle to find the power associated with the 2A current source in the circuit in Figure Q2. Is the power delivered or absorbed by the current source?

Kill the current source.

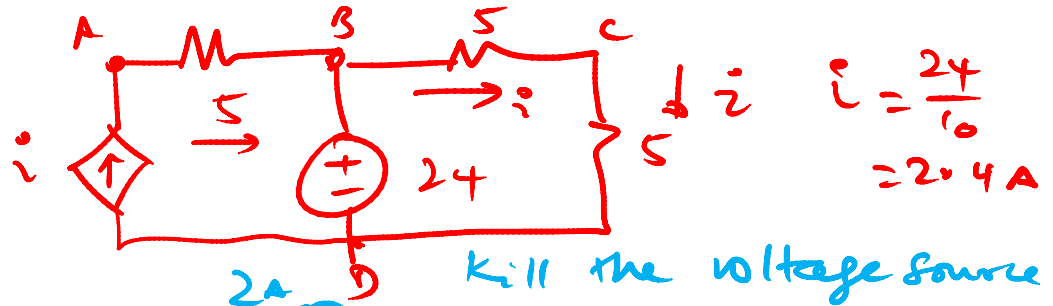


$$i = \frac{24}{10} = 2.4 \text{ A}$$

$$\begin{aligned} V_{2A1} &= V_{AC} \\ &= 5 \times 2.4 + 5 \times 2.4 \\ &= 24 \text{ V.} \end{aligned}$$

$$\begin{aligned} V_{2A2} &= 5 \times (-i) + 5 \times (-i) \\ &= -10 \text{ V.} \end{aligned}$$

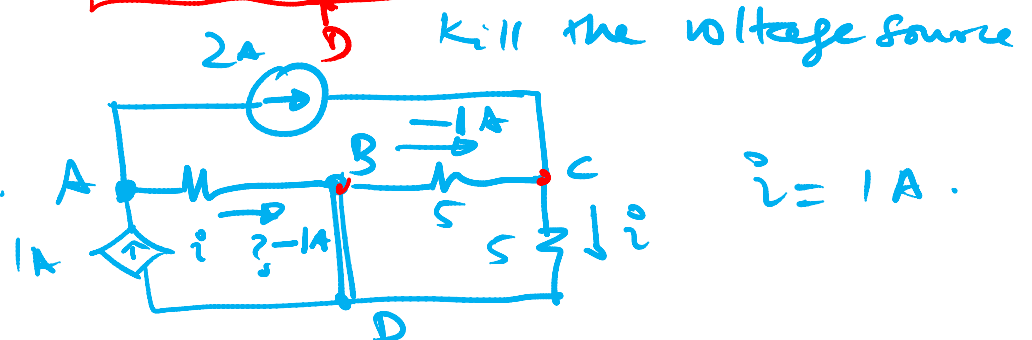
$$\begin{aligned} V_{2A} &= V_{2A1} + V_{2A2} \\ &= 14 \text{ V.} \end{aligned}$$



$$i = 1 \text{ A.}$$

Equivalent Circuits

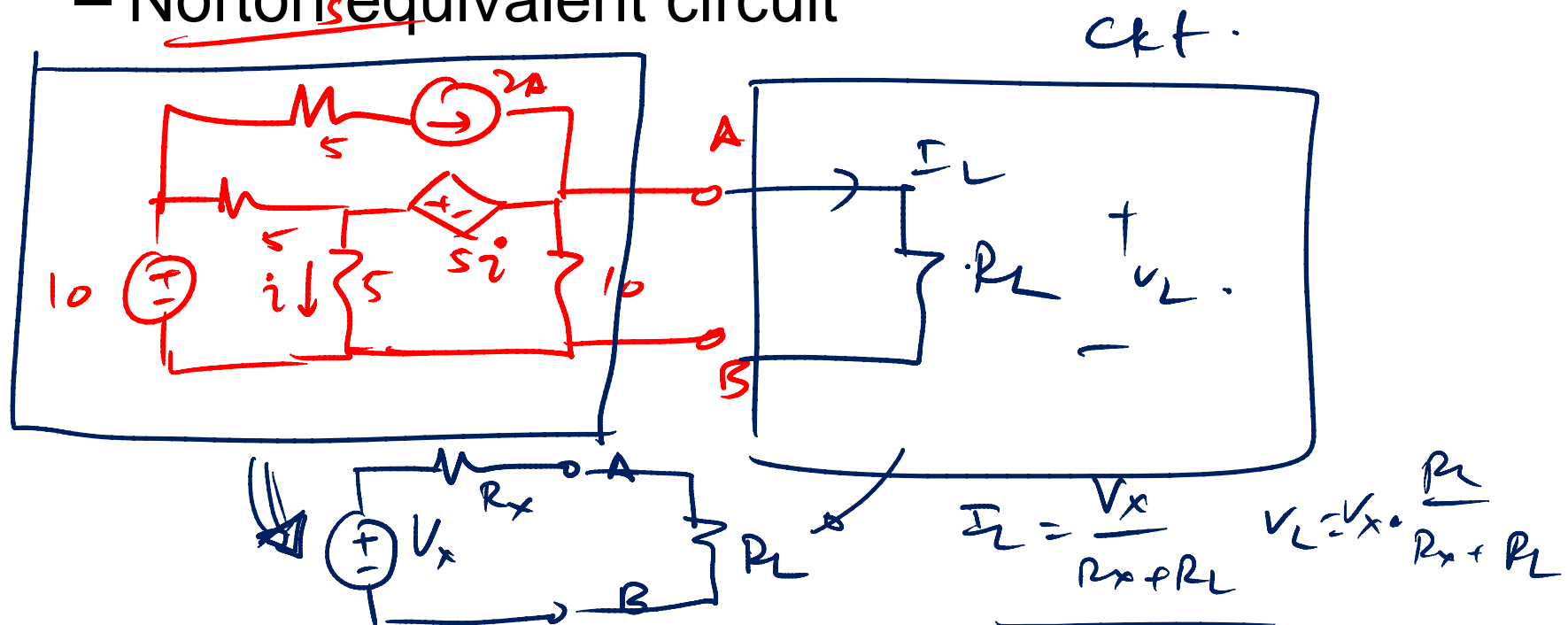
- One-port networks and equivalent circuits
 - Thevenin's equivalent circuit
 - Norton's equivalent circuit



One-port networks and equivalent circuits

- Two-terminal circuits can be replaced by an **equivalent circuit** consisting of a source and a resistance.
- A voltage source with a series resistance (Thevenin equivalent circuit)
- A current source with a parallel resistance (Norton equivalent circuit)


Thevenin equivalent

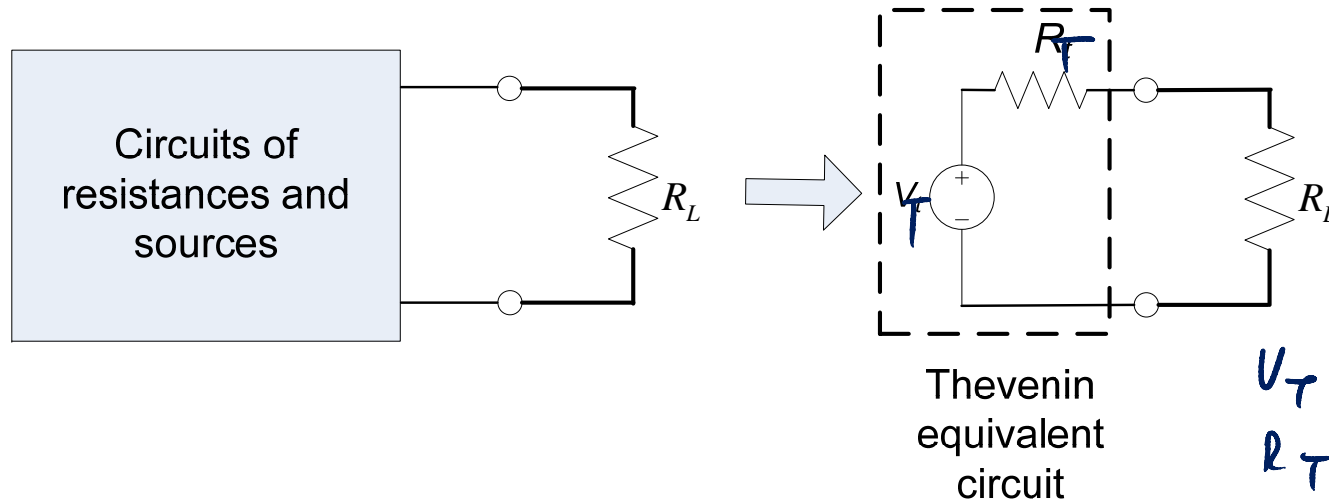

- A voltage source in series with a resistance
- The voltage source is called Thevenin's voltage
- The series resistance is called Thevenin's resistance


Thevenin Voltage

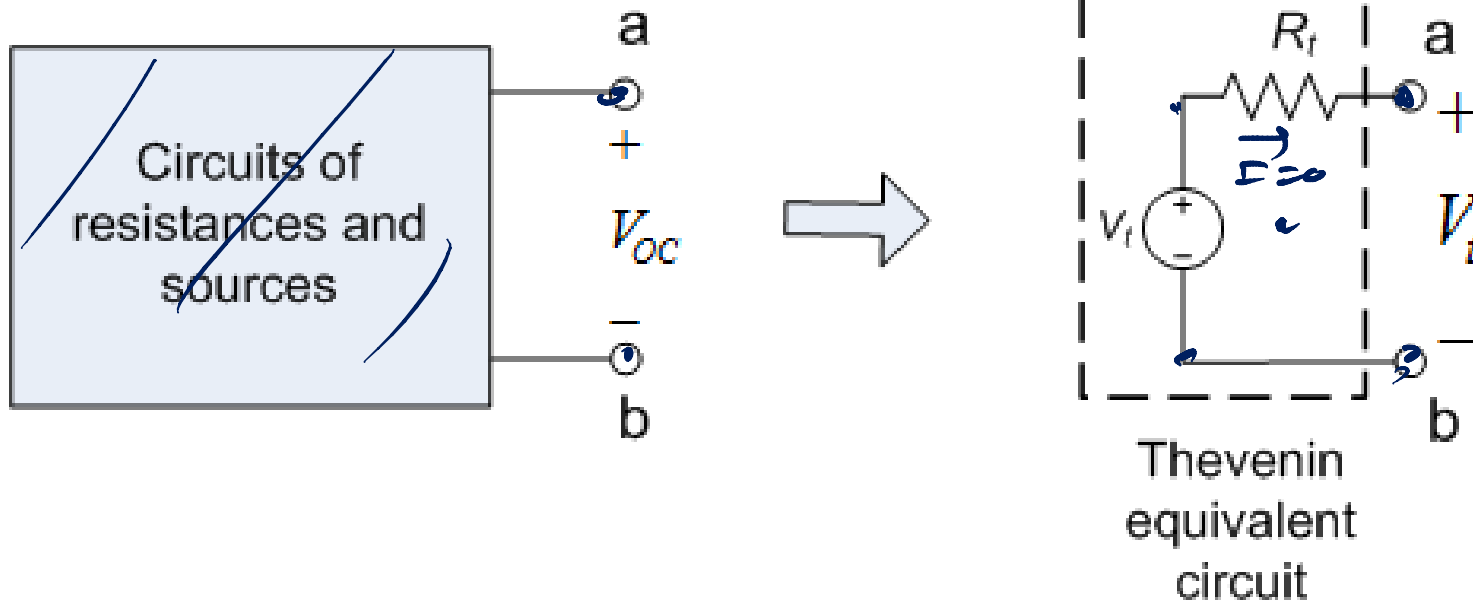- Value of the voltage source is the open circuit voltage between the two terminals
- Called the Thevenin voltage




Thevenin Resistance

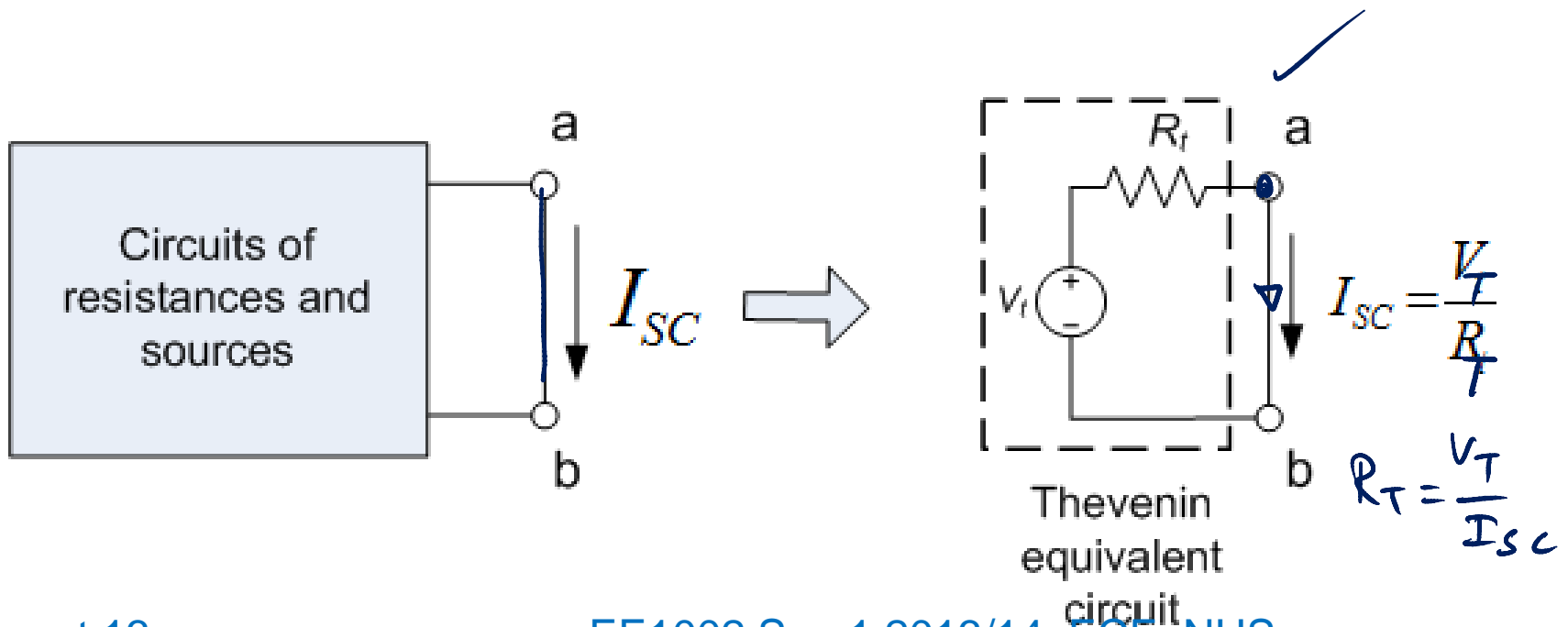- Find the **short circuit current** between the two terminals
- Calculate the Thevenin resistance



Norton Equivalent

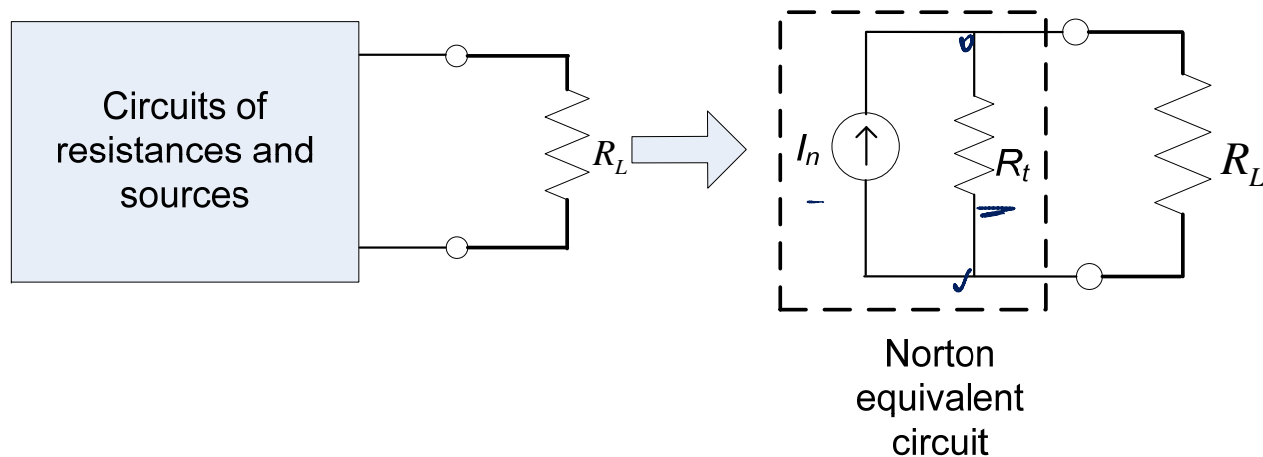


- A current source in parallel with a resistance
- The current source is called Norton's current
- The series resistance is called Thevenin's resistance

Norton's current

- Value of the current source is the **short circuit current** between the two terminals
- Called the Norton's current




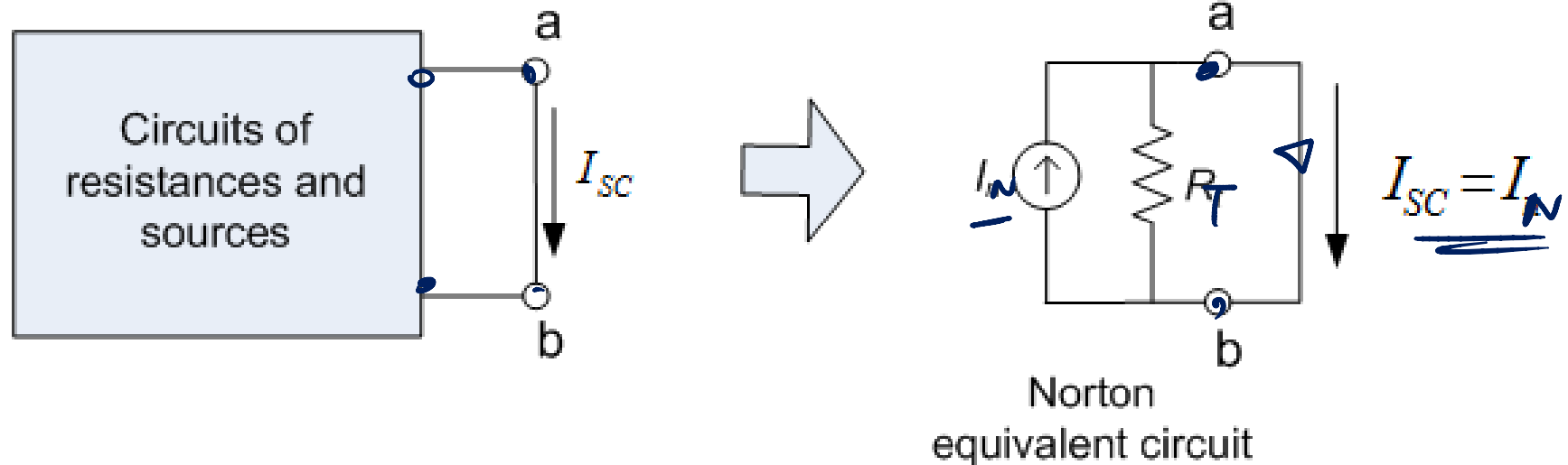
$$I_{SC} = I_N \times \frac{R_T}{R_T + 0}$$



Steps to find the equivalent circuits

- Obtain the open circuit voltage between the two terminals – Thevenin's voltage
- Obtain the short circuit current between the two terminals – Norton's current
- Calculate the Thevenin's resistance as
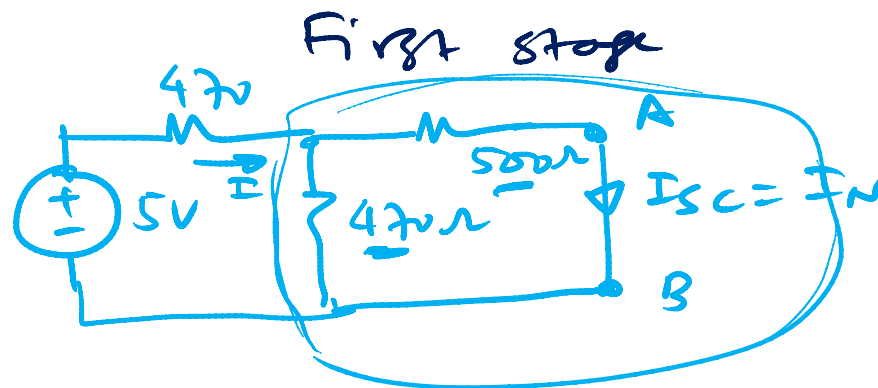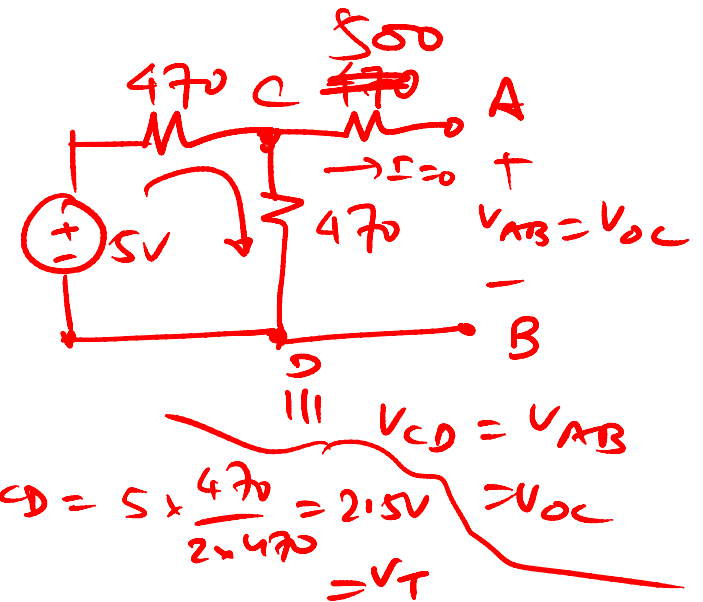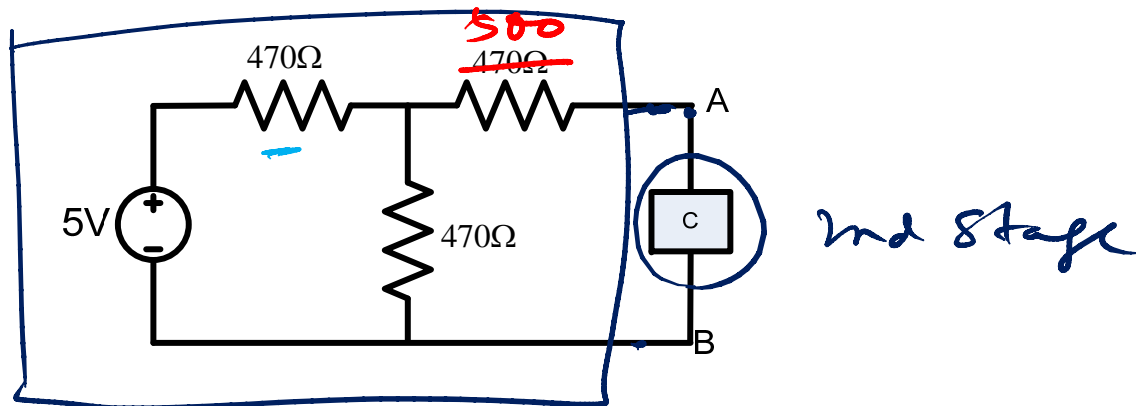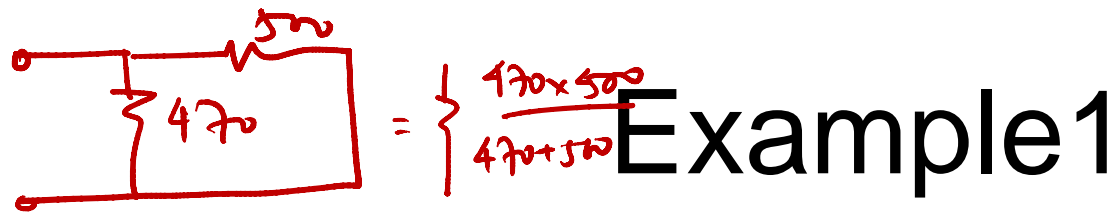
$$R_T = \frac{V_{OC}}{I_{SC}} \quad \checkmark$$



$$I = \frac{5}{470 + \frac{470 \times 500}{470 + 500}}$$

$$I_{SC} = I \times \frac{470}{470 + 500} \quad A = I_N$$

To find open circuit voltage and short circuit current of the circuit

$$R_T = \frac{V_{OC}}{I_{SC}} = \frac{V_T}{I_N}$$

Example2

To find open circuit voltage and short circuit current of the circuit.

