

EE1002

Introduction to Circuits and Systems

Part 1 : Lecture 2

Announcement


- LT Spice lab next week
- Safety Quiz:
 - <http://my.ece.nus.edu.sg/safety/quiz/>
 - Need to take this online quiz, pass it and submit the printed passing certificate when you come for lab 2.
 - It is a must to be able to work in the lab.

Rules for the lab

- Proper Attire
 - No flip-flop allowed
 - Covered-toe shoes only allowed
- Do not put water bottles on working tables
- Be punctual else you will miss the briefing

Current

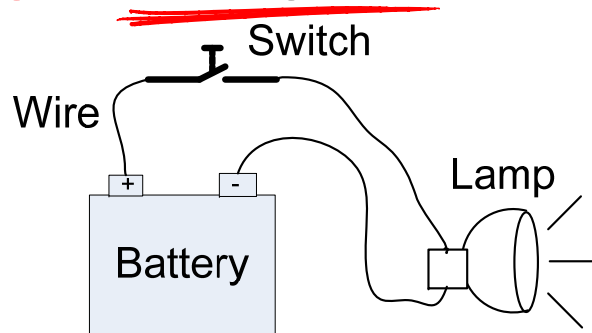
- Electric current is the time **rate of flow of electrical charge** through an element



$$i(t) = \frac{dq(t)}{dt}$$

$$V_{AB} = V_A - V_B$$

$$q(t) = q(t_0) + \int_{t_0}^t i(t) dt$$

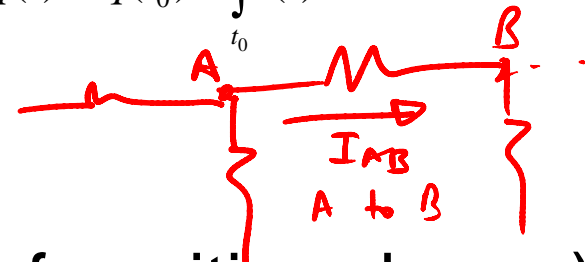

- Unit – Ampere, symbol - /
- Current has a **direction** (that of positive charge)
- DC – direct current (unidirectional)
- AC – alternating current (bidirectional and periodic)

Voltage



- Voltage is electrical potential difference (is a measure of the energy transferred per unit charge between two points).
- Unit – Volt, symbol - V
- Energy can be gained or lost, thus voltage has polarity: positive and negative
 - $V_{ab} = -V_{ba}$

$$V_{ab} = P_a - P_b \\ = V_a - V_b$$

Review of Lec 1



- Voltage Source

- Current Source

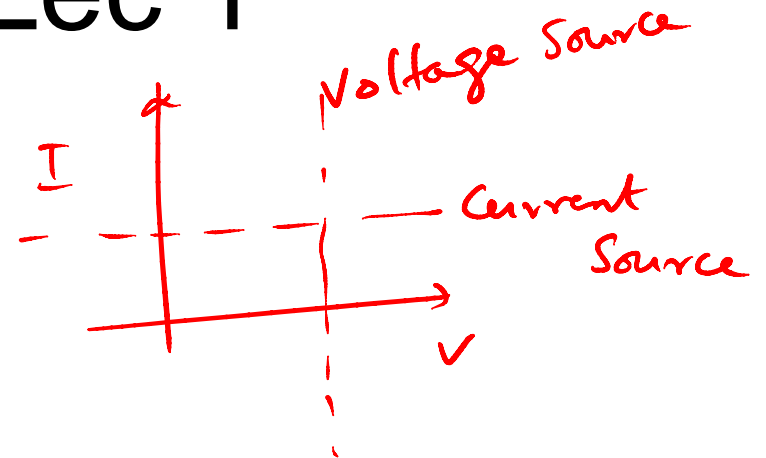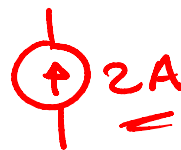


- Independent Source

- Dependent Source

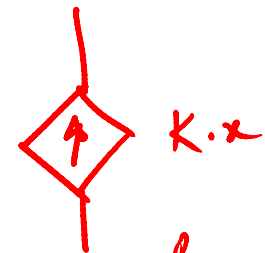
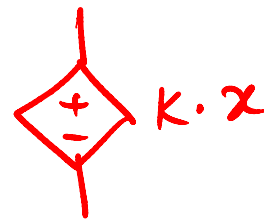


- Active Element (Source)

- Passive Element (Load)

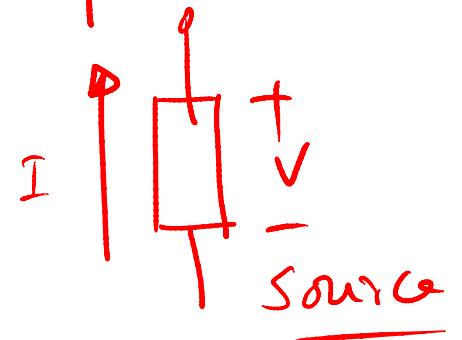


Examples of Dependent source

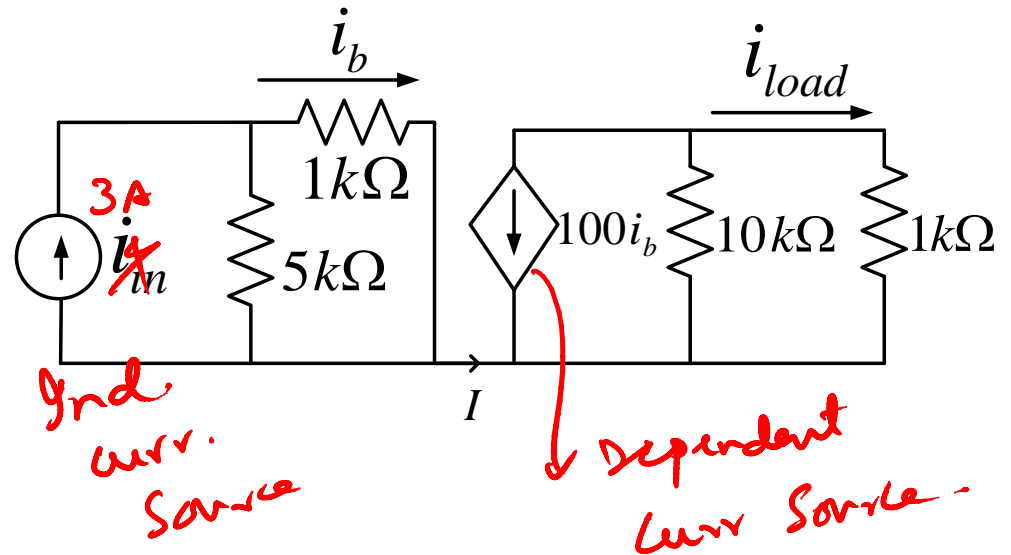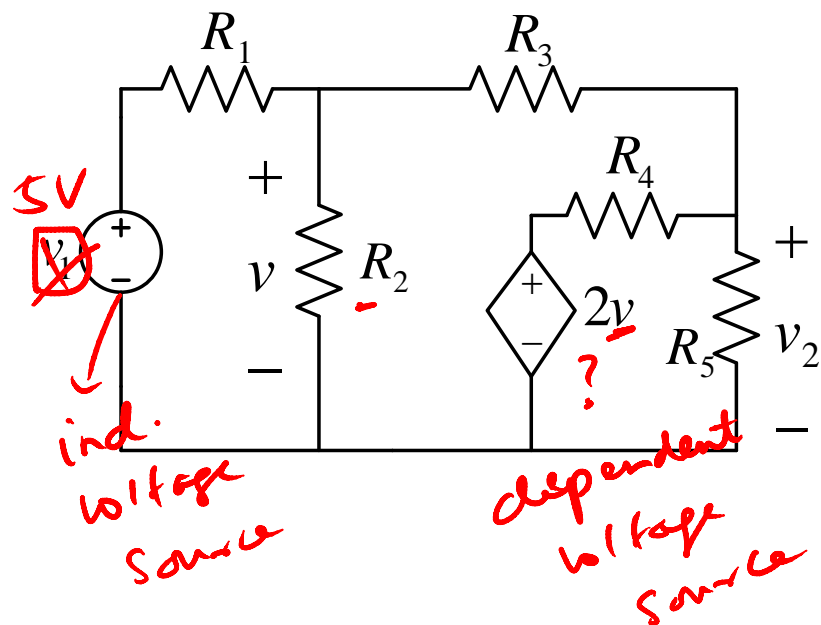

Resistance – R

Resistance and Ohm's Law

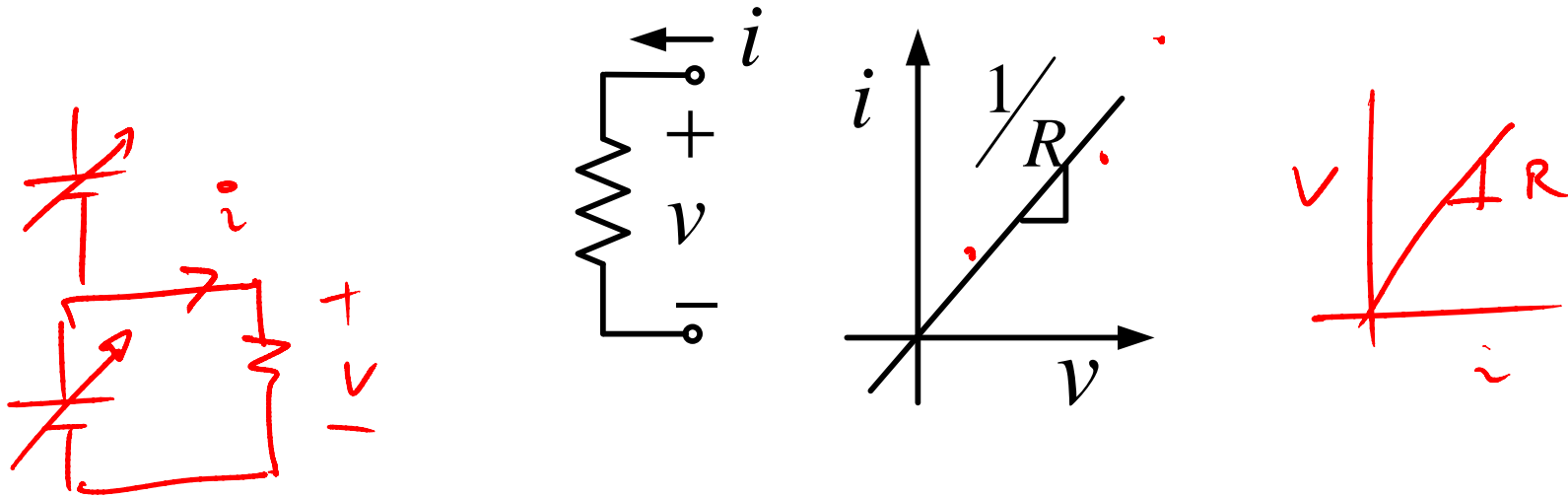
- Current flows through a metal wire or other circuit elements, it encounters some **resistance**



Ohm's law : $v = iR$

Resistance and Ohm's Law

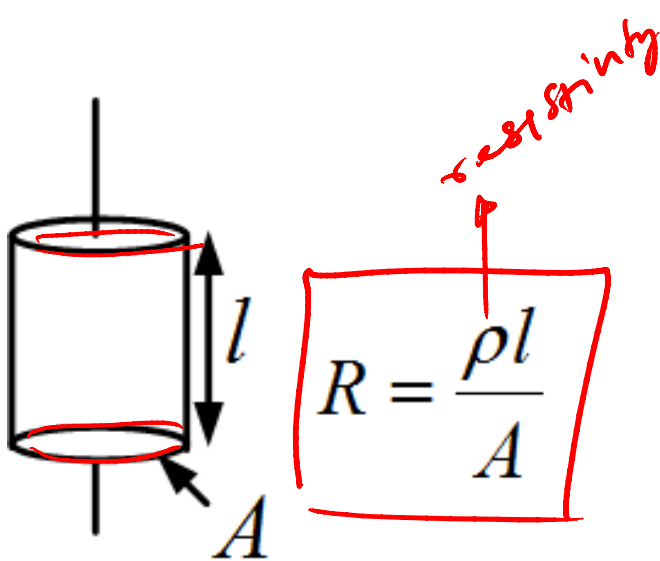- This resistance is related to the **material and size** of the element



Material	Resistivity (Ohm-meter)
Silver	1.629×10^{-8}
Copper	1.725×10^{-8} ←
Gold	2.271×10^{-8}
Aluminium	2.733×10^{-8} ←
Iron	9.98×10^{-8}
Carbon	3.5×10^{-5}

Resistor

Resistor color code

$$22 \times (1 \pm 0.05)$$

BROWN RED YELLOW

COLOR	1ST BAND	2ND BAND	3TH BAND	MULTIPLIER	TOLERANCE	
BLACK	0	0	0	1		
BROWN	1	1	1	10	± 1%	F
RED	2	2	2	100	± 2%	G
ORANGE	3	3	3	1K		
YELLOW	4	4	4	10K		
GREEN	5	5	5	100K	± 0.5%	D
BLUE	6	6	6	1M	± 0.25%	C
VIOLET	7	7	7	10M	± 0.10%	B
GREY	8	8	8		± 0.05%	A
WHITE	9	9	9			
GOLD				0.1	± 5%	J
SILVER				0.01	± 10%	K
PLAIN					± 20%	M

$$22 \times 1 = 22 \Omega$$

Brown | Red | Yellow

1 2 4

12 × 10⁴ K

= 120 K

Power in resistors

- Power is product of voltage and current.

$$p = vi$$

$$\underline{v = iR} \quad \text{ohm's law}$$

$$\underline{p = i^2 R}$$

$$i = \frac{v}{R}$$

$$\boxed{p = \frac{v^2}{R}}$$



$$V_{\max} = \sqrt{P_{\max} \times R} = \sqrt{0.25 \times 22} \approx 2.2 \text{ V}$$

$$R = 22 \Omega$$

$$P_{\max} = 0.25 \text{ W}$$


What is V_{\max} ? I_{\max} ?

power is always the for a resistor.


Load or passive element.

- Thus, power in resistor is always positive

Short Circuit and Open Circuit

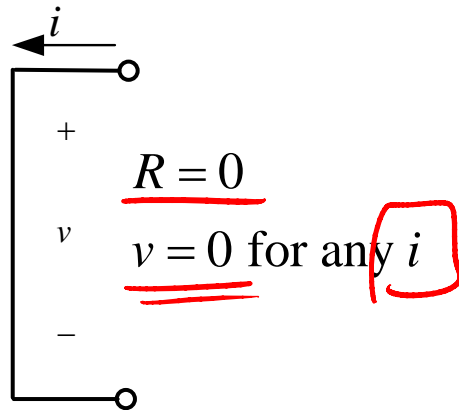

Short Circuit

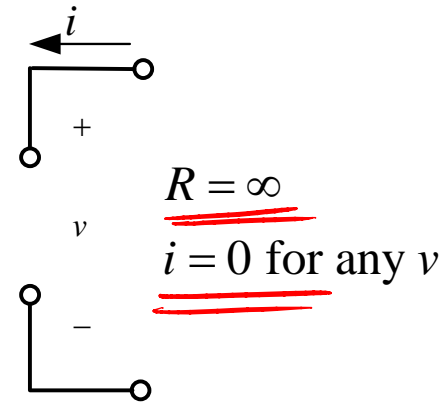

Open Circuit


- These are idealization only.

Circuit Elements

Node, branch, etc. defined

- A **node** in an electrical circuit is a point at which **two or more elements are joined** together.
- A **super node is a closed surface** enclosing part of a circuit. It may contain some sources and other nodes.


Terms of Circuit/Network Analysis

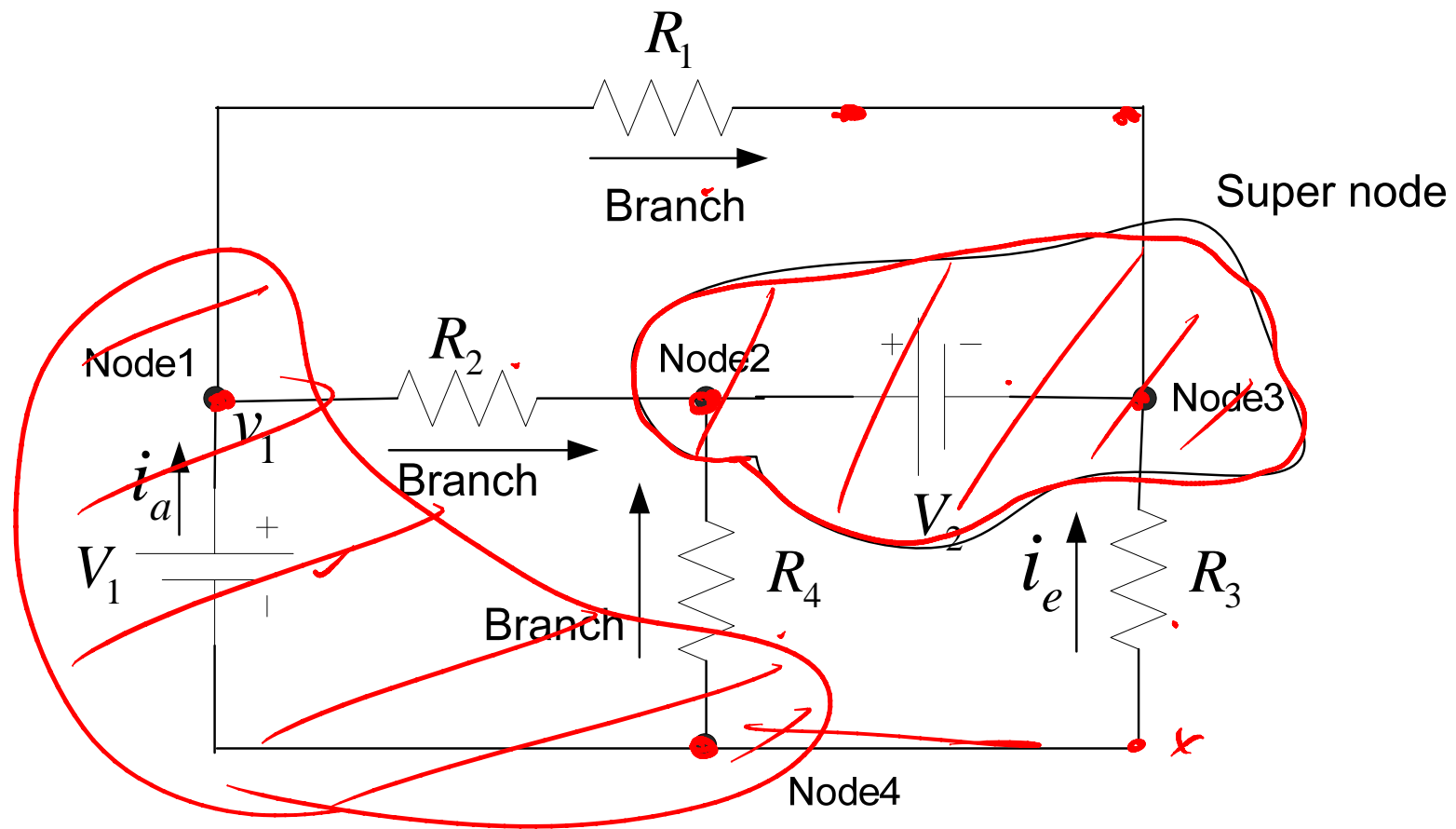

Mesh, Loop

- A **mesh is a closed path** in the circuit.
- A **loop is also a closed path** in the circuit.
- A mesh cannot have any other mesh or loop inside it.
- A loop can have meshes inside it.

Mesh and Loop

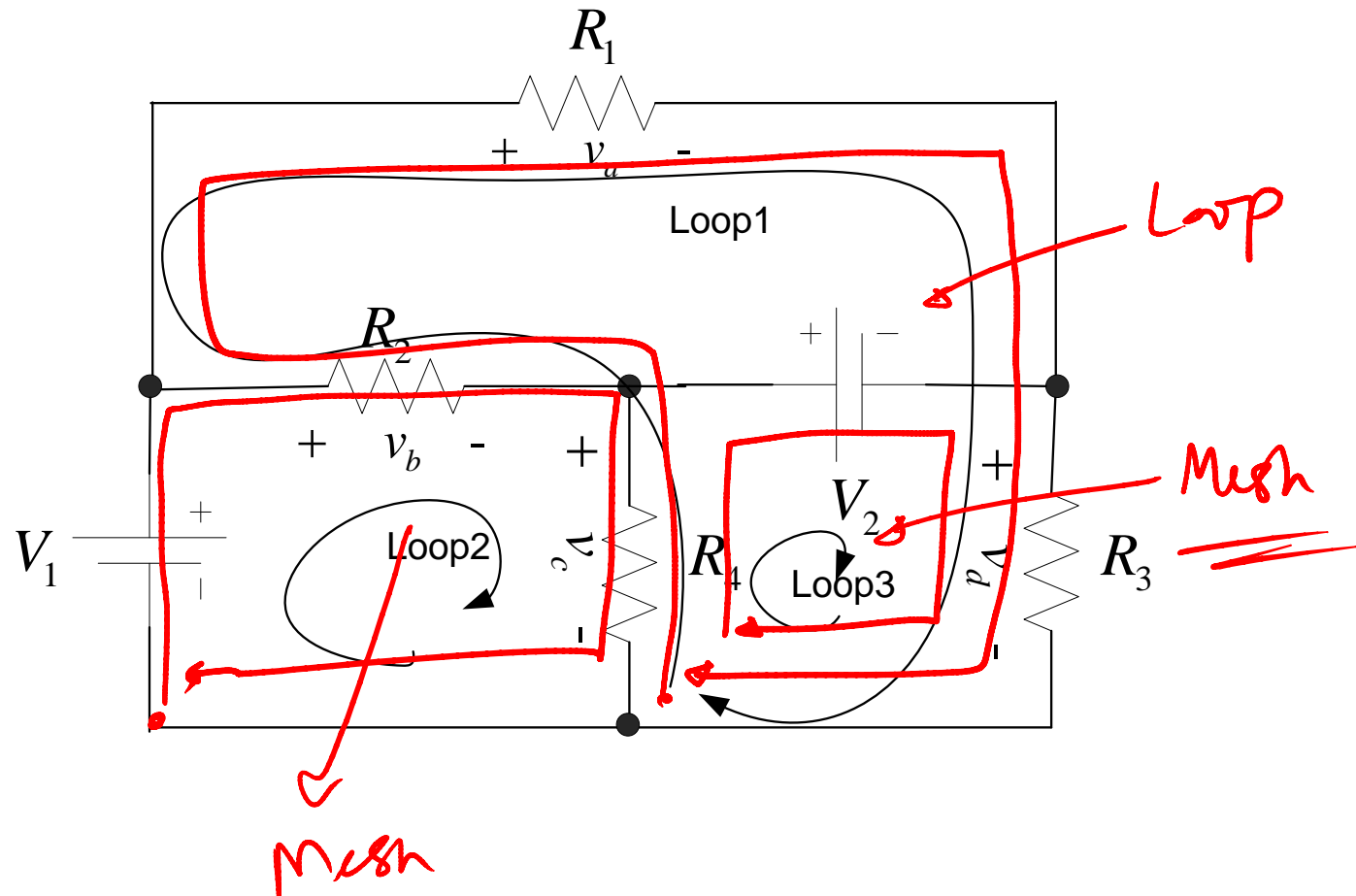


- Circuit Analysis
 - Kirchoff's Laws
 - Analysis techniques

Circuit Analysis


- To find the unknown voltage and current for various elements in the circuit
- We need to find the voltage polarity and current direction along with the magnitude
- Some elements in the circuits may be either giving power or taking power: can be known only after solving the circuit
- For unknown elements, we need to have reference polarity and direction first.

Reference direction and polarity

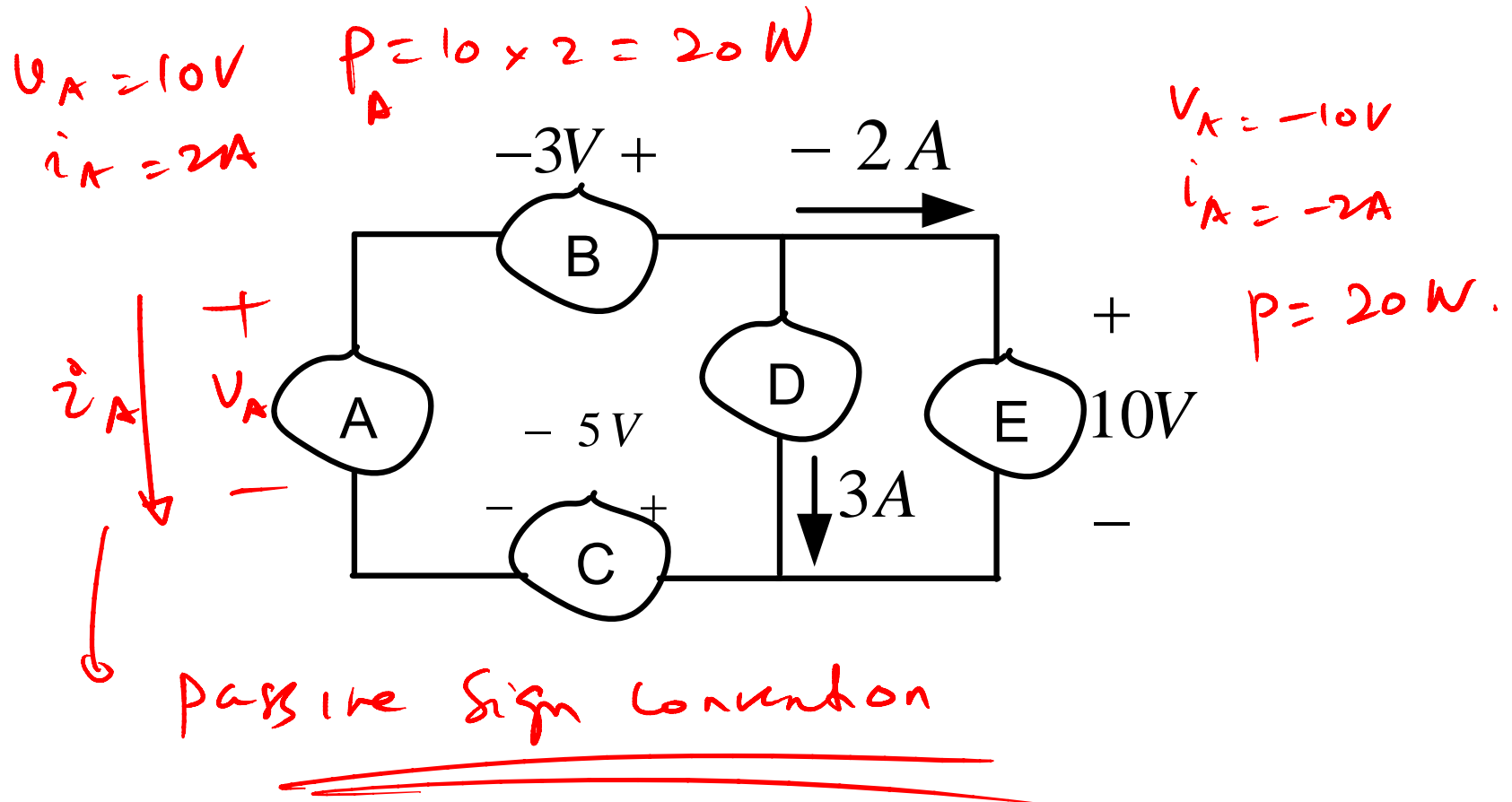

Passive sign convention

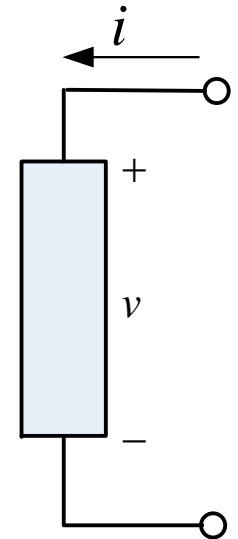- **Reference direction** (positive current direction) for current is to enter into the positive voltage terminal of the element
- If power is positive, the element is passive (dissipating energy)
- **i-v characteristics** of for various circuit elements will follow this sign convention



Kirchoff's Laws

Kirchoff's Voltage Law (KVL)

- Net voltage fall (or voltage rise) around a closed path (loop or mesh) is zero
 - Voltage rises when we go from negative polarity to positive polarity
 - Voltage falls when we go from positive polarity to negative polarity
- Imagine this law was violated!


KVL Example

$$-V_1 + v_b + v_c = 0$$

Net fall around loop 2 = 0

$$V_1 - v_b - v_c = 0$$

~~Net rise = 0~~

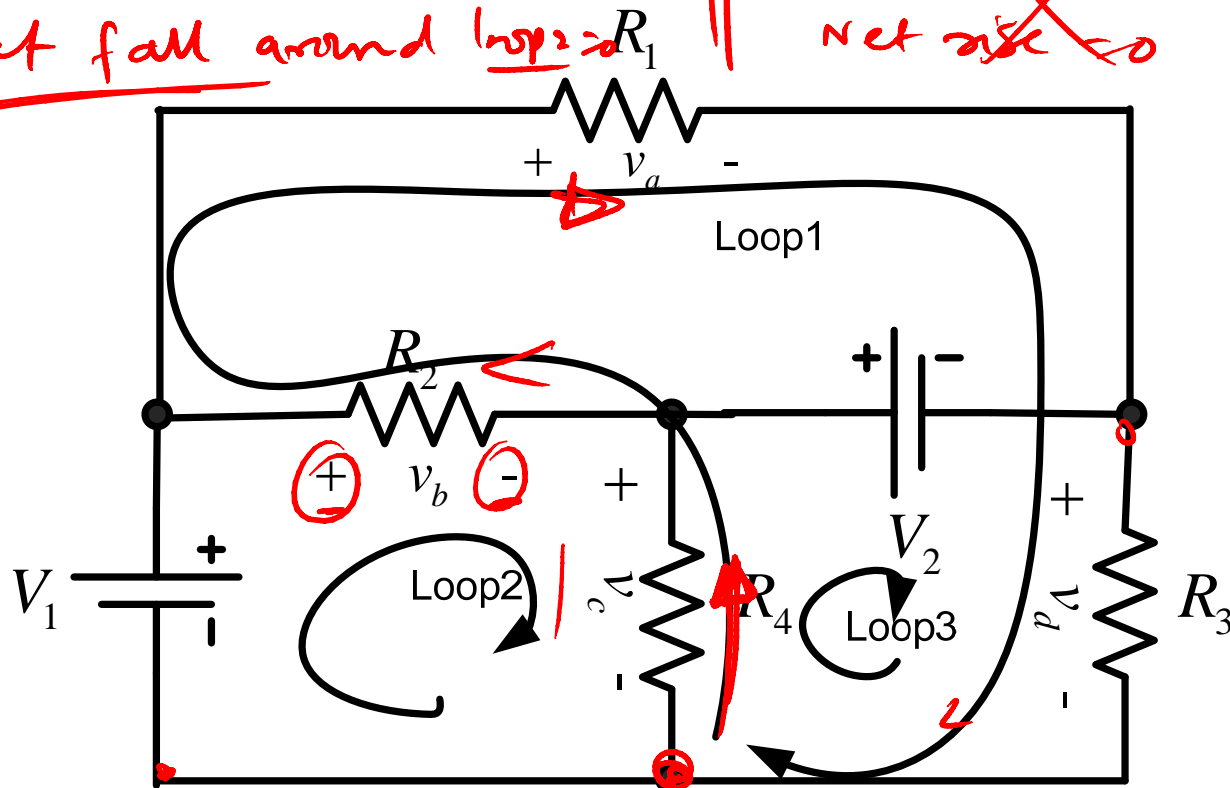

Loop3:

Net fall: $-v_c - v_b + v_a + v_d = 0$

KVL

Kirchoff's Current Law (KCL)

- Net current leaving (or entering) a node/supernode is zero
- Imagine if this law was violated!


KCL: Leaving. ✓

$$I_0 + I_1 + I_2 = 0$$

KCL Example

~~KCL entering~~
 ~~$-I_0 - I_1 - I_2 = 0$~~

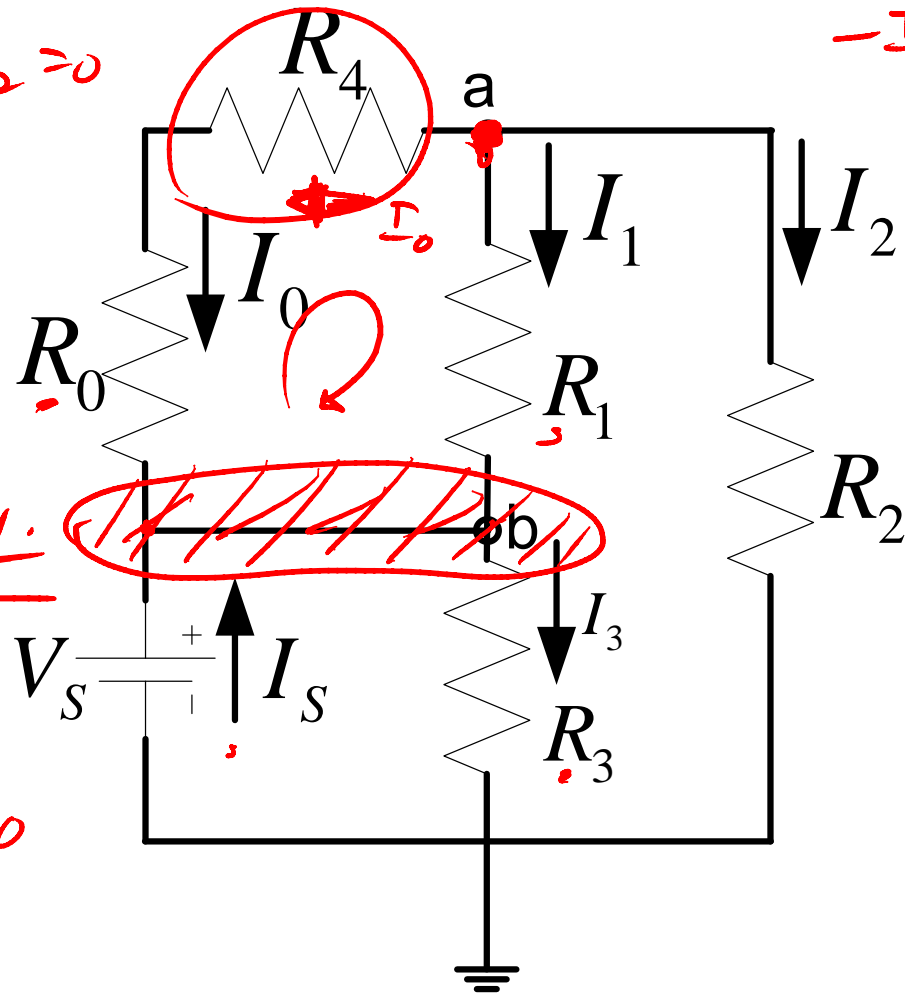KCL at S.N.
 Leaving:
 $-I_0 - I_1 + I_3 - I_S = 0$




~~R₁~~ and R₀
 are in
 series

R₁ is not
 parallel with R₀.

Series, Parallel

Series Connection

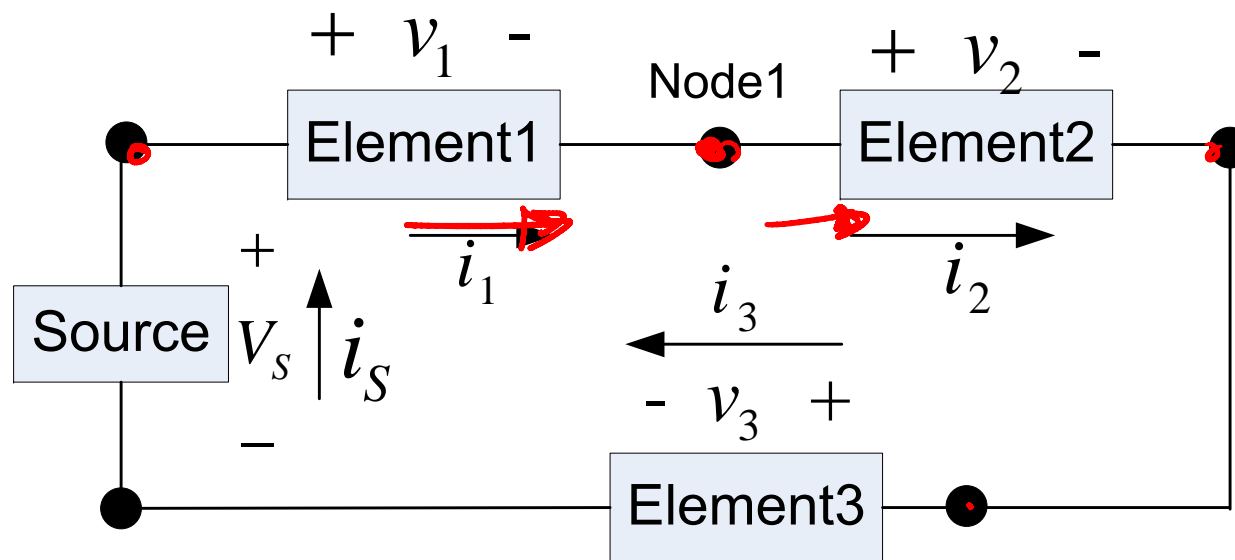- When elements are **connected end to end**
- they **carry the same current**
 - Apply KCL at any node to find this




KCL at node1
 $-i_1 + i_2 = 0$
 $i_1 = i_2$

Parallel Circuit

- If both ends of one element are connected to the corresponding ends of the other element
- Voltages across all the elements are identical

– KVL

$$-v_1 + v_2 = 0$$
$$v_1 = v_2$$

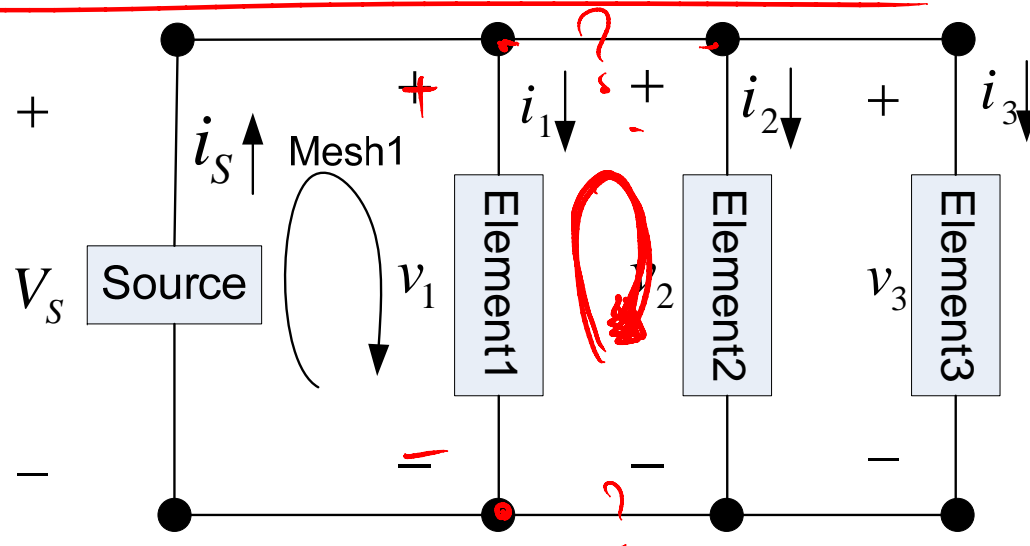


Resistances in series

- Resistors in series lead to increased resistance as they add up

$$\underline{v_1 = R_1 i}, \underline{v_2 = R_2 i}, \underline{v_3 = R_3 i}$$

$$\underline{v = v_1 + v_2 + v_3 = (R_1 + R_2 + R_3) i = R_{eq} i}$$

$$\underline{R_{eq} = R_1 + R_2 + R_3}$$

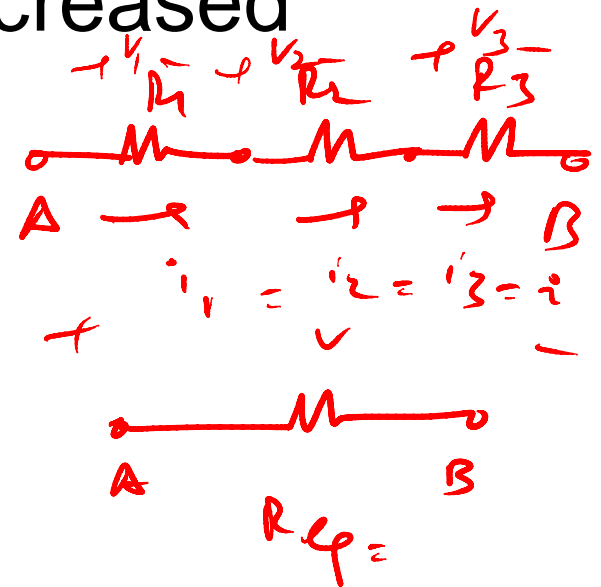

- This can be used to simplify circuits

Resistances in parallel


- Resistances in parallel reduce the equivalent resistance.

$$i_1 = \frac{v}{R_1}, i_2 = \frac{v}{R_2}, i_3 = \frac{v}{R_3}$$


$$i = i_1 + i_2 + i_3$$

$$\frac{v}{R_{eq}} = \frac{v}{R_1} + \frac{v}{R_2} + \frac{v}{R_3}$$
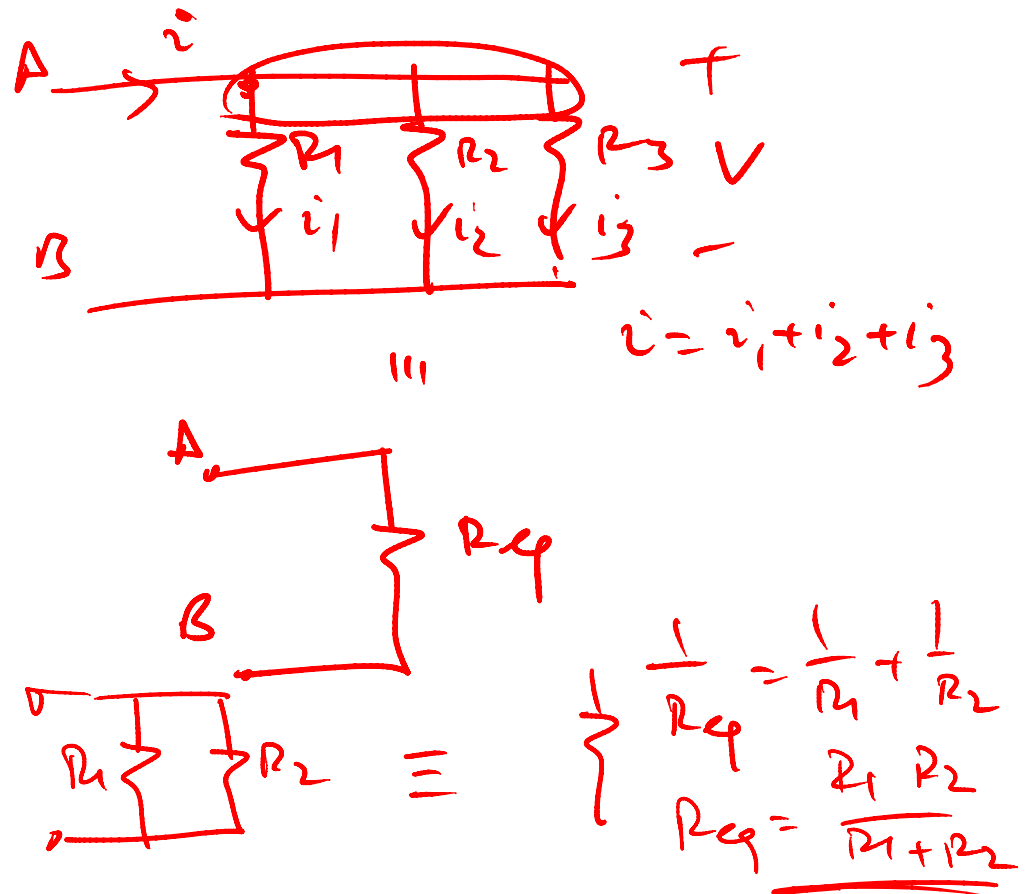
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



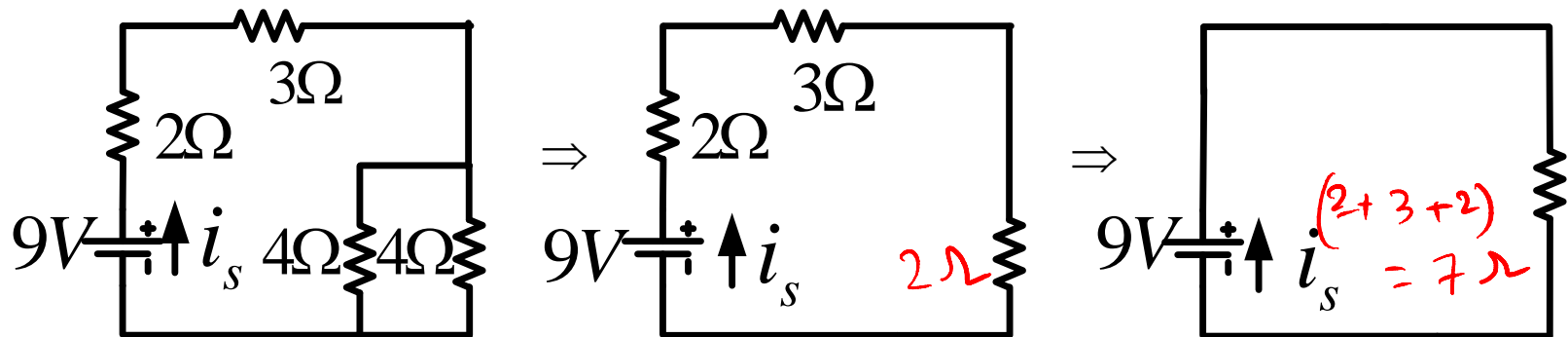Network analysis by series and parallel rules for resistance



$$4\Omega \parallel 4\Omega = \frac{4 \times 4}{4 + 4} = 2\Omega$$

$$\underline{\underline{i_s = \frac{9}{7} \text{ A}}}$$