

NATIONAL UNIVERSITY OF SINGAPORE

EXAMINATION FOR

(Semester I: 2012/2013)

EE1002 – INTRODUCTION TO CIRCUITS AND SYSTEMS

November/December 2012 - Time Allowed: 2.0 Hours

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **FOUR** (4) questions and comprises **SIX** (6) printed pages.
2. Answer all questions in **Section-A**. Answer **either** Q3(a) **or** Q3(b) and similarly **either** Q4(a) **or** Q4(b) **in Section-B**.
3. This is a **CLOSED BOOK** examination. The students may refer to the Formula Sheet given to them during the course of the examination.

SECTION-A: ANSWER ALL QUESTIONS IN THIS SECTION

Q.1 (a) Using the principles of superposition, find the current I in the circuit of Fig. Q1(a).

(10 marks)


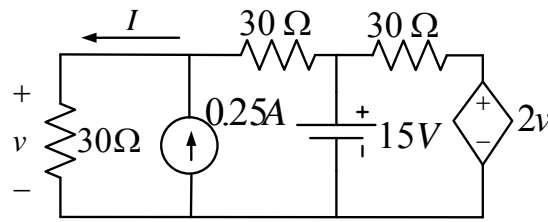


Fig. Q1(a)

(b) Write the expression for $v_o(t)$ shown in Fig. Q1(b).

(10 marks)

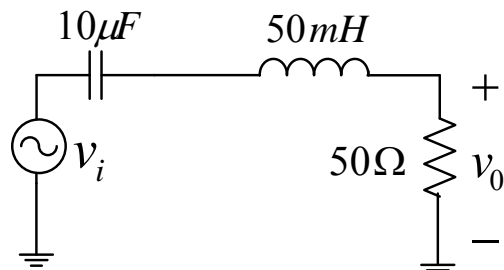

$$v_i(t) = 300\sin(1000t - 45^\circ)$$

Fig. Q1(b)

- Q.2 (a) A linear DC machine has a constant flux-density of 0.5 Wb/m^2 directed into the page of the paper, a resistance of 0.4Ω , a conductor bar of length 1.0 m , and a battery voltage of 120 V as shown in Fig. Q2(a).

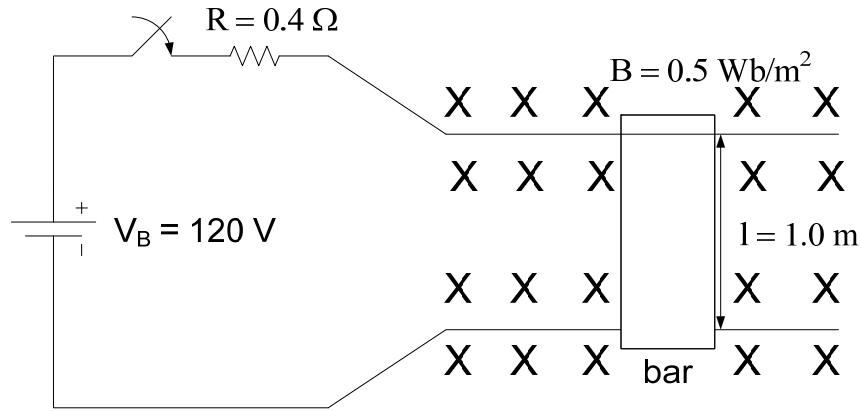


Fig. Q2(a)

- (i) If no load is applied on the bar, determine the corresponding starting current and the force induced on the bar. (3 marks)
- (ii) Determine the corresponding steady-state speed of the bar. (3 marks)
- (iii) If a load of 25 N acting in a direction opposite to the motion of the bar is applied, determine the corresponding new steady-state speed of the bar. (6 marks)
- (iv) Determine the efficiency of the linear DC motor for the operating conditions in part (iii). (3 marks)

Q.2 is continued on Page 4

- (b) A toroid has a circular cross section as shown in Fig. Q2(b) and is made from a magnetic material with a relative permeability of 2500. Its outer radius is 12 cm and inner radius is 8 cm. The magnetic flux-density in the core is 1.25 wb/m^2 measured at the mean diameter of the toroid.

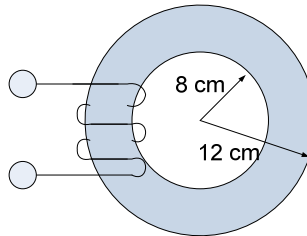


Fig. Q2(b) Magnetic circuit

- (i) If the coil consists of 250 turns, applying Ampere's law determine the magnitude of the current that must be applied to the coil to produce a magnetic flux-density of 1.25 wb/m^2 .
(3 marks)
- (ii) Determine the corresponding magnetic flux in the core.
(5 marks)
- (iii) A 10 mm air-gap is cut across the toroid shown in Fig. Q2(b). Determine the magnitude of the current that must be applied to the coil to produce the flux-density of 1.25 wb/m^2 .
(7 marks)

END OF SECTION-A

SECTION-B: ANSWER EITHER Q3(a) or Q3(b) AND Q4(a) or Q4(b)

- Q.3 (a) A 220 V DC shunt motor has the armature and field winding resistances of $0.15\ \Omega$ and $110\ \Omega$, respectively. The motor draws a line current of 5 A from the DC voltage source while running on no-load. When driving at rated load, the motor runs at a speed of 1100 rpm and draws a current of 48 A of line current. Determine the no-load speed of the motor.

(20 marks)

OR

- (b) A 10 kVA transformer has a constant core loss of 150 W and a full-load copper loss of 250 W.

Determine the transformer efficiency for the following load conditions:

- (i) full-load at 0.8 power factor lagging and
- (ii) 50% of full-load at unity power factor.

(20 marks)

- Q.4 (a) Figure Q4(a) shows the schematic circuit of a TTL signal from a signal generator (in the dotted box) connected to an RC circuit. The internal resistor of the signal generator is $500\ \Omega$. The TTL signal has a frequency of 500 Hz and 50% duty cycle.

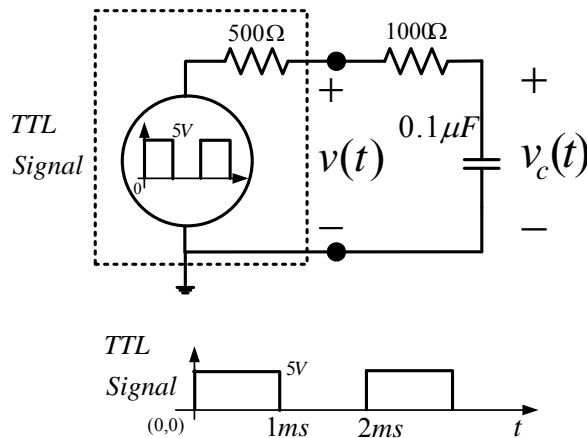


Fig. Q4(a)

Q.4(a) is continued on Page 6

Q.4(a) is continued from Page 5

- (i) What are the values of $v(t)$ at the instant when the TTL signal changes from 0V to 5V and from 5V to 0V?
(5 marks)
- (ii) Sketch and dimension the wave form of the voltage $v(t)$ for one cycle.
(5 marks)
- (iii) Write the expression for voltage, $v_c(t)$ across the capacitor for one complete cycle of the TTL signal.
(10 marks)
- (iv) If the TTL signal is changed to a sinusoidal signal of frequency 500Hz, what will be the phase difference between $v_c(t)$ and $v(t)$.
(10 marks)

OR

- (b) The circuit in Figure Q4(b) shows two loads connected to a sinusoidal source of 230V rms and 50 Hz. Load-1 is of 1000W with a lagging power factor of 0.8. Load-2 is of 500W with a leading power factor of 0.75.
 - (i) Represent both the loads as series combinations of R and C or L. Calculate the values of R and L or C for each load.
(12 marks)
 - (ii) Find the value of the capacitor, which when connected in parallel to the loads, will improve the power factor to unity as seen by the source.
(13 marks)

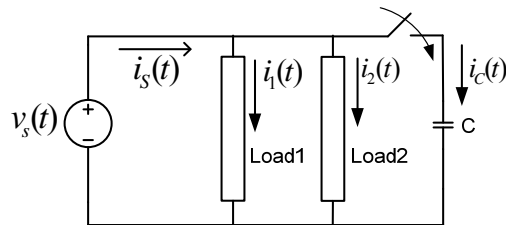


Fig. 4(b)

- (iii) Draw the phasor diagram for quantities showing $v_s(t)$, $i_s(t)$, $i_1(t)$, $i_2(t)$ and $i_c(t)$.

(5 marks)

END OF SECTION-B

END OF PAPER