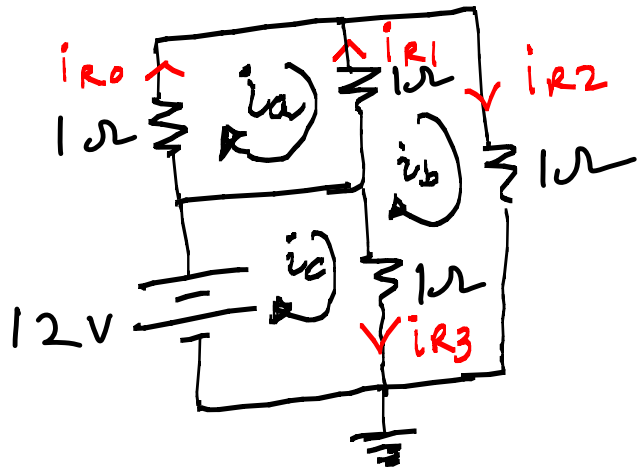


Extra Practice Questions.

Note Title

2/5/2013

Q.1



KVL for mesh a:

$$i_a \cdot 1 + (i_a - i_b) \cdot 1 = 0$$

$$2i_a - i_b = 0 \quad \text{--- (1)}$$

KVL for mesh b:

$$(i_b - i_a) \cdot 1 + i_b \cdot 1 + (i_b - i_c) \cdot 1 = 0$$

$$-i_a + 3i_b - i_c = 0 \quad \text{--- (2)}$$

KVL for mesh c:

$$-12 + (i_c - i_b) \cdot 1 = 0$$

$$-i_b + i_c = 12 \quad \text{--- (3)}$$

The equations can be put in matrix form

$$\begin{bmatrix} 2 & -1 & 0 \\ -1 & 3 & -1 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 12 \end{bmatrix}$$

Solution: $i_a = 4 \text{ A}$, $i_b = 8 \text{ A}$, $i_c = 20 \text{ A}$.



$$i_{R0} = i_a = 4 \text{ A}.$$

$$i_{R1} = i_b - i_a = 8 - 4 = 4 \text{ A}.$$

$$i_{R2} = i_b = 8 \text{ A}.$$

$$i_{R3} = i_c - i_b = 20 - 8 = 12 \text{ A}.$$

Q.2 .

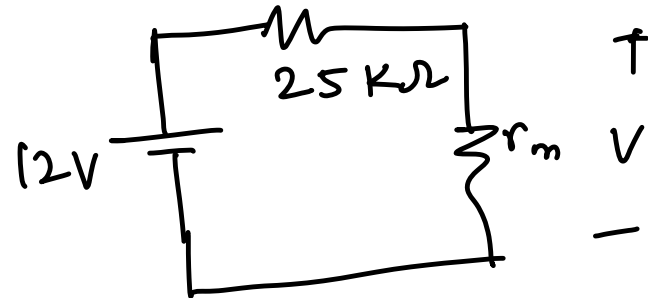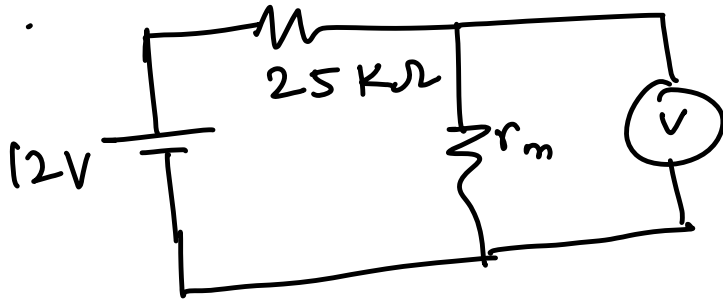

(volt-meter represented by its equivalent resistance)


Given $V = 11.81V$.

Voltage divider rule $\Rightarrow V = 12 \times \frac{r_m}{25K + r_m} = 11.81$

$$12 r_m = 25000 \times 11.81 + 11.81 r_m$$

$$r_m = \frac{25 \times 11.81}{0.19} K = \underline{\underline{1554 K \Omega}} .$$

Q.3

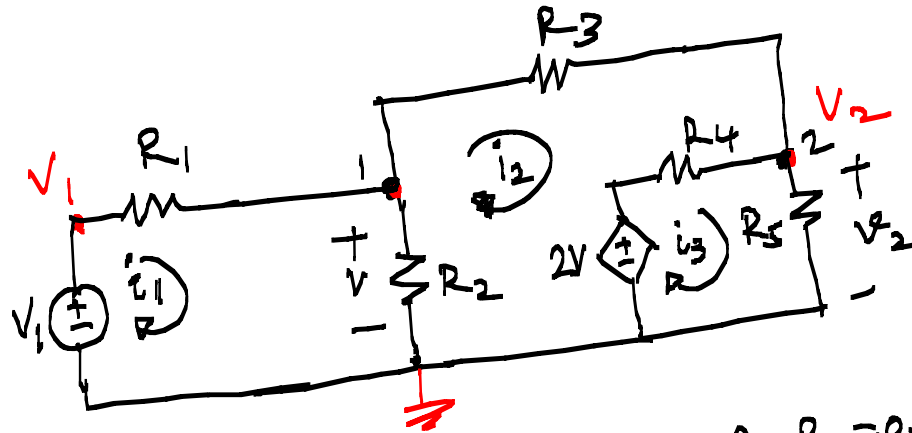

$$R_1 = 1\Omega, R_2 = 0.5\Omega, R_3 = 0.25\Omega, R_4 = 0.25\Omega, R_5 = 0.25\Omega$$

we can use either node voltage or mesh current analysis method. In mesh current analysis method, we have to solve for 3 unknown variables. In node voltage analysis method, we need to solve for 2 unknowns only.

Voltage gain $A_v = \frac{V_2}{V_1}$

Let us try node voltage analysis:

KCL at node 1 (unknowns V, V_2).

$$\frac{V-V_1}{R_1} + \frac{V}{R_2} + \frac{V-V_2}{R_3} = 0 \quad \text{--- (1)}$$

$$\frac{V-V_1}{1} + \frac{V}{0.5} + \frac{V-V_2}{0.25} = 0$$

$$(V-V_1) + 2V + 4(V-V_2) = 0$$

$$7V - 4V_2 = V_1 \quad \text{--- (1)}$$

contd...

KCL at node 2

$$\frac{V_2-2V}{R_4} + \frac{V_2}{R_5} + \frac{V_2-V}{R_3} = 0 \quad \text{--- (2)}$$

$$\frac{V_2-2V}{0.25} + \frac{V_2}{0.25} + \frac{V_2-V}{0.25} = 0$$

$$V_2 - 2V + V_2 + V_2 - V = 0$$


$$3V_2 - 3V = 0 \Rightarrow V_2 = V.$$

$$\therefore 7V_2 - 4V_2 = V_1 \Rightarrow 3V_2 = V_1,$$


$$\therefore A_v = \frac{V_2}{V_1} = \frac{1}{3} = \underline{\underline{0.33}}.$$

contd.


Q.4.

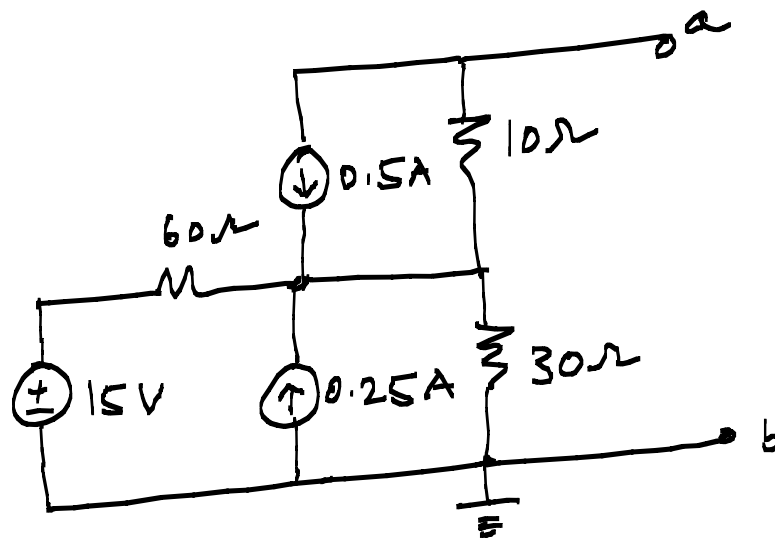

(simpler ckt with only one mesh!)

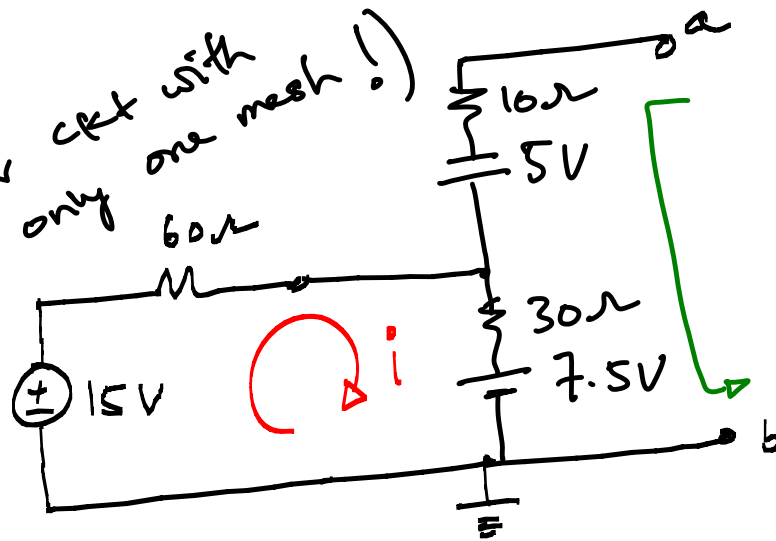

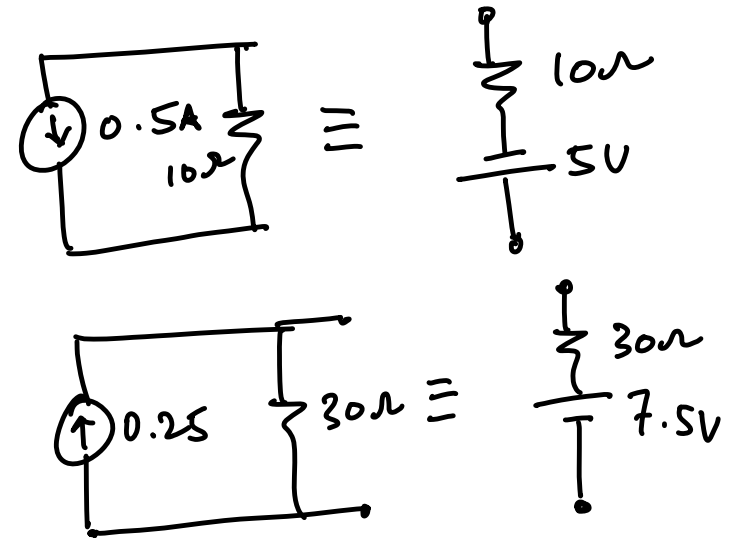- The ckt has 3 meshes.
- However, if we do source conversion it will be simpler.
- Let us convert current source with parallel resistor to voltage source with series resistor.



KVL around the only mesh: $-15 + 60i + 30i + 7.5 = 0$

$$90i = 7.5 \text{ V} \Rightarrow i = \frac{7.5}{90} \text{ A}.$$


Voltage V_{ab} (Find a path from a to b and add the voltage falls along the way!) =

$$= -5 + 30 \times i + 7.5 = -5 + \cancel{30} \times \frac{7.5}{90} + 7.5 = 5 \text{ V}.$$

$$\therefore \underline{V_{oc} = V_t = 5 \text{ V}}.$$


Thevenin resistance can be obtained by killing all the independent sources:
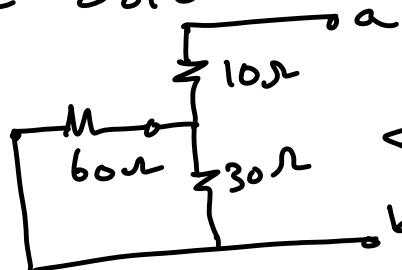
$$\therefore \underline{V_t = 5 \text{ V}, R_t = 30 \Omega.} \quad \text{Ans.}$$





$$R_{eq} = 10 + \frac{30 \times 60}{30 + 60} = 10 + 20 = 30 \Omega = R_t.$$


Q.5

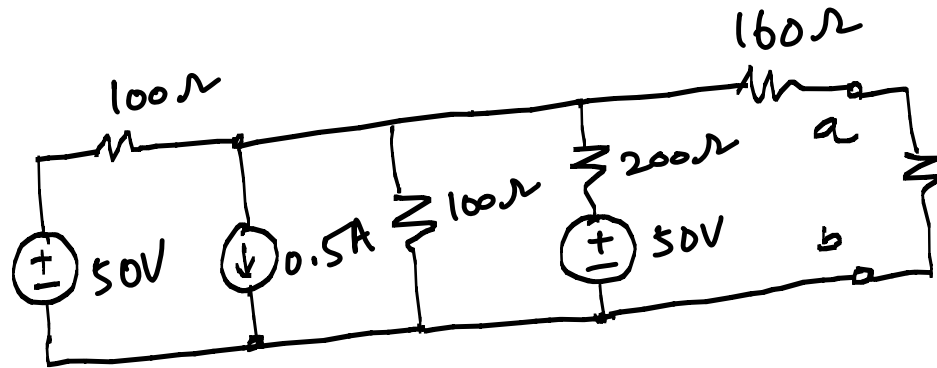

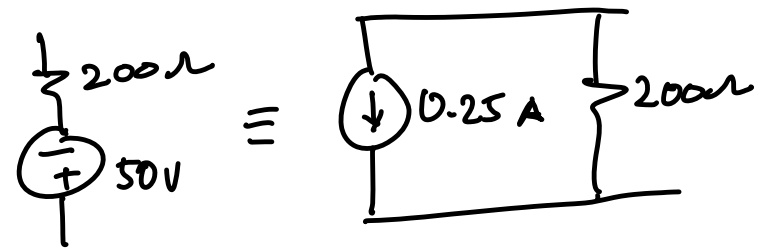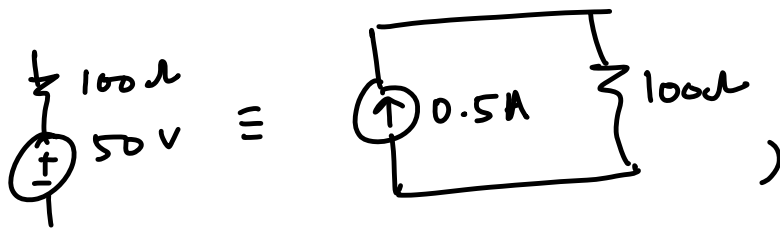
We shall convert voltage source with series resistance to current source with parallel resistance.



Circuit after source conversion:

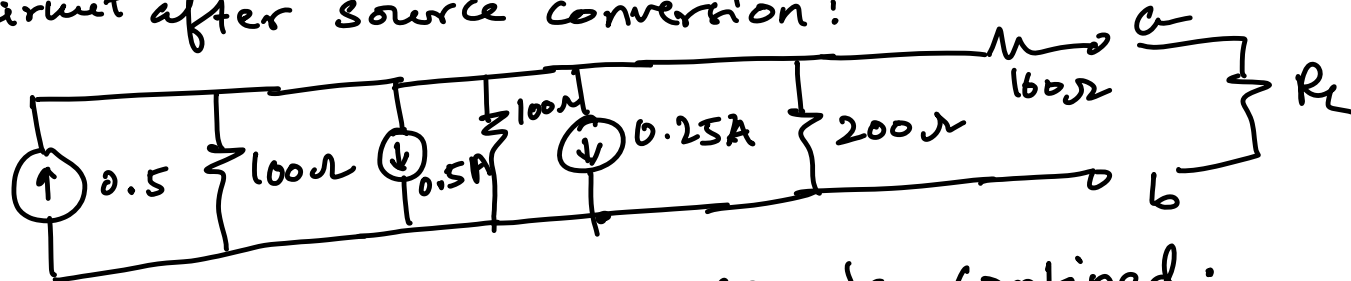

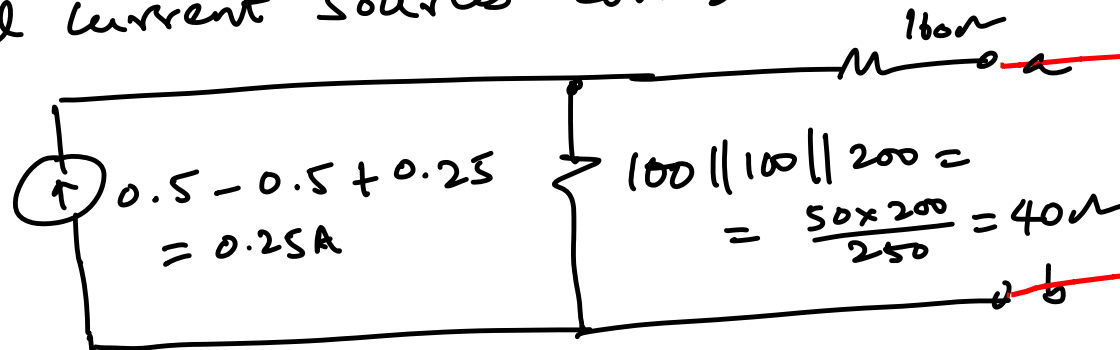Parallel current sources can be combined:



Current divider rule


$$I_{sc} = 0.25 \times \frac{40}{200}$$

$$= 0.05A$$



$$= I_N$$

R_t : killing the current source


$I_N = 0.05A$, $R_t = 200\Omega$

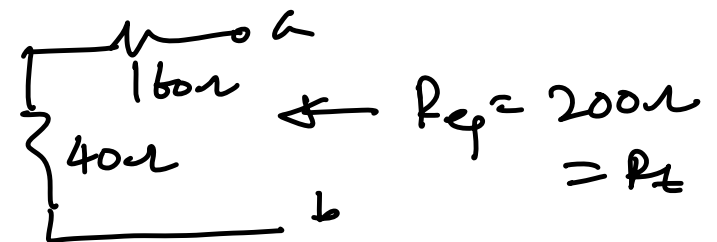


Q.6

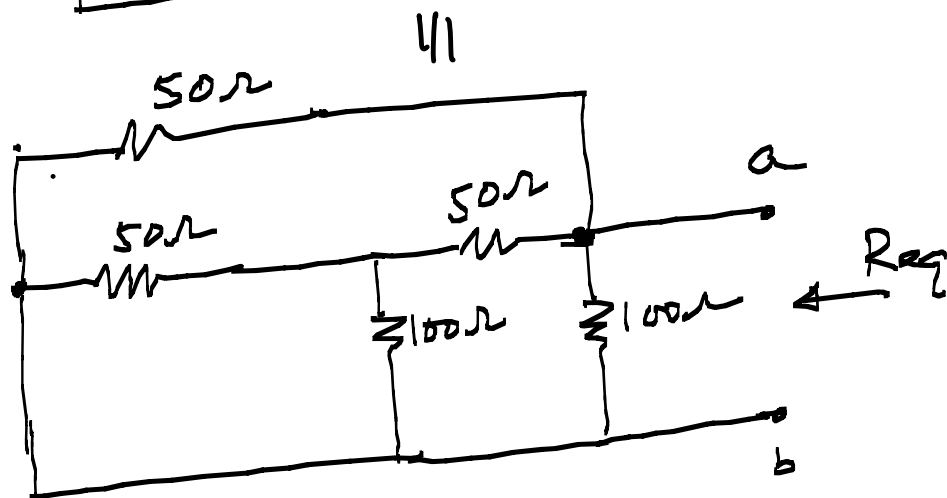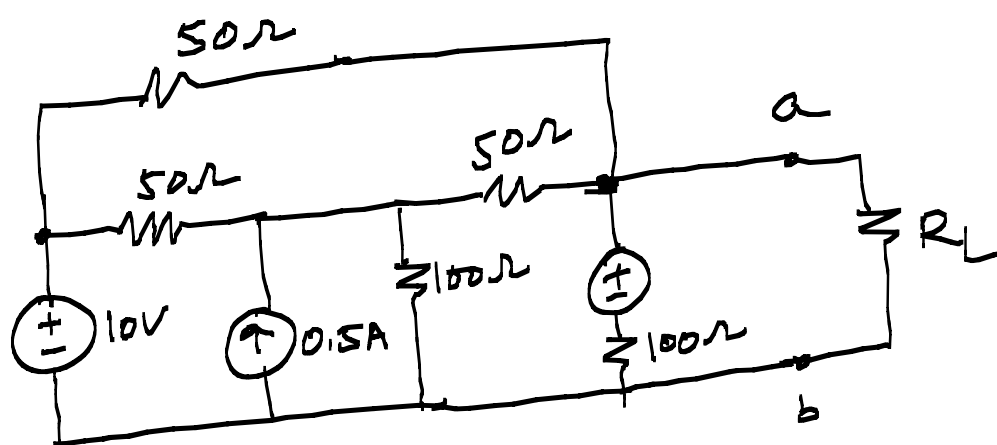


|||

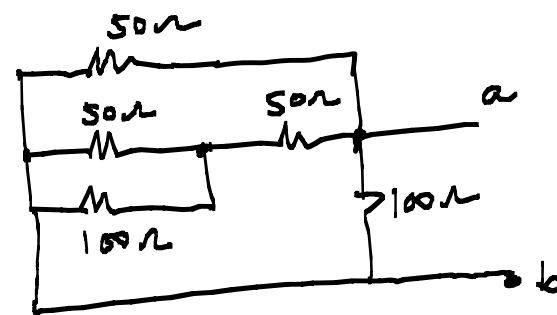

|||

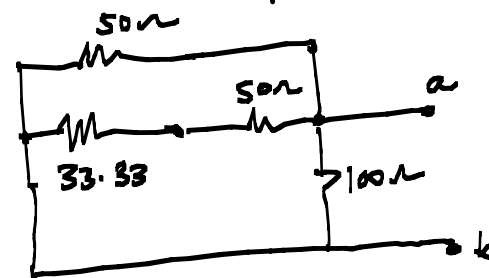

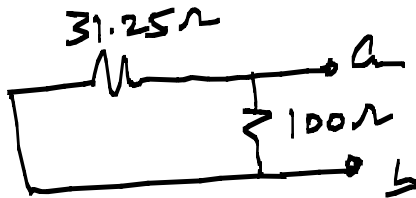- All sources are independent
- We can kill these sources and then find R_{eq} .




$$50 \parallel (33.33 + 50) = 50 \parallel 83.33$$

$$= \frac{50 \times 83.33}{133.33} = 31.25 \Omega$$

$$R_{eq} = \frac{31.25 \times 100}{131.25} = 23.81 \Omega$$

$$\underline{\underline{R_t = 23.81 \Omega}}$$

Q.7

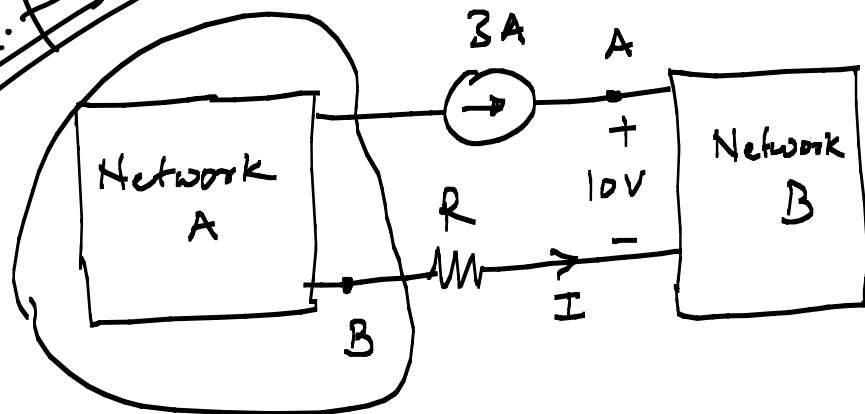

KCL at the supernode:

$$3 + I = 0 \Rightarrow I = -3 \text{ A}.$$

KVL around the loop:

As we have to find V_{AB} , let us start from point A and go counter clockwise $V_{AB} = V_A - V_B$ i.e. the voltage fall from point A to point B.

$$\therefore V_{AB} + R \cdot I - 10 = 0$$


$$\therefore V_{AB} = 10 - R \cdot I.$$

$$\text{When } R = 2 \Omega, \quad V_{AB} = 10 - 2 \times (-3) = 16 \text{ V}$$

$$\text{When } R = 0 \Omega, \quad V_{AB} = 10 - 0 \times (-3) = 10 \text{ V}$$


$$\text{When } R = 6 \Omega, \quad V_{AB} = 10 - 6 \times (-3) = 28 \text{ V}.$$

Q.8

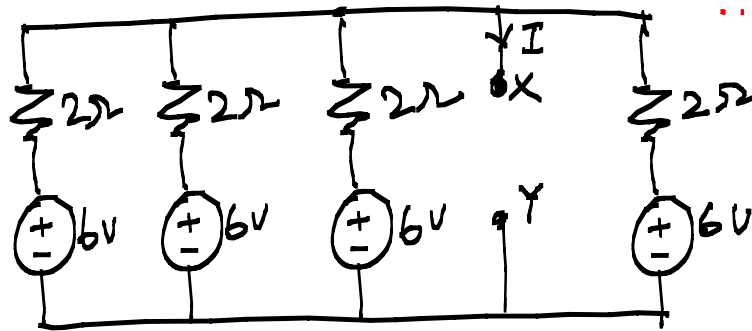


... contd

We can do source conversion:

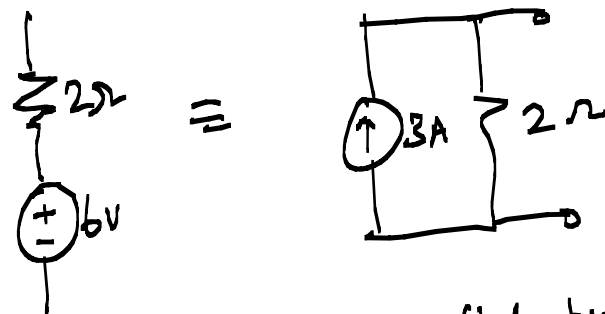

∴ with 4 such parallel branches, we get:

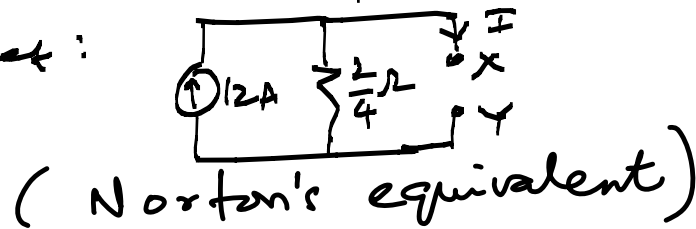

Ⓐ When open circuited:
 $I = 0$, $V_{XY} = 12 \times \frac{2}{4} = 6V$.


Ⓑ When short circuited:
 $I = 12A$, $V_{XY} = 0$.

Ⓒ When 1Ω is connected across them,

$$I = \frac{2/4}{1 + 2/4} \times 12 = \frac{2}{4+2} \times 12 = \frac{24}{4+2} = 4A$$

$$V_{XY} = 1 \times 4 = 4V$$

Q.9

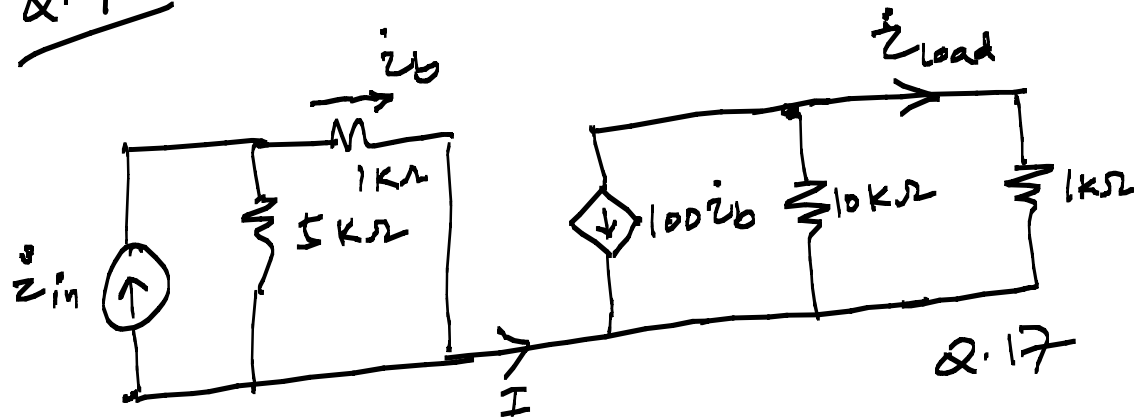

We can show that $I = 0$.


$$\therefore i_b = i_{in} \times \frac{5}{5+1} = i_{in} \times \frac{5}{6} \quad (\text{Current divider rule})$$

$$v_{load} = -100 i_b \times \frac{10}{10+1} =$$

$$= -100 \times i_{in} \times \frac{5}{6} \times \frac{10}{11}$$

$$\therefore A_i = \frac{i_{load}}{v_{in}} = -100 \times \frac{50}{66}$$

Q.10

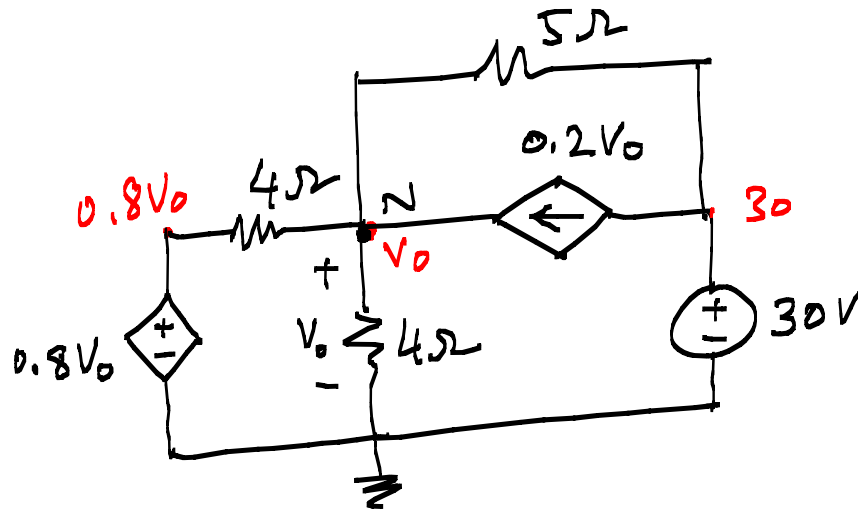

KCC at node N.

$$\frac{V_0 - 0.8V_0}{4} + \frac{V_0}{4} + \frac{V_0 - 30}{5} - 0.2V_0 = 0$$


Multiplying by 20:

$$5 \times 0.2V_0 + 5V_0 + 4(V_0 - 30) - 20 \times 0.2V_0 = 0$$

$$V_0 + 5V_0 + 4V_0 - 120 - 4V_0 = 0$$

$$6V_0 = 120 \Rightarrow V_0 = 20V.$$

2.11.

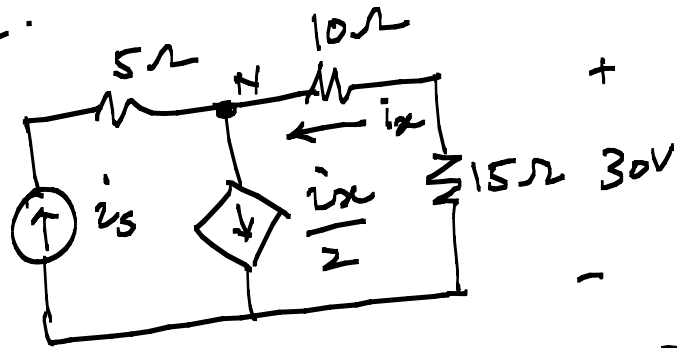


$$30V = 15 i_x \Rightarrow i_x = \frac{30}{15} = 2 A.$$

KCL at node N.

$$-i_s - i_x + \frac{i_x}{2} = 0$$

$$\therefore -i_s = i_x/2 \Rightarrow i_s = -\frac{i_x}{2} = -1 A.$$

Q.12

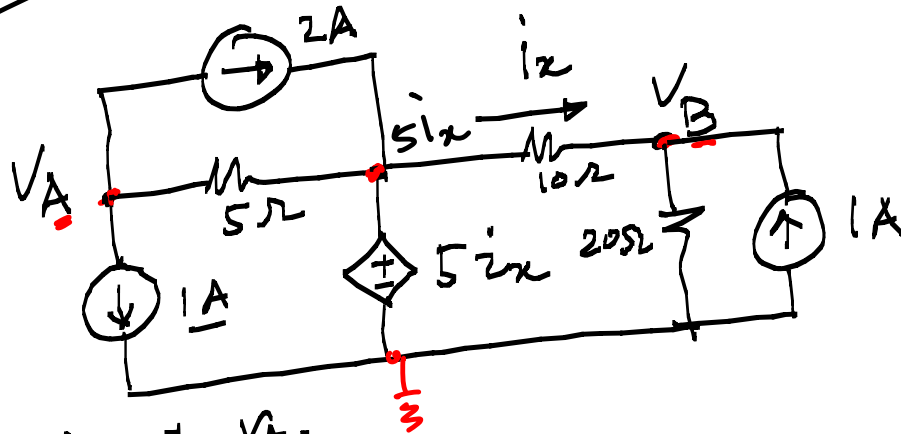

• Node voltage analysis
• unknowns V_A and V_B .

$$i_x = \frac{V_A - V_B}{10}$$

$$\Rightarrow 10i_x = V_A - V_B \Rightarrow \underline{i_x = -0.2V_B}$$

KCL at V_A :

$$1 + 2 + \frac{V_A - V_B}{5} = 0 \Rightarrow 3 + \frac{V_A - 5(-0.2V_B)}{5} = 0 \Rightarrow V_A + V_B = -15 \quad (1)$$

KCL at V_B :

$$-i_x + \frac{V_B}{20} - 1 = 0 \Rightarrow 0.2V_B + \frac{V_B}{20} - 1 = 0 \Rightarrow 4V_B + V_B - 20 = 0$$

$$\Rightarrow V_B = 4V.$$

$$\therefore V_A = -15 - V_B = -19V.$$

$$\therefore V_{AB} = V_A - V_B = -19 - 4 = -23V. \quad \underline{\text{ANS}}$$